



KINGS
ENGINEERING COLLEGE

An Autonomous Institution

Affiliated to Anna University, Chennai

Department of Computer Science and Engineering

Regulation 2021

II Year – III Semester

**CS242303- DIGITAL PRINCIPLES AND COMPUTER
ORGANIZATION**

CS242303	DIGITAL PRINCIPLES AND COMPUTER ORGANIZATION	L	T	P	C
		3	0	2	4

COURSE OBJECTIVES:

- To analyze and design combinational circuits.
- To analyze and design sequential circuits
- To understand the basic structure and operation of a digital computer.
- To study the design of data path unit, control unit for processor and to familiarize with the hazards
- To understand the concept of various memories and I/O interfacing.

UNIT I COMBINATIONAL LOGIC 9

Combinational Circuits – Karnaugh Map – Analysis and Design Procedures – Binary Adder – Subtractor – 2 Bit Magnitude Comparator – Decoder – Encoder – Multiplexers – Demultiplexers

UNIT II SYNCHRONOUS SEQUENTIAL LOGIC 9

Introduction to Sequential Circuits – Flip-Flops – operation and excitation tables, Triggering of FF, Analysis and design of clocked sequential circuits – Design – Moore/Mealy models, circuit implementation - Registers – Counters.

UNIT III COMPUTER FUNDAMENTALS 9

Functional Units of a Digital Computer: Von Neumann Architecture – Operation and Operands of Computer Hardware Instruction – Instruction Set Architecture (ISA): Memory Location, Address and Operation – Instruction and Instruction Sequencing – Addressing Modes.

UNIT IV PROCESSOR 9

Instruction Execution – Building a Data Path – Designing a Control Unit – Hardwired Control, Microprogrammed Control – Pipelining.

UNIT V MEMORY AND I/O 9

Memory Concepts and Hierarchy – Memory Management – Cache Memories: Mapping and Replacement Techniques – Virtual Memory – DMA – I/O – Accessing I/O: Parallel and Serial Interface.

TOTAL: 45 PERIODS

PRACTICAL EXERCISES:

30 PERIODS

1. Verification of Boolean theorems using logic gates.
2. Design and implementation of combinational circuits using gates for arbitrary functions.
3. Implementation of 4-bit binary adder/subtractor circuits.
4. Implementation of code converters.
5. Implementation of BCD adder, encoder and decoder circuits
6. Implementation of functions using Multiplexers.
7. Implementation of the synchronous counters
8. Implementation of a Universal Shift register.
9. Simulator based study of Computer Architecture

TOTAL : 75 PERIODS

COURSE OUTCOMES:

At the end of this course, the students will be able to:

- CO1: Design various combinational digital circuits using logic gates
- CO2 : Design sequential circuits and analyze the design procedures
- CO3: State the fundamentals of computer systems and analyze the execution of an instruction
- CO4 : Analyze different types of control design and identify hazards
- CO5: Identify the characteristics of various memory systems and I/O communication

TEXTBOOKS:

- 1.M. Morris Mano, Michael D. Ciletti, “Digital Design : With an Introduction to the Verilog HDL, VHDL, and System Verilog”, Sixth Edition, Pearson Education, 2018.
- 2. David A. Patterson, John L. Hennessy, “Computer Organization and Design, The Hardware/Software Interface”, Sixth Edition, Morgan Kaufmann/Elsevier, 2020.

REFERENCES:

- 1. Carl Hamacher, Zvonko Vranesic, Safwat Zaky, Naraig Manjikian, “Computer Organization and Embedded Systems”, Sixth Edition, Tata McGraw-Hill, 2012.
- 2. William Stallings, “Computer Organization and Architecture – Designing for Performance”, Tenth Edition, Pearson Education, 2016.
- 3. M. Morris Mano, “Digital Logic and Computer Design”, Pearson Education, 2016.

CO’s-PO’s & PSO’s MAPPING

CO’s	PO’s												PSO’s		
	1	2	3	4	5	6	7	8	9	10	11	12	1	2	3
1	3	3	3	3	3	2	1	1	1	1	2	3	2	3	3
2	3	3	3	3	2	1	1	1	1	1	2	3	1	2	2
3	3	3	3	3	2	2	1	1	1	1	2	3	2	3	1
4	3	3	3	3	1	1	1	1	1	1	1	2	1	3	1
5	3	3	3	3	1	2	1	1	1	1	1	2	1	2	1
AVg.	3	3	3	3	1.8	1.6	1	1	1	1	1.6	2.6	1.4	2.6	1.6

1 - low, 2 - medium, 3 - high, '-' - no correlation

UNIT I
COMBINATIONAL LOGIC

Combinational Circuits – Karnaugh Map - Analysis and Design Procedures – Binary Adder
–Subtractor – Decimal Adder - Magnitude Comparator – Decoder – Encoder – Multiplexers -
Demultiplexers

INTRODUCTION:

The digital system consists of two types of circuits, namely


- (i) Combinational circuits
- (ii) Sequential circuits

Combinational circuit consists of logic gates whose output at any time is determined from the present combination of inputs. The logic gate is the most basic building block of combinational logic. The logical function performed by a combinational circuit is fully defined by a set of Boolean expressions.

Sequential logic circuit comprises both logic gates and the state of storage elements such as flip-flops. As a consequence, the output of a sequential circuit depends not only on present value of inputs but also on the past state of inputs.

In the previous chapter, we have discussed binary numbers, codes, Boolean algebra and simplification of Boolean function and logic gates. In this chapter, formulation and analysis of various systematic designs of combinational circuits will be discussed.

A combinational circuit consists of input variables, logic gates, and output variables. The logic gates accept signals from inputs and output signals are generated according to the logic circuits employed in it. Binary information from the given data transforms to desired output data in this process. Both input and output are obviously the binary signals, *i.e.*, both the input and output signals are of two possible states, logic 1 and logic 0.

 

Block diagram of a combinational logic circuit

For n number of input variables to a combinational circuit, 2^n possible combinations of binary input states are possible. For each possible combination, there is one and only one possible output combination. A combinational logic circuit can be described by m Boolean functions and each output can be expressed in terms of n input variables.

DESIGN PROCEDURE:

Any combinational circuit can be designed by the following steps of design procedure.

1. The problem is stated.
2. Identify the input and output variables.
3. The input and output variables are assigned letter symbols.
4. Construction of a truth table to meet input -output requirements.
5. Writing Boolean expressions for various output variables in terms of input variables.
6. The simplified Boolean expression is obtained by any method of minimization— algebraic method, Karnaugh map method, or tabulation method.
7. A logic diagram is realized from the simplified boolean expression using logic gates.

The following guidelines should be followed while choosing the preferred form for hardware implementation:

1. The implementation should have the minimum number of gates, with the gates used having the minimum number of inputs.
2. There should be a minimum number of interconnections.
3. Limitation on the driving capability of the gates should not be ignored.


ARITHMETIC CIRCUITS - BASIC BUILDING BLOCKS:

In this section, we will discuss those combinational logic building blocks that can be used to perform addition and subtraction operations on binary numbers. Addition and subtraction are the two most commonly used arithmetic operations, as the other two, namely multiplication and division, are respectively the processes of repeated addition and repeated subtraction.

The basic building blocks that form the basis of all hardware used to perform the arithmetic operations on binary numbers are half-adder, full adder, half-subtractor, full-subtractor.

Half-Adder:

 A half-adder is a combinational circuit that can be used to add two binary bits. It has two inputs that represent the two bits to be added and two outputs, with one producing the SUM output and the other producing the CARRY.




Block schematic of half-adder

The truth table of a half-adder, showing all possible input combinations and the corresponding outputs are shown below.


Inputs		Outputs	
A	B	Carry (C)	Sum (S)
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Truth table of half-adder

K-map simplification for carry and sum:

 

Carry = A . B

 

**Sum = AB' + A'B
= A ⊕ B**


The Boolean expressions for the SUM and CARRY outputs are given by the equations,

Sum, S = A'B + AB' = A ⊕ B

Carry, C = A . B

The first one representing the SUM output is that of an EX-OR gate, the second one representing the CARRY output is that of an AND gate.

The logic diagram of the half adder is,

 


Logic Implementation of Half-adder

Full-Adder:

A full adder is a combinational circuit that forms the arithmetic sum of three input bits. It consists of 3 inputs and 2 outputs.

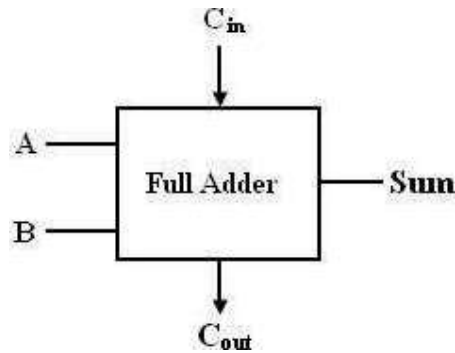Two of the input variables, represent the significant bits to be added. The third input represents the carry from previous lower significant position. The block diagram of full adder is given by,



Block schematic of full-adder

The full adder circuit overcomes the limitation of the half-adder, which can be used to add two bits only. As there are three input variables, eight different input combinations are possible. The truth table is shown below,

Truth Table:

Inputs			Outputs	
A	B	C _{in}	Sum (S)	Carry (C _{out})
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

To derive the simplified Boolean expression from the truth table, the Karnaugh map method is adopted as,

		For Carry			
		BC _{in}			
A		00	01	11	10
0	0	0	0	1	0
1	0	1	1	1	1

$$\text{Carry, } C_{out} = AB + AC_{in} + BC_{in}$$

		For Sum			
		BC _{in}			
A		00	01	11	10
0	0	0	1	0	1
1	1	1	0	1	0


$$\text{Sum, } S = A'B'C_{in} + A'BC'_{in} + AB'C'_{in} + ABC_{in}$$

The Boolean expressions for the SUM and CARRY outputs are given by the equations,

$$\text{Sum, } S = A'B'C_{in} + A'BC'_{in} + AB'C'_{in} + ABC_{in}$$

$$\text{Carry, } C_{out} = AB + AC_{in} + BC_{in}$$

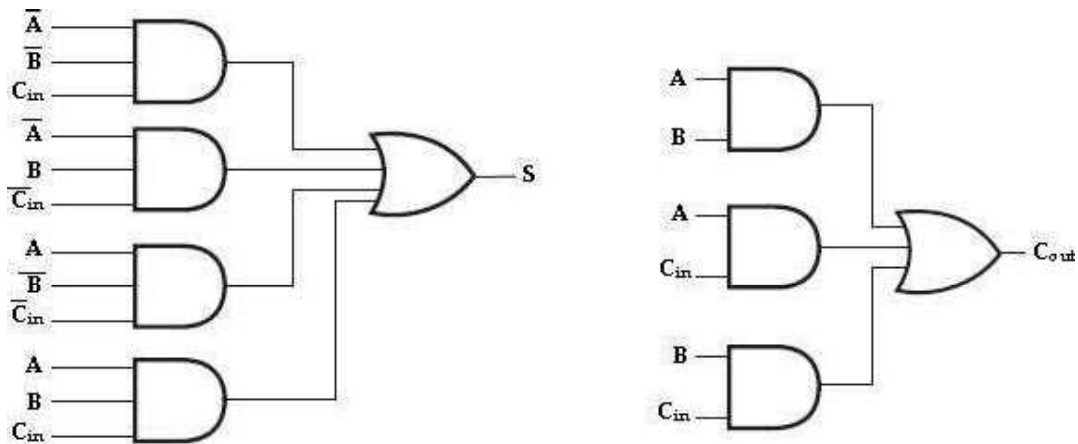The logic diagram for the above functions is shown as,



Implementation of full-adder in Sum of Products

The logic diagram of the full adder can also be implemented with two half-adders and one OR gate. The S output from the second half adder is the exclusive-OR of C_{in} and the output of the first half-adder, giving


$$\begin{aligned} \text{Sum} &= C_{in} \dagger (A \dagger B) \\ &= C_{in} \dagger (A'B + AB') \\ &= C'_{in} (A'B + AB') + C_{in} (A'B + AB')' \\ &= C'_{in} (A'B + AB') + C_{in} (AB + A'B') \\ &= A'BC'_{in} + AB'C'_{in} + ABC_{in} + A'B'C_{in} \end{aligned}$$

$$[x \dagger y = x'y + xy']$$

$$[(x'y + xy)'] = (xy + x'y)']$$

and the carry output is,

$$\begin{aligned}
 \text{Carry, } C_{out} &= AB + C_{in} (A'B + AB') \\
 &= AB + A'BC_{in} + AB'C_{in} \\
 &= AB (C_{in} + 1) + A'BC_{in} + AB'C_{in} && [C_{in} + 1 = 1] \\
 &= ABC_{in} + AB + A'BC_{in} + AB'C_{in} \\
 &= AB + AC_{in} (B + B') + A'BC_{in} \\
 &= AB + AC_{in} + A'BC_{in} \\
 &= AB (C_{in} + 1) + AC_{in} + A'BC_{in} && [C_{in} + 1 = 1] \\
 &= ABC_{in} + AB + AC_{in} + A'BC_{in} \\
 &= AB + AC_{in} + BC_{in} (A + A') \\
 &= AB + AC_{in} + BC_{in}.
 \end{aligned}$$

 

Implementation of full adder with two half-adders and an OR gate

Half -Subtractor:

A *half-subtractor* is a combinational circuit that can be used to subtract one binary digit from another to produce a DIFFERENCE output and a BORROW output. The BORROW output here specifies whether a 1 has been borrowed to perform the subtraction.




Block schematic of half-subtractor

The truth table of half-subtractor, showing all possible input combinations and the corresponding outputs are shown below.

Input		Output	
A	B	Difference (D)	Borrow (B _{out})
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

 K-map simplification for half subtractor:




The Boolean expressions for the DIFFERENCE and BORROW outputs are given by the equations,

Difference, D = $A'B + AB' = A \oplus B$

Borrow, B_{out} = $A' \cdot B$

The first one representing the DIFFERENCE (D) output is that of an exclusive-OR gate, the expression for the BORROW output (B_{out}) is that of an AND gate with input A complemented before it is fed to the gate.

 The logic diagram of the half subtractor is,




Logic Implementation of Half-Subtractor

Comparing a half-subtractor with a half-adder, we find that the expressions for the SUM and DIFFERENCE outputs are just the same. The expression for BORROW in the case of the half-subtractor is also similar to what we have for CARRY in the case of the half-adder. If the input A, ie., the minuend is complemented, an AND gate can be used to implement the BORROW output.

Full Subtractor:

A *full subtractor* performs subtraction operation on two bits, a minuend and a subtrahend, and also takes into consideration whether a '1' has already been borrowed by the previous adjacent lower minuend bit or not.

 As a result, there are three bits to be handled at the input of a full subtractor, namely the two bits to be subtracted and a borrow bit designated as B_{in}. There are two outputs, namely the DIFFERENCE output D and the BORROW output B_o. The





BORROW output bit tells whether the minuend bit needs to borrow a 1 from the next possible higher minuend bit.

Block schematic of full-adder

The truth table for full-subtractor is,

Inputs			Outputs	
A	B	B _{in}	Difference(D)	Borrow(B _{out})
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

  K-map simplification for full-subtractor:



Difference, D = A'B'B_{in} + A'BB'_{in} + AB'B'_{in} + ABB_{in}



Borrow, B_{out} = A'B + A'B_{in} + BB_{in}

The Boolean expressions for the DIFFERENCE and BORROW outputs are given by the equations,

Difference, D = A'B'B_{in} + A'BB'_{in} + AB'B'_{in} + ABB_{in}

Borrow, B_{out} = A'B + A'B_{in} + BB_{in}

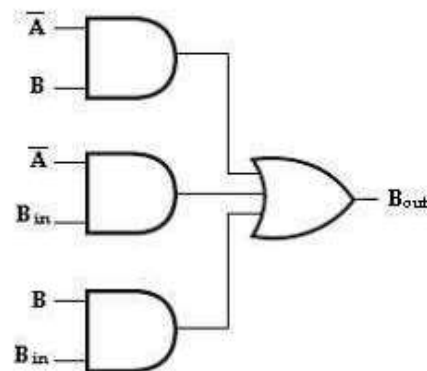 The logic diagram for the above functions is shown as,



Implementation of full-adder in Sum of Products

The logic diagram of the full-subtractor can also be implemented with two half-subtractors and one OR gate. The difference, D output from the second half subtractor is the exclusive-OR of B_{in} and the output of the first half-subtractor, giving **Difference, D**


$$\begin{aligned}
 B_{in} \dagger (A \dagger B) &= B_{in} \dagger (A'B + AB') & [x \dagger y = x'y + xy'] \\
 &= B'_{in} (A'B + AB') + B_{in} (A'B + AB')' & [(x'y + xy')' = (xy + x'y')] \\
 &= B'_{in} (A'B + AB') + B_{in} (AB + A'B') \\
 &= A'BB'_{in} + AB'B'_{in} + ABB_{in} + A'B'B_{in}
 \end{aligned}$$

and the borrow output is,

$$\begin{aligned}
 \text{Borrow, } B_{out} &= A'B + B_{in} (A'B + AB')' & [(x'y + xy')' = (xy + x'y')] \\
 &= A'B + B_{in} (AB + A'B') \\
 &= A'B + ABB_{in} + A'B'B_{in} \\
 &= A'B (B_{in} + 1) + ABB_{in} + A'B'B_{in} & [C_{in} + 1 = 1] \\
 &= A'BB_{in} + A'B + ABB_{in} + A'B'B_{in} \\
 &= A'B + BB_{in} (A + A') + A'B'B_{in} & [A + A' = 1] \\
 &= A'B + BB_{in} + A'B'B_{in} \\
 &= A'B (B_{in} + 1) + BB_{in} + A'B'B_{in} & [C_{in} + 1 = 1] \\
 &= A'BB_{in} + A'B + BB_{in} + A'B'B_{in} \\
 &= A'B + BB_{in} + A'B_{in} (B + B') \\
 &= A'B + BB_{in} + A'B_{in}
 \end{aligned}$$

Therefore,

 
we can implement full-subtractor using two half-subtractors and OR gate as,



Implementation of full-subtractor with two half-subtractors and an OR gate

Binary Adder (Parallel Adder):

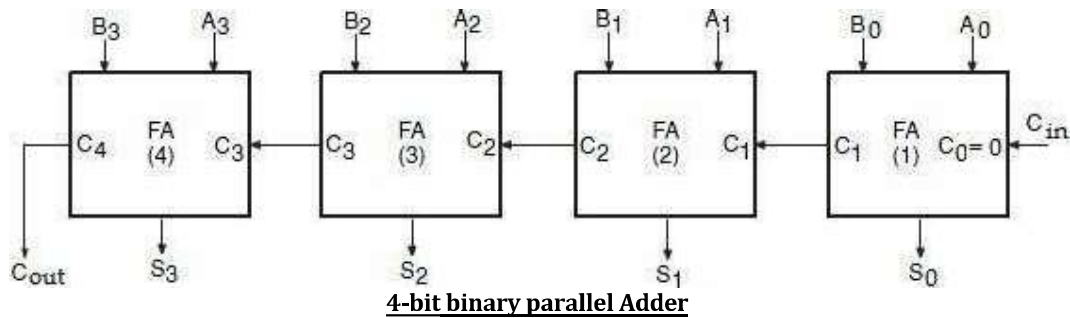The 4-bit binary adder using full adder circuits is capable of adding two 4-bit numbers resulting in a 4-bit sum and a carry output as shown in figure below.



Since all the bits of augend and addend are fed into the adder circuits simultaneously and the additions in each position are taking place at the same time, this circuit is known as parallel adder.

Let the 4-bit words to be added be represented by,
 $A_3A_2A_1A_0 = 1111$ and $B_3B_2B_1B_0 = 0011$.

Significant place	4	3	2	1	
Input carry	1	1	1	0	
Augend word A :	1	1	1	1	
Addend word B :	0	0	1	1	

	1	0	0	1	0 ← Sum
	↑				
	Output Carry				

The bits are added with full adders, starting from the least significant position, to form the sum bit and carry bit. The input carry C_0 in the least significant position must be 0. The carry output of the lower order stage is connected to the carry input of the next higher order stage. Hence this type of adder is called ripple-carry adder.

In the least significant stage, A_0 , B_0 and C_0 (which is 0) are added resulting in sum S_0 and carry C_1 . This carry C_1 becomes the carry input to the second stage. Similarly in the second stage, A_1 , B_1 and C_1 are added resulting in sum S_1 and carry C_2 , in the third stage, A_2 , B_2 and C_2 are added resulting in sum S_2 and carry C_3 , in the fourth stage, A_3 , B_3 and C_3 are added resulting in sum S_3 and C_4 , which is the output carry. Thus the circuit results in a sum ($S_3S_2S_1S_0$) and a carry output (C_{out}).

Though the parallel binary adder is said to generate its output immediately after the inputs are applied, its speed of operation is limited by the carry propagation delay


through all stages. However, there are several methods to reduce this delay.

One of the methods of speeding up this process is look-ahead carry addition which eliminates the ripple-carry delay.

Carry Propagation–Look-Ahead Carry Generator:


In Parallel adder, all the bits of the augend and the addend are available for computation at the same time. The carry output of each full-adder stage is connected to the carry input of the next high-order stage. Since each bit of the sum output depends on the value of the input carry, time delay occurs in the addition process. This time delay is called as **carry propagation delay**.

For example, addition of two numbers (0011+ 0101) gives the result as 1000. Addition of the LSB position produces a carry into the second position. This carry when added to the bits of the second position, produces a carry into the third position. This carry when added to bits of the third position, produces a carry into the last position. The sum bit generated in the last position (MSB) depends on the carry that was generated by the addition in the previous position. i.e., the adder will not produce correct result until LSB carry has propagated through the intermediate full-adders. This represents a time delay that depends on the propagation delay produced in an each full-adder. For example, if each full adder is considered to have a propagation delay of 30nsec, then S_3 will not react its correct value until 90 nsec after LSB is generated. Therefore total time required to perform addition is $90+ 30 = 120\text{nsec}$.

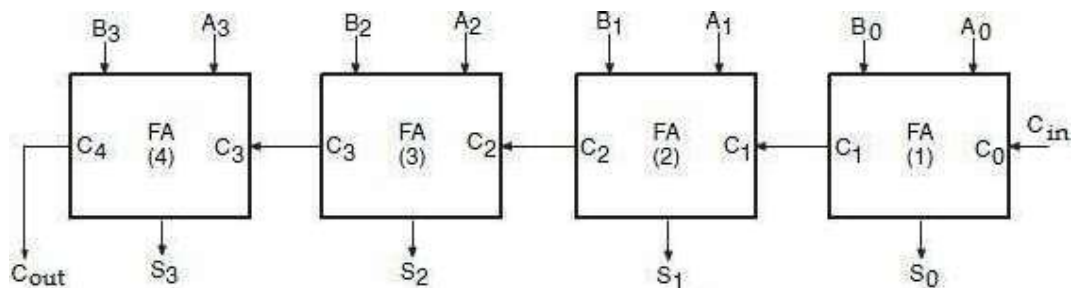

4-bit Parallel Adder

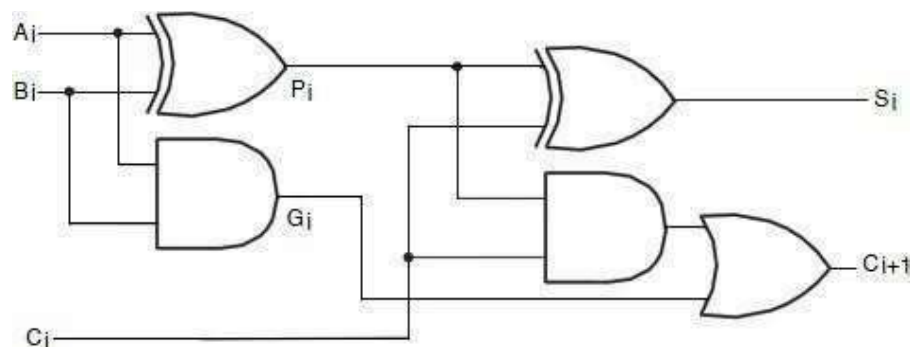The method of speeding up this process by eliminating inter stage carry delay is called **look ahead-carry addition**. This method utilizes logic gates to look at the lower order bits of the augend and addend to see if a higher-order carry is to be generated. It uses two functions: carry generate and carry propagate.



Full-Adder circuit

Consider the circuit of the full-adder shown above. Here we define two functions: carry generate (G_i) and carry propagate (P_i) as,

$$\text{Carry generate, } \mathbf{G_i = A_i \uparrow B_i}$$

$$\text{Carry propagate, } \mathbf{P_i = A_i \uparrow B_i}$$

the output sum and carry can be expressed as,

$$\mathbf{S_i = P_i \uparrow C_i}$$

$$\mathbf{C_{i+1} = G_i \uparrow P_i C_i}$$

G_i (carry generate), it produces a carry 1 when both A_i and B_i are 1, regardless of the input carry C_i .

P_i (carry propagate) because it is the term associated with the propagation of the carry from C_i to C_{i+1} .


The Boolean functions for the carry outputs of each stage and substitute for each C_i its value from the previous equation:

$$C_0 = \text{input carry } C_1 =$$

$$G_0 + P_0 C_0$$

$$\begin{aligned} C_2 = G_1 + P_1 C_1 &= G_1 + P_1 (G_0 + P_0 C_0) \\ &= G_1 + P_1 G_0 + P_1 P_0 C_0 \end{aligned}$$

 
$$\begin{aligned} C_3 = G_2 + P_2 C_2 &= G_2 + P_2 (G_1 + P_1 G_0 + P_1 P_0 C_0) \\ &= G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0 \end{aligned}$$



Since the Boolean function for each output carry is expressed in sum of products, each function can be implemented with one level of AND gates followed by an OR gate. The three Boolean functions for C_1 , C_2 and C_3 are implemented in the carry look-ahead generator as shown below. Note that C_3 does not have to wait for C_2 and C_1 to propagate; in fact C_3 is propagated at the same time as C_1 and C_2 .

Logic diagram of Carry Look-ahead Generator

Using a Look-ahead Generator we can easily construct a 4-bit parallel adder with a Look-ahead carry scheme. Each sum output requires two exclusive-OR gates. The output of the first exclusive-OR gate generates the P_i variable, and the AND gate generates the G_i variable. The carries are propagated through the carry look-ahead generator and applied as inputs to the second exclusive-OR gate. All output carries are generated after a delay through two levels of gates. Thus, outputs S_1 through S_3 have equal propagation delay times.

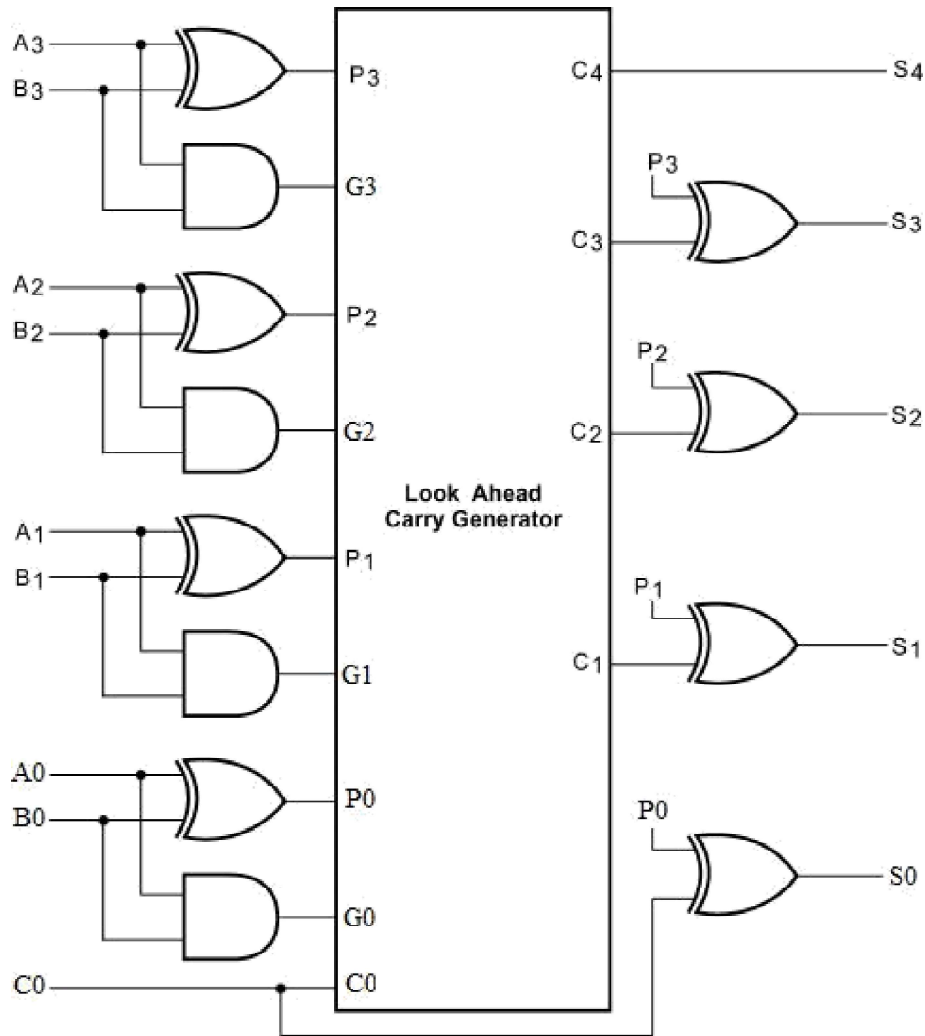


4-Bit Adder with Carry Look-ahead

Binary Subtractor (Parallel Subtractor):

The subtraction of unsigned binary numbers can be done most conveniently by means of complements. The subtraction $A-B$ can be done by taking the 2's complement of B and adding it to A . The 2's complement can be obtained by taking the 1's complement and adding 1 to the least significant pair of bits. The 1's complement can be implemented with inverters and a 1 can be added to the sum through the input carry.

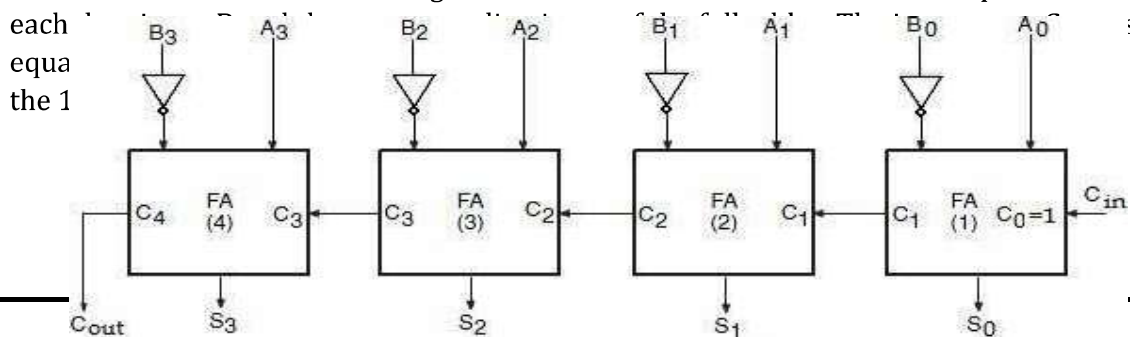
The circuit for subtracting $A-B$ consists of an adder with inverters placed between each bit of B and the carry-in. The carry-in is set to 1. The sum bits S_i and carry-out C_{out} are the result of the addition.



4-bit Parallel Subtractor

Parallel Adder/ Subtractor:

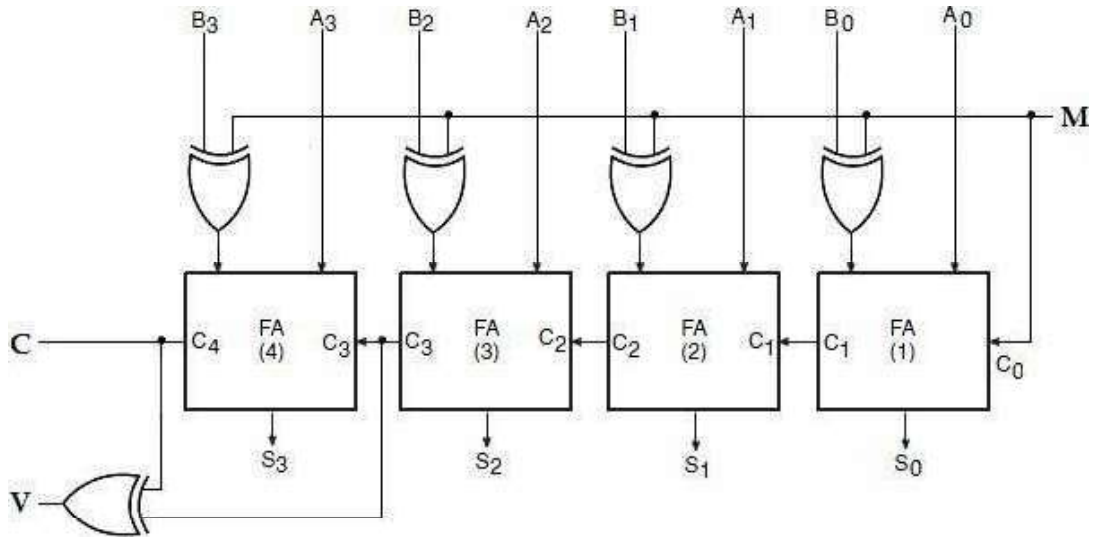The addition and subtraction operation can be combined into one circuit with one common binary adder. This is done by including an exclusive-OR gate with each full adder. A 4-bit adder Subtractor circuit is shown below.



4-Bit Adder Subtractor

The mode input M controls the operation. When $M=0$, the circuit is an adder and when $M=1$, the circuit becomes a Subtractor. Each exclusive-OR gate receives input M and one of the inputs of B . When $M=0$, we have $B_0 = B$. The full adders receive the value of B , the input carry is 0, and the circuit performs A plus B . When $M=1$, we have $B_1 = B'$ and $C_0 = 1$. The B inputs are all complemented and a 1 is added through the input carry. The circuit performs the operation A plus the 2's complement of B . The exclusive-OR with output V is for detecting an overflow.

Decimal Adder (BCD Adder):

The digital system handles the decimal number in the form of binary coded decimal numbers (BCD). A BCD adder is a circuit that adds two BCD bits and produces a sum digit also in BCD.

Consider the arithmetic addition of two decimal digits in BCD, together with an input carry from a previous stage. Since each input digit does not exceed 9, the output sum cannot be greater than $9 + 9 + 1 = 19$; the 1 is the sum being an input carry. The adder will form the sum in binary and produce a result that ranges from 0 through 19.

These binary numbers are labeled by symbols K, Z_8, Z_4, Z_2, Z_1, K is the carry. The columns under the binary sum list the binary values that appear in the outputs of the 4-bit binary adder. The output sum of the two decimal digits must be represented in BCD.

Binary Sum					BCD Sum					Decimal
K	Z ₈	Z ₄	Z ₂	Z ₁	C	S ₈	S ₄	S ₂	S ₁	
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	2
0	0	0	1	1	0	0	0	1	1	3
0	0	1	0	0	0	0	1	0	0	4
0	0	1	0	1	0	0	1	0	1	5
0	0	1	1	0	0	0	1	1	0	6
0	0	1	1	1	0	0	1	1	1	7
0	1	0	0	0	0	1	0	0	0	8
0	1	0	0	1	0	1	0	0	1	9
	1	0	1	0	1	0	0	0	0	10
0	1	0	1	1	1	0	0	0	1	11
0	1	1	0	0	1	0	0	1	0	12
0	1	1	0	1	1	0	0	1	1	13
0	1	1	1	0	1	0	1	0	0	14
0	1	1	1	1	1	0	1	0	1	15
1	0	0	0	0	1	0	1	1	0	16
1	0	0	0	1	1	0	1	1	1	17
1	0	0	1	0	1	1	0	0	0	18
1	0	0	1	1	1	1	0	0	1	19

In examining the contents of the table, it is apparent that when the binary sum is equal to or less than 1001, the corresponding BCD number is identical, and therefore no conversion is needed. When the binary sum is greater than 9 (1001), we obtain a non-valid BCD representation. The addition of binary 6 (0110) to the binary sum converts it to the correct BCD representation and also produces an output carry as required.

Inputs				Output
S ₃	S ₂	S ₁	S ₀	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

		S ₁	S ₀		
S ₃	S ₂				
		00	01	11	10
00	0	0	0	0	0
01	0	0	0	0	0
11	1	1	1	1	1
10	0	0	1	1	1


$$Y = S_3S_2 + S_3S_1$$

→ simplifying

To implement BCD adder we require:

- x 4-bit binary adder for initial addition
- x Logic circuit to detect sum greater than 9 and
- x One more 4-bit adder to add 0110_2 in the sum if the sum is greater than 9 or carry is 1.

The two decimal digits, together with the input carry, are first added in the top 4-bit binary adder to provide the binary sum. When the output carry is equal to zero, nothing is added to the binary sum. When it is equal to one, binary 0110 is added to the binary sum through the bottom 4-bit adder. The output carry generated from the bottom adder can be ignored, since it supplies information already available at the output carry terminal. The output carry from one stage must be connected to the input carry of the next higher-order stage.

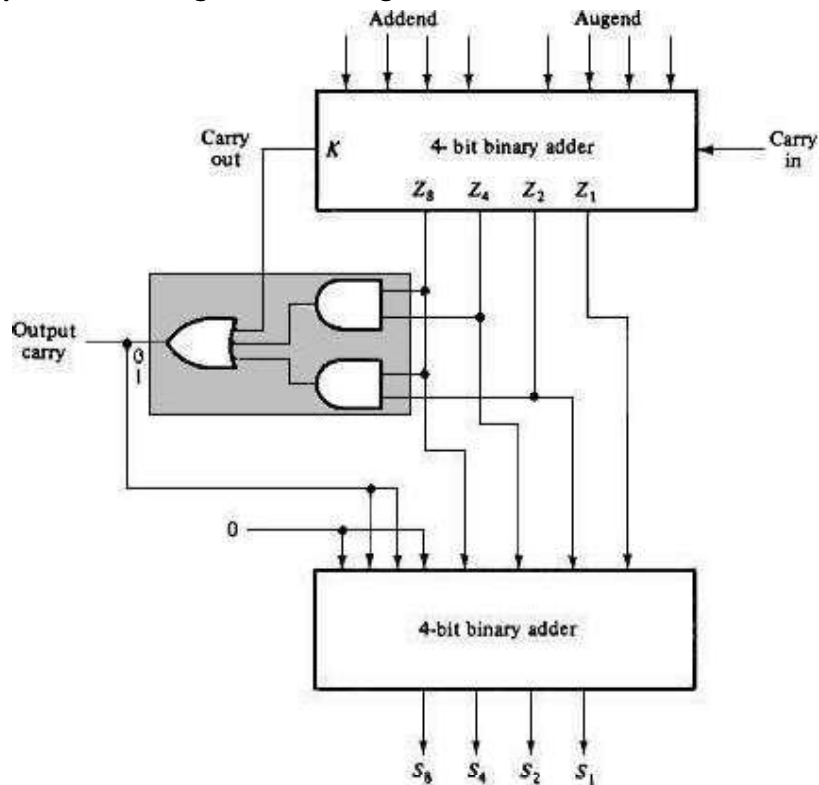

Block diagram of BCD adder

MAGNITUDE COMPARATOR:

A *magnitude comparator* is a combinational circuit that compares two given numbers (A and B) and determines whether one is equal to, less than or greater than the other. The output is in the form of three binary variables representing the conditions $A = B$, $A > B$ and $A < B$, if A and B are the two numbers being compared.



Block diagram of magnitude comparator

2-bit Magnitude Comparator:

The truth table of 2-bit comparator is given in table below—

Truth table:

Inputs				Outputs		
A ₃	A ₂	A ₁	A ₀	A>B	A=B	A<B
0	0	0	0	0	1	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	1	0	0
0	1	0	1	0	1	0
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	1	0
1	0	1	1	0	0	1
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	0	1	0

K-map Simplification:

		For A>B			
		B ₁ B ₀	00	01	11
A ₁ A ₀	00	0	0	0	0
	01	1	0	0	0
	11	1	1	0	1
	10	1	1	0	0

		For A=B			
		B ₁ B ₀	00	01	11
A ₁ A ₀	00	1	0	0	0
	01	0	1	0	0
	11	0	0	1	0
	10	0	0	0	1

$$A > B = A_0 B_1' B_0' + A_1 B_1' + A_1 A_0 B_0'$$

$$A = B = A_1' A_0' B_1' B_0' + A_1' A_0 B_1' B_0 + A_1 A_0 B_1 B_0 + A_1 A_0' B_1 B_0'$$


$$= A_1' B_1' (A_0' B_0' + A_0 B_0) + A_1 B_1 (A_0 B_0 + A_0' B_0')$$

$$= (A_0 \odot B_0) (A_1 \odot B_1)$$


		For A<B			
		B ₁ B ₀	00	01	11
A ₁ A ₀	00	0	1	1	1
	01	0	0	1	1
	11	0	0	0	0
	10	0	0	1	0

$$A < B = A_1' A_0' B_0 + A_0' B_1 B_0 + A_1' B_1$$

Logic Diagram:

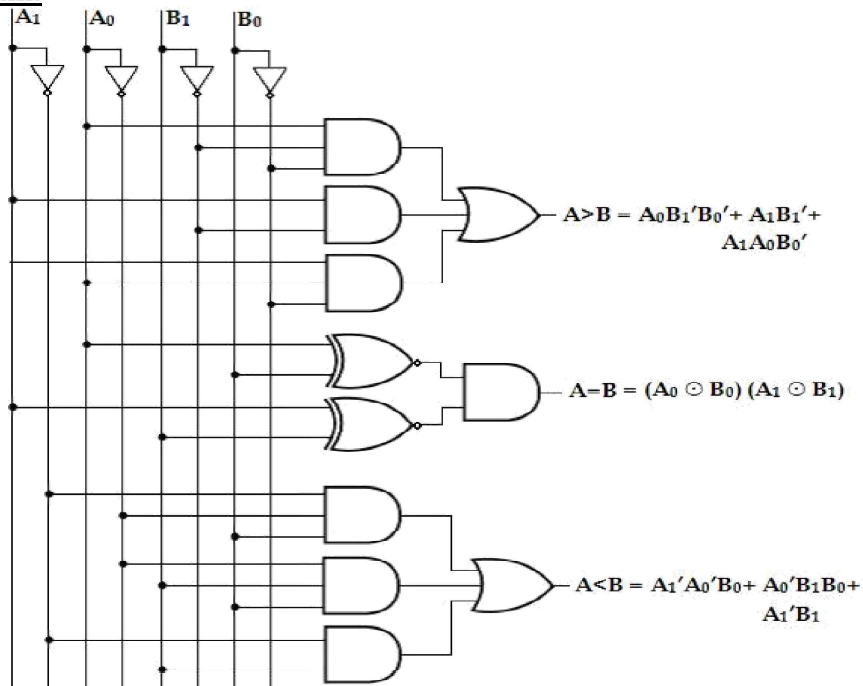

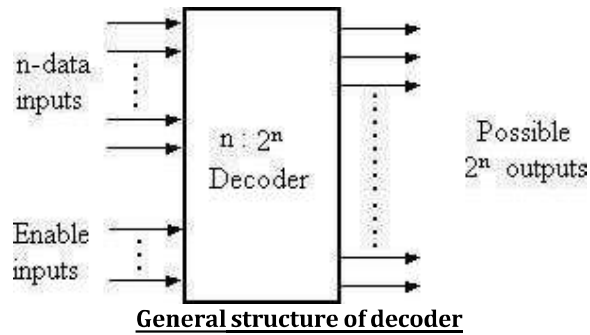
A decoder is a combinational circuit that converts binary information from n input lines to a maximum of 2^n unique output lines. The general structure of decoder circuit is –




The encoded information is presented as n inputs producing 2^n possible outputs. The 2^n output values are from 0 through 2^n-1 . A decoder is provided with enable inputs to activate decoded output based on data inputs. When any one enable input is unasserted, all outputs of decoder are disabled.

Binary Decoder (2 to 4 decoder):

 A binary decoder has n bit binary input and a one activated output out of 2^n outputs. A binary decoder is used when it is necessary to activate exactly one of 2^n outputs based on an n -bit input value.



 

3-to-8 line decoder


Applications of decoders:

1. Decoders are used in counter system.
2. They are used in analog to digital converter.
3. Decoder outputs can be used to drive a display system.

ENCODERS:

An encoder is a digital circuit that performs the inverse operation of a decoder. Hence, the opposite of the decoding process is called encoding. An encoder is a combinational circuit that converts binary information of 2^n unique input lines into n unique output lines.

 The general structure of an encoder is shown below:



General structure of Encoder

It has 2^n input lines, only one which is active at any time and n output lines. It encodes one of the active inputs to a coded binary output with n bits. In an encoder, the number of outputs is less than the number of inputs.

Octal-to-Binary Encoder:

It has eight inputs (one for each of the octal digits) and the three outputs that generate the corresponding binary number. It is assumed that only one input has a value of 1 at any given time.



D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇	A	B	C
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

The encoder can be implemented with OR gates whose inputs are determined directly from the truth table. Output z is equal to 1, when the input octal digit is 1 or 3 or 5 or 7. Output y is 1 for octal digits 2, 3, 6, or 7 and the output is 1 for digits 4, 5, 6 or


8. These conditions can be expressed by the following output Boolean functions: $z = D_1 + D_3 + D_5 + D_7$

$$y = D_2 + D_3 + D_6 + D_7$$

$$x = D_4 + D_5 + D_6 + D_7$$

The encoder can be implemented with three OR gates. The encoder defined in the below table, has the limitation that only one input can be active at any given time. If two inputs are active simultaneously, the output produces an undefined combination.

For eg., if D₃ and D₆ are 1 simultaneously, the output of the encoder may be 111. This does not represent either D₆ or D₃. To resolve this problem, encoder circuits must establish an input priority to ensure that only one input is encoded. If we establish a higher priority for inputs with higher subscript numbers and if D₃ and D₆ are 1 at the same time, the output will be 110 because D₆ has higher priority than D₃.

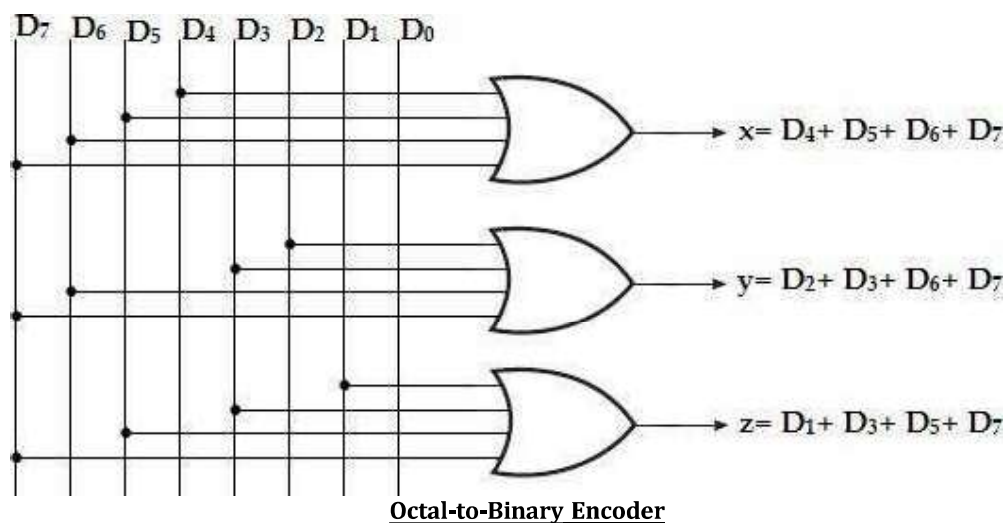


Another problem in the octal-to-binary encoder is that an output with all 0's is generated when all the inputs are 0; this output is same as when D₀ is equal to 1. The discrepancy can be resolved by providing one more output to indicate that atleast one input is equal to 1.

MULTIPLEXER: (Data Selector)

A **multiplexer** or **MUX**, is a combinational circuit with more than one input line, one output line and more than one selection line. A multiplexer selects binary information present from one of many input lines, depending upon the logic status of the selection inputs, and routes it to the output line. Normally, there are 2_n input lines and n selection lines whose bit combinations determine which input is selected. The multiplexer is often labeled as MUX in

block diagrams.

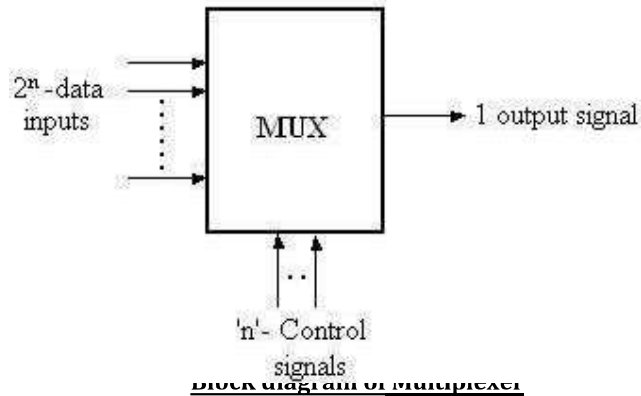
A multiplexer is also called a **data selector**, since it selects one of many inputs and steers the binary information to the output line.



4-to-1-line Multiplexer:

A 4-to-1-line multiplexer has four (2_n) input lines, two (n) select lines and one output line. It is the multiplexer consisting of four input channels and information of one of the channels can be selected and transmitted to an output line according to the select inputs combinations. Selection of one of the four input channel is possible by two selection inputs.

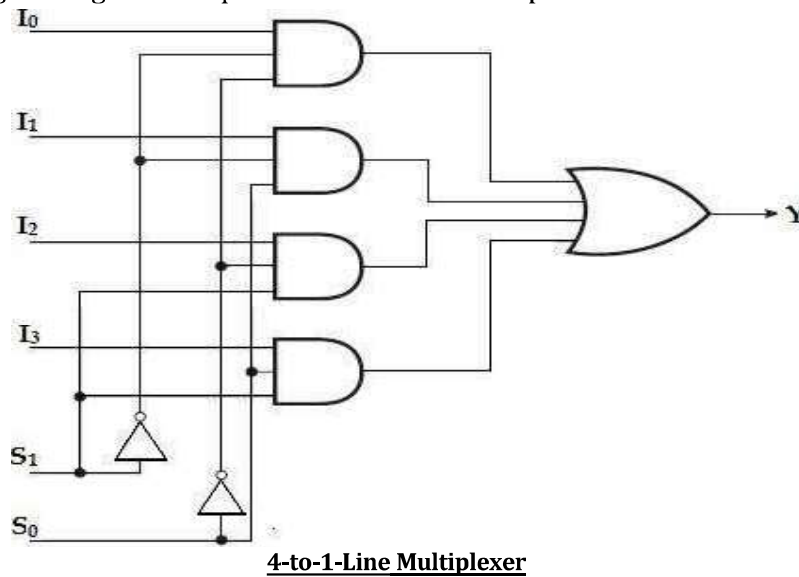Each of the four inputs I_0 through I_3 , is applied to one input of AND gate. Selection lines S_1 and S_0 are decoded to select a particular AND gate. The outputs of the AND gate are applied to a single OR gate that provides the 1-line output.



Function table:

S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

To demonstrate the circuit operation, consider the case when $S_1S_0 = 10$. The AND gate associated with input I_2 has two of its inputs equal to 1 and the third input connected to I_2 . The other three AND gates have atleast one input equal to 0, which makes their outputs equal to 0. The OR output is now equal to the value of I_2 , providing a path from the selected

input to the output.

The data output is equal to I_0 only if $S_1= 0$ and $S_0= 0$; $Y= I_0S_1'S_0'$. The data output is equal to I_1 only if $S_1= 0$ and $S_0= 1$; $Y= I_1S_1'S_0$. The data output is equal to I_2 only if $S_1= 1$ and $S_0= 0$; $Y= I_2S_1S_0'$. The data output is equal to I_3 only if $S_1= 1$ and $S_0= 1$; $Y= I_3S_1S_0$.

When these terms are ORed, the total expression for the data output is,


$$Y= I_0S_1'S_0' + I_1S_1'S_0 + I_2S_1S_0' + I_3S_1S_0.$$

As in decoder, multiplexers may have an enable input to control the operation of the unit. When the enable input is in the inactive state, the outputs are disabled, and when it is in the active state, the circuit functions as a normal multiplexer.

DEMULTIPLEXER:

Demultiplex means one into many. Demultiplexing is the process of taking information from one input and transmitting the same over one of several outputs.

 A demultiplexer is a combinational logic circuit that receives information on a single input and transmits the same information over one of several (2^n) output lines.




Block diagram of demultiplexer

The block diagram of a demultiplexer which is opposite to a multiplexer in its operation is shown above. The circuit has one input signal, n' select signals and 2_n output signals. The select inputs determine to which output the data input will be connected. As the serial data is changed to parallel data, i.e., the input caused to appear on one of the n output lines, the demultiplexer is also called a **—data distributor** or a **—serial-to-parallel converter** .

1-to-4 Demultiplexer:

 A 1-to-4 demultiplexer has a single input, D_{in} , four outputs (Y_0 to Y_3) and two select inputs (S_1 and S_0).



The input variable D_{in} has a path to all four outputs, but the input information is directed to only one of the output lines. The truth table of the 1-to-4 demultiplexer is shown below.

Enable	S_1	S_0	D_{in}	Y_0	Y_1	Y_2	Y_3
0	x	x	x	0	0	0	0

1	0	0	0	0	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	0	0	0	0
1	0	1	1	0	1	0	0
1	1	0	0	0	0	0	0
1	1	0	1	0	0	1	0
1	1	1	0	0	0	0	0
1	1	1	1	0	0	0	1

Truth table of 1-to-4 demultiplexer


From the truth table, it is clear that the data input, D_{in} is connected to the output Y_0 , when $S_1=0$ and $S_0=0$ and the data input is connected to output Y_1 when $S_1=0$ and $S_0=1$. Similarly, the data input is connected to output Y_2 and Y_3 when $S_1=1$ and $S_0=0$ and when $S_1=1$ and $S_0=1$, respectively. Also, from the truth table, the expression for outputs can be written as follows,

$$Y_0 = S_1'S_0'D_{in}$$

$$Y_1 = S_1'S_0D_{in}$$

$$Y_2 = S_1S_0'D_{in}$$

$$Y_3 = S_1S_0D_{in}$$

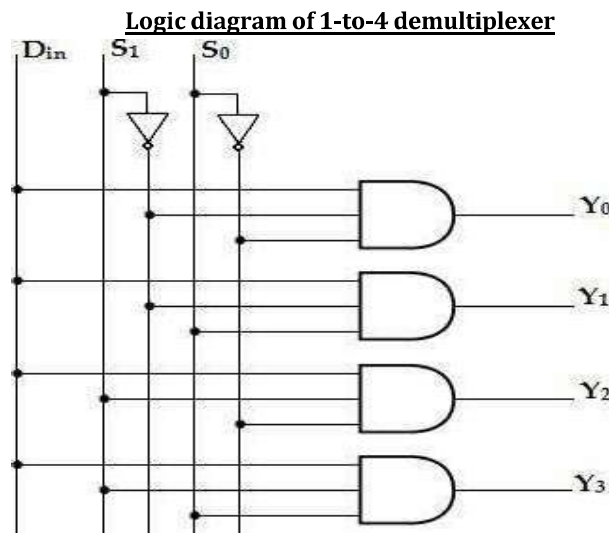


Now, using the above expressions, a 1-to-4 demultiplexer can be implemented using four 3-input AND gates and two NOT gates. Here, the input data line D_{in} , is connected to all the AND gates. The two select lines S_1, S_0 enable only one gate at a time and the data that appears on the input line passes through the selected gate to the associated output line.

UNIT II SYNCHRONOUS SEQUENTIAL LOGIC

 
2.1 INTRODUCTION

In **combinational logic circuits**, the outputs at any instant of time depend only on the input signals present at that time. For a change in input, the output occurs immediately.



In **sequential logic circuits**, it consists of combinational circuits to which storage elements are connected to form a feedback path. The storage elements are devices capable of storing binary information either 1 or 0.

 The information stored in the memory elements at any given time defines the present state of the sequential circuit. The present state and the external circuit determine the output and the next state of sequential circuits.



Thus in sequential circuits, the output variables depend not only on the present input variables but also on the past history of input variables.


The rotary channel selected knob on an old-fashioned TV is like a combinational. Its output selects a channel based only on its current input – the position of the knob. The channel-up and channel-down push buttons on a TV is like a sequential circuit. The channel selection depends on the past sequence of up/down pushes.

The comparison between combinational and sequential circuits is given in table below.

S.No	Combinational logic	Sequential logic
1	The output variable, at all times depends on the combination of input variables.	The output variable depends not only on the present input but also depend upon the past history of inputs.
2	Memory unit is not required	Memory unit is required to store the past history of input variables.
3	Faster in speed	Slower than combinational circuits.

4	Easy to design	Comparatively harder to design.
5	Eg. Parallel adder	Eg. Serial adder

2.2 Classification of Logic Circuits

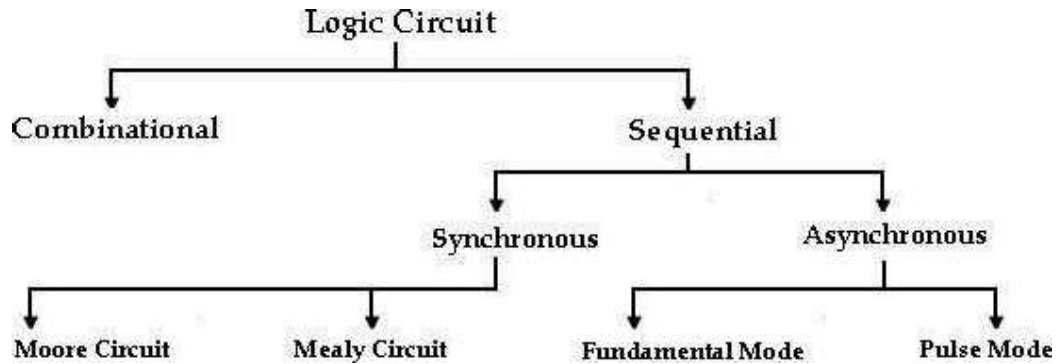

The sequential circuits can be classified depending on the timing of their signals:

- ✓ Synchronous sequential circuits
- ✓ Asynchronous sequential circuits.

In synchronous sequential circuits, signals can affect the memory elements only at discrete instants of time. In asynchronous sequential circuits change in input signals can affect memory element at any instant of time. The memory elements used in both circuits are Flip-Flops, which are capable of storing 1-bit information.


S.No	Synchronous sequential circuits	Asynchronous sequential circuits
1	Memory elements are clocked Flip-Flops	Memory elements are either unclocked Flip-Flops or time delay elements.
2	The change in input signals can affect memory element upon activation of clock signal.	The change in input signals can affect memory element at any instant of time.
3	The maximum operating speed of clock depends on time delays involved.	Because of the absence of clock, it can operate faster than synchronous circuits.
4	Easier to design	More difficult to design

2.3 TRIGGERING OF FLIP-FLOPS

The state of a Flip-Flop is switched by a momentary change in the input signal. This momentary change is called a trigger and the transition it causes is said to trigger the Flip-Flop. Clocked Flip-Flops are triggered by pulses. A clock pulse starts from an initial value of 0, goes momentarily to 1 and after a short time, returns to its initial 0 value.

Latches are controlled by enable signal, and they are level triggered, either positive level triggered or negative level triggered. The output is free to change according to the S and R input values, when active level is maintained at the enable input.

 Flip-Flops are different from latches. Flip-Flops are pulse or clock edge triggered instead of level triggered.



2.4 EDGE TRIGGERED FLIP-FLOPS


Flip-Flops are synchronous bistable devices (has two outputs Q and Q'). In this case, the term synchronous means that the output changes state only at a specified point on the triggering input called the clock (CLK), i.e., changes in the output occur in synchronization with the clock.

An *edge-triggered Flip-Flop* changes state either at the positive edge (rising edge) or at the negative edge (falling edge) of the clock pulse and is sensitive to its inputs only at this transition of the clock. The different types of edge-triggered Flip-Flops are—S-R Flip-Flop, J-K Flip-Flop, D Flip-Flop, T Flip-Flop.

Although the S-R Flip-Flop is not available in IC form, it is the basis for the D and J-K Flip-Flops. Each type can be either positive edge-triggered (no bubble at C input) or negative edge-triggered (bubble at C input). The key to identifying an edge-triggered Flip-Flop by its logic symbol is the small triangle inside the block at the clock (C) input. This triangle is called the **dynamic input indicator**.

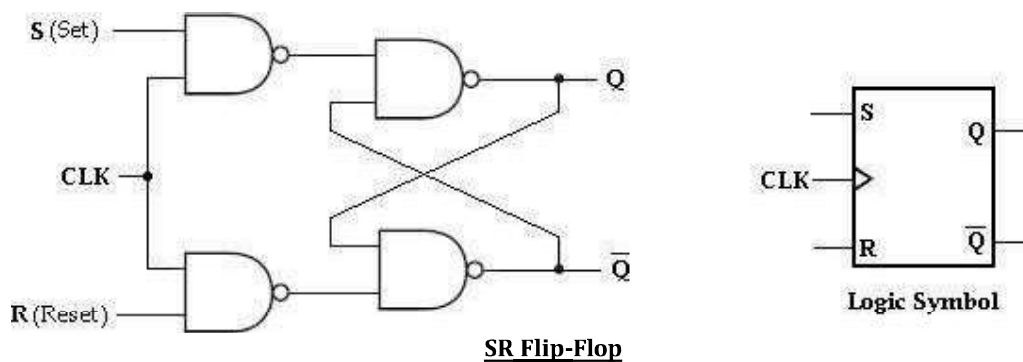2.4.1 S-R Flip-Flop

The S and R inputs of the S-R Flip-Flop are called *synchronous* inputs because data on these inputs are transferred to the Flip-Flop's output only on the triggering edge of the clock pulse. The circuit is similar to SR latch except enable signal is replaced by clock pulse (CLK). On the positive edge of the clock pulse, the circuit responds to the S and R inputs.




When S is HIGH and R is LOW, the Q output goes HIGH on the triggering edge of the clock pulse, and the Flip-Flop is SET. When S is LOW and R is HIGH, the Q output goes LOW on the triggering edge of the clock pulse, and the Flip-Flop is RESET. When both S and R are LOW, the output does not change from its prior state. An invalid

condition exists when both S and R are HIGH.

CLK	S	R	Q_n	Q_{n+1}	State
1	0	0	0	0	No Change (NC)
1	0	0	1	1	
1	0	1	0	0	Reset
1	0	1	1	0	
1	1	0	0	1	Set
1	1	0	1	1	
1	1	1	0	x	Indeterminate *
1	1	1	1	x	
0	x	x	0	0	No Change (NC)
0	x	x	1	1	


Truth table for SR Flip-Flop

 

Input and output waveforms of SR Flip-Flop

 2.4.2 J-K Flip-Flop:


JK means Jack Kilby, Texas Instrument (TI) Engineer, who invented IC in 1958. JK Flip-Flop has two inputs J(set) and K(reset). A JK Flip-Flop can be obtained from the clocked SR Flip-Flop by augmenting two AND gates as shown below.




JK Flip Flop

The data input J and the output Q' are applied to the first AND gate and its output (JQ') is applied to the S input of SR Flip-Flop. Similarly, the data input K and

 the output Q are applied to the second AND gate and its output (KQ) is applied to the R input of SR Flip-Flop.



(a) Using SR flipflop

 

(b) Graphic symbol

J= K= 0

When J=K= 0, both AND gates are disabled. Therefore clock pulse have no effect, hence the Flip-Flop output is same as the previous output.

J= 0, K= 1

When J= 0 and K= 1, AND gate 1 is disabled i.e., S= 0 and R= 1. This condition will reset the Flip-Flop to 0.


J= 1, K= 0

When J= 1 and K= 0, AND gate 2 is disabled i.e., S= 1 and R= 0. Therefore the Flip-Flop will set on the application of a clock pulse.

J= K= 0

When J=K= 1, it is possible to set or reset the Flip-Flop. If Q is High, AND gate 2 passes on a reset pulse to the next clock. When Q is low, AND gate 1 passes on a set pulse to the next clock. Eitherway, Q changes to the complement of the last state i.e., toggle. Toggle means to switch to the opposite state. The truth table of JK Flip-Flop is given below.

CLK	Inputs		Output	State
	J	K	Q_{n+1}	
1	0	0	Q_n	No Change
1	0	1	0	Reset
1	1	0	1	Set
1	1	1	Q_n'	Toggle

 

Input and output waveforms of JK Flip-Flop

Characteristic table and Characteristic equation:

The characteristic table for JK Flip-Flop is shown in the table below. From the table, K-map for the next state transition (Q_{n+1}) can be drawn and the simplified logic expression which represents the characteristic equation of JK Flip-Flop can be found.

Q_n	J	K	Q_{n+1}
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Characteristic table


K-map Simplification:

		JK			
Q_n		00	01	11	10
0		0	0	1	1
1		1	0	0	1

Characteristic equation: $Q_{n+1} = JQ' + K'Q$.

 
2.4.3 D Flip-Flop:

Like in D latch, in D Flip-Flop the basic SR Flip-Flop is used with complemented inputs. The D Flip-Flop is similar to D-latch except clock pulse is used instead of enable input.




D Flip-Flop

 To eliminate the undesirable condition of the indeterminate state in the RS Flip-Flop is to ensure that inputs S and R are never equal to 1 at the same time. This is done by D Flip-Flop. The D (*delay*) Flip-Flop has one input called delay input and clock pulse input. The D Flip-Flop using SR Flip-Flop is shown below.



(a) Using SR flipflop

 


(b) Graphic symbol

The truth table of D Flip-Flop is given below.

Clock	D	Q_{n+1}	State
1	0	0	Reset
1	1	1	Set
0	x	Q_n	No Change

Truth table for D Flip-Flop

 

Input and output waveforms of clocked D Flip-Flop

Looking at the truth table for D Flip-Flop we can realize that Q_{n+1} function follows the D input at the positive going edges of the clock pulses.

Characteristic table and Characteristic equation:


The characteristic table for D Flip-Flop shows that the next state of the Flip-Flop is independent of the present state since Q_{n+1} is equal to D. This means that an input pulse will transfer the value of input D into the output of the Flip-Flop independent of the value of the output before the pulse was applied.

The characteristic equation is derived from K-map.

Q_n	D	Q_{n+1}
0	0	0
0	1	1
1	0	0
1	1	1

Characteristic table


K-map simplification

 

Characteristic equation: $Q_{n+1} = D$.

 
2.4.4 T Flip-Flop

The T (*Toggle*) Flip-Flop is a modification of the JK Flip-Flop. It is obtained from JK Flip-Flop by connecting both inputs J and K together, i.e., single input. Regardless of the present state, the Flip-Flop complements its output when the clock pulse occurs while input T= 1.




When $T = 0$, $Q_{n+1} = Q_n$, i.e., the next state is the same as the present state and no change occurs.

 When $T = 1$, $Q_{n+1} = Q_n'$, i.e., the next state is the complement of the present state.



(a) Using JK flipflop

 

(b) Graphic symbol

The truth table of T Flip-Flop is given below.

T	Q_n	Q_{n+1} State
0	Q_n	No Change
1	Q_n'	Toggle

Characteristic table and Characteristic equation:

The characteristic table for T Flip-Flop is shown below and characteristic equation is derived using K-map.

Q_n	T	Q_{n+1}
0	0	0
0	1	1
1	0	1
1	1	0


K-map Simplification:

$Q_n \backslash T$	0	1
0	0	1
1	1	0

Characteristic equation: $Q_{n+1} = TQ_n' + T'Q_n$.

 2.4.5 Master-Slave JK Flip-Flop


A master-slave Flip-Flop is constructed using two separate JK Flip-Flops. The first Flip-Flop is called the master. It is driven by the positive edge of the clock pulse. The second Flip-Flop is called the slave. It is driven by the negative edge of the clock pulse. The logic diagram of a master-slave JK Flip-Flop is shown below.



When the clock pulse has a positive edge, the master acts according to its J-K inputs, but the slave does not respond, since it requires a negative edge at the clock input.

When the clock input has a negative edge, the slave Flip-Flop copies the master outputs. But the master does not respond since it requires a positive edge at its clock input.

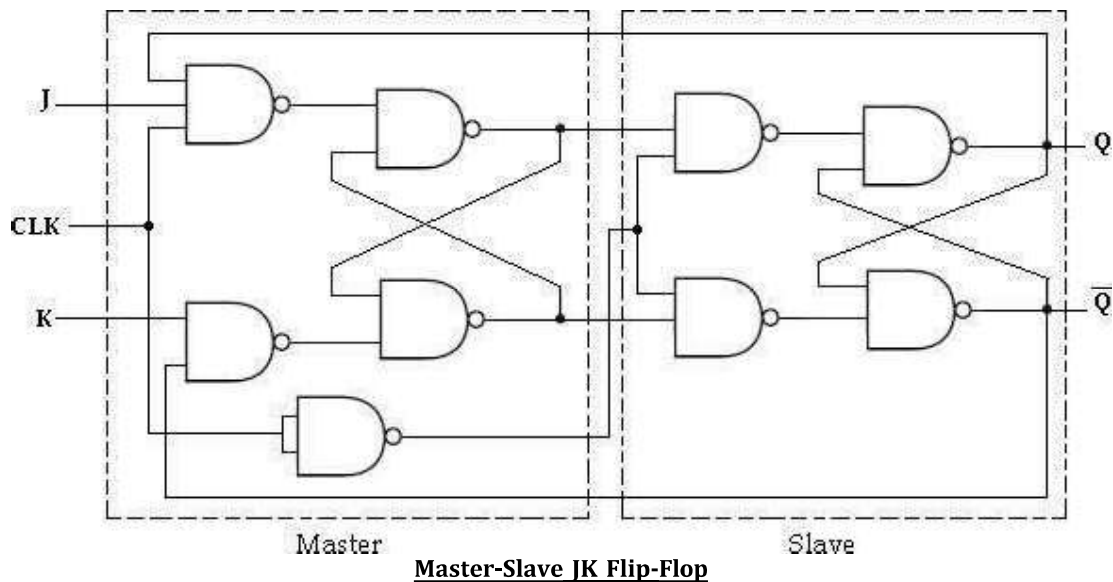The clocked master-slave J-K Flip-Flop using NAND gates is shown below.



2.5 APPLICATION TABLE (OR) EXCITATION TABLE:

The *characteristic table* is useful for **analysis** and for defining the operation of the Flip-Flop. It specifies the next state (Q_{n+1}) when the inputs and present state are known.

The *excitation or application table* is useful for **design** process. It is used to find the Flip-Flop input conditions that will cause the required transition, when the present state (Q_n) and the next state (Q_{n+1}) are known.

2.5.1 SR Flip-Flop:

Present State	Inputs		Next State
	S	R	
Q_n			Q_{n+1}
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	x
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	x

Characteristic Table		Modified Table			
Present State	Next State	Inputs		Inputs	
Q_n	Q_{n+1}	S	R	S	R
0	0	0	0		
0	0	0	1	0	x
0	1	1	0	1	0
1	0	0	1	0	1
1	1	0	0	x	0
1	1	1	0		

Present State	Next State	Inputs	
Q_n	Q_{n+1}	S	R
0	0	0	x
0	1	1	0
1	0	0	1
1	1	x	0

Excitation Table

The above table presents the excitation table for SR Flip-Flop. It consists of present state (Q_n), next state (Q_{n+1}) and a column for each input to show how the required transition is achieved.

There are 4 possible transitions from present state to next state. The required Input conditions for each of the four transitions are derived from the information available in the characteristic table. The symbol 'x' denotes the don't care condition, it does not matter whether the input is 0 or 1.

2.5.2 JK Flip-Flop:

Present State	Inputs		Next State
	Q_n	Q_{n+1}	
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

Characteristic Table

Present State	Next State	Inputs		Inputs	
		J	K	J	K
0	0	0	0	0	x
0	0	0	1		
0	1	1	0	1	x
0	1	1	1		
1	0	0	1	x	1
1	0	1	1		
1	1	0	0	x	0
1	1	1	0		

Modified Table

Present State	Next State	Inputs	
		J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

Excitation Table

2.5.3 D Flip-Flop

Present State	Input	Next State
Q_n	D	Q_{n+1}
0	0	0
0	1	1
1	0	0
1	1	1

Characteristic Table

Present State	Next State	Input
Q_n	Q_{n+1}	D
0	0	0
0	1	1
1	0	0
1	1	1

Excitation Table

2.5.4 T Flip-Flop

Present State	Input	Next State
Q_n	T	Q_{n+1}
0	0	0
0	1	1
1	0	1
1	1	0

Characteristic Table

Present State	Next State	Input
Q_n	Q_{n+1}	T
0	0	0
0	1	1
1	0	1
1	1	0

Modified Table

2.6 CLASSIFICATION OF SYNCHRONOUS SEQUENTIAL CIRCUIT:


In synchronous or clocked sequential circuits, clocked Flip-Flops are used as memory elements, which change their individual states in synchronism with the periodic clock signal. Therefore, the change in states of Flip-Flop and change in state of the entire circuits occur at the transition of the clock signal.

The synchronous or clocked sequential networks are represented by two models.

- **Moore model:** The output depends only on the present state of the Flip-Flops.
- **Mealy model:** The output depends on both the present state of the Flip-Flops and on the inputs.

 
2.6.1 Moore model:

In the Moore model, the outputs are a function of the present state of the Flip-Flops only. The output depends only on present state of Flip-Flops, it appears only after the clock pulse is applied, i.e., it varies in synchronism with the clock input.



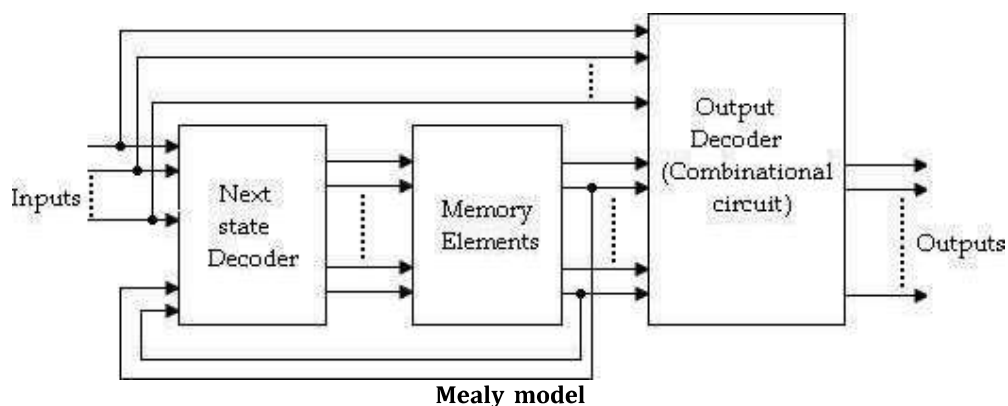2.6.2 Mealy model:

In the Mealy model, the outputs are functions of both the present state of the Flip-Flops and inputs.



2.6.3 Difference between Moore and Mealy model

Sl.No	Moore model	Mealy model
1	Its output is a function of present state only.	Its output is a function of present state as well as present input.
2	Input changes does not affect the output.	Input changes may affect the output of the circuit.
3	It requires more number of states for implementing same function.	It requires less number of states for implementing same function.

2.7 ANALYSIS OF SYNCHRONOUS SEQUENTIAL CIRCUIT:

The behavior of a sequential circuit is determined from the inputs, outputs and the state of its Flip-Flops. The outputs and the next state are both a function of the inputs and the present state. The analysis of a sequential circuit consists of obtaining a table or diagram from the time sequence of inputs, outputs and internal states.


Before going to see the analysis and design examples, we first understand the state diagram, state table.

2.7.1 State Diagram


State diagram is a pictorial representation of a behavior of a sequential circuit.

- In the state diagram, a state is represented by a circle and the transition between states is indicated by directed lines connecting the circles.
- A directed line connecting a circle with circle with itself indicates that next state is same as present state.
- The binary number inside each circle identifies the state represented by the circle.
- The directed lines are labeled with two binary numbers separated by a symbol '/'. The input value that causes the state transition is labeled first and the output value during the present state is labeled after the symbol '/'.

 In case of Moore circuit, the directed lines are labeled with only one binary number representing the state of the input that causes the state transition. The output state is indicated within the circle, below the present state because output state depends only on present state and not on the input.



State diagram for Mealy circuit

 

State diagram for Moore circuit

2.7.2 State Table

State table represents relationship between input, output and Flip-Flop states.

It consists of three sections labeled present state, next state and output.

2.7.2.1 The present state designates the state of Flip-Flops before the occurrence of a clock pulse, and the output section gives the values of the output variables during the present state.

2.7.2.2 Both the next state and output sections have two columns representing two possible input conditions: $X=0$ and $X=1$.

Present state	Next state		Output	
	X= 0	X= 1	X= 0	X= 1
AB	AB	AB	Y	Y
a	a	c	0	0
b	b	a	0	0
c	d	c	0	1
d	b	d	0	0

- In case of Moore circuit, the output section has only one column since output does not depend on input.

Present state	Next state		Output Y
	X= 0	X= 1	
AB	AB	AB	
a	a	c	0
b	b	a	0
c	d	c	1
d	b	d	0

2.9.3 State Equation

It is an algebraic expression that specifies the condition for a Flip-Flop state transition.

The Flip-Flops may be of any type and the logic diagram may or may not include combinational circuit gates.

2.9.4 ANALYSIS PROCEDURE

The synchronous sequential circuit analysis is summarized as given below:

1. Assign a state variable to each Flip-Flop in the synchronous sequential circuit.
2. Write the excitation input functions for each Flip-Flop and also write the Moore/ Mealy output equations.
3. Substitute the excitation input functions into the bistable equations for the Flip-Flops to obtain the next state output equations.
4. Obtain the state table and reduced form of the state table.
5. Draw the state diagram by using the second form of the state table.

2.9.5 Analysis of Mealy Model

1. A sequential circuit has two JK Flip-Flops A and B, one input (x) and one output

(y). the Flip-Flop input functions are,


$$J_A = B + x \quad J_B = A' + x'$$

$$K_A = 1 \quad K_B = 1$$

and the circuit output function, $Y = xA'B$.

- Draw the logic diagram of the Mealy circuit,
- Tabulate the state table,
- Draw the state diagram.

Soln:

 

State table:


To obtain the next-state values of a sequential circuit with JK Flip-Flops, use the JK Flip-Flop characteristics table.

Present state		Input	Flip-Flop Inputs				Next state		Output
A	B	x	$J_A = B + x$	$K_A = 1$	$J_B = A' + x'$	$K_B = 1$	$A(t+1)$	$B(t+1)$	$Y = xA'B$
0	0	0	0	1	1	1	0	1	0
0	0	1	1	1	1	1	1	1	0
0	1	0	1	1	1	1	1	0	0
0	1	1	1	1	1	1	1	0	1
1	0	0	0	1	1	1	0	1	0
1	0	1	1	1	0	1	0	0	0
1	1	0	1	1	1	1	0	0	0
1	1	1	1	1	0	1	0	0	0

Present state		Next state				Output	
		x= 0		x= 1		x= 0	x= 1
A	B	A	B	A	B	y	y
0	0	0	1	1	1	0	0
0	1	1	0	1	0	0	1
1	0	0	1	0	0	0	0
1	1	0	0	0	0	0	0

Second form of state table

State Diagram:

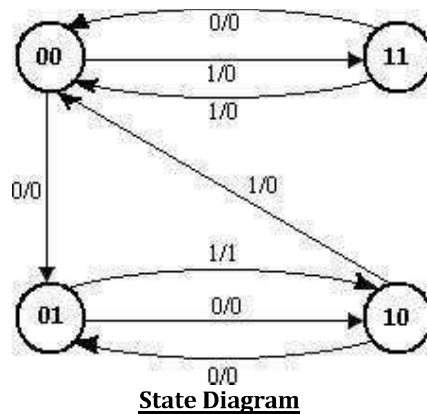

State Diagram

2. A sequential circuit with two 'D' Flip-Flops A and B, one input (x) and one output (y), the Flip-Flop input functions are:


$$D_A = Ax + Bx$$

$$D_B = A'x \text{ and the circuit output function is,}$$

$$Y = (A + B)x'$$

- Draw the logic diagram of the circuit,
- Tabulate the state table,
- Draw the state diagram.

Soln:

 


State Table:

Present state		Input	Flip-Flop Inputs		Next state		Output
A	B	x	$D_A = Ax + Bx$	$D_B = A'x$	$A(t+1)$	$B(t+1)$	$Y = (A+B)x'$
0	0	0	0	0	0	0	0
0	0	1	0	1	0	1	0
0	1	0	0	0	0	0	1
0	1	1	1	1	1	1	0
1	0	0	0	0	0	0	1
1	0	1	1	0	1	0	0
1	1	0	0	0	0	0	1
1	1	1	1	0	1	0	0

Present state		Next state				Output	
		x = 0		x = 1		x = 0	x = 1
A	B	A	B	A	B	Y	Y
0	0	0	0	0	1	0	0
0	1	0	0	1	1	1	0
1	0	0	0	1	0	1	0
1	1	0	0	1	0	1	0

Second form of state table

State Diagram:

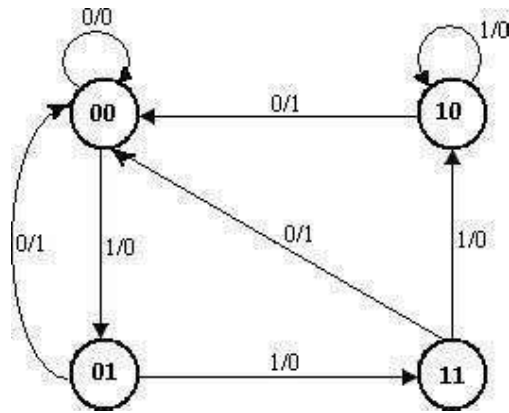


2.10 STATE REDUCTION/ MINIMIZATION

The state reduction is used to avoid the redundant states in the sequential circuits. The reduction in redundant states reduces the number of required Flip-Flops and logic gates, reducing the cost of the final circuit.

The two states are said to be redundant or equivalent, if every possible set of inputs generate exactly same output and same next state. When two states are equivalent, one of them can be removed without altering the input-output relationship.

Since 'n' Flip-Flops produced 2^n state, a reduction in the number of states may result in a reduction in the number of Flip-Flops.

 The need for state reduction or state minimization is explained with one example.



State diagram

Step 1: Determine the state table for given state diagram

Present state	Next state		Output	
	X= 0	X= 1	X= 0	X= 1
a	b	c	0	0
b	d	e	1	0
c	c	d	0	1
d	a	d	0	0
e	c	d	0	1

State table


Step 2: Find equivalent states

From the above state table **c** and **e** generate exactly same next state and same output for every possible set of inputs. The state **c** and **e** go to next states **c** and **d** and have outputs 0 and 1 for $x=0$ and $x=1$ respectively. Therefore state **e** can be removed and replaced by **c**. The final reduced state table is shown below.

Present state	Next state		Output	
	X= 0	X= 1	X= 0	X= 1
a	b	c	0	0
b	d	c	1	0
c	c	d	0	1
d	a	d	0	0

Reduced state table

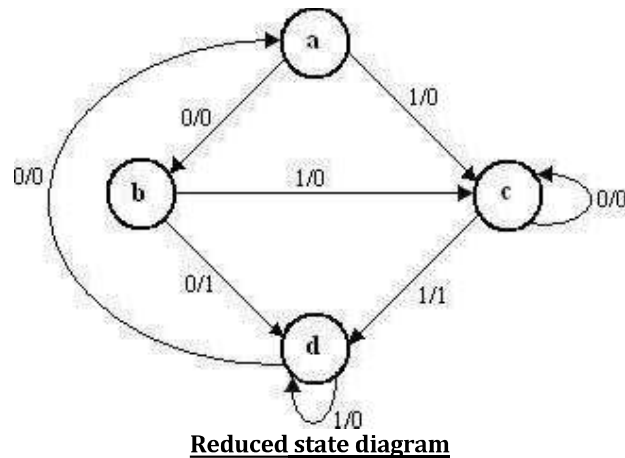The state diagram for the reduced table consists of only four states and is shown below.



1. Reduce the number of states in the following state table and tabulate the reduced state table.

Present state	Next state		Output	
	X= 0	X= 1	X= 0	X= 1
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	f	0	1
e	a	f	0	1
f	g	f	0	1
g	a	f	0	1

Soln:

From the above state table **e** and **g** generate exactly same next state and same output for every possible set of inputs. The state **e** and **g** go to next states **a** and **f** and have outputs 0 and 1 for x=0 and x=1 respectively. Therefore state **g** can be removed and replaced by **e**.

The reduced state table-1 is shown below.

Present state	Next state		Output	
	X= 0	X= 1	X= 0	X= 1
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	f	0	1
e	a	f	0	1
f	e	f	0	1

Reduced state table-1

Now states d and f are equivalent. Both states go to the same next state (e, f) and have same output (0, 1). Therefore one state can be removed; **f** is replaced by **d**. The final reduced state table-2 is shown below.

Present state	Next state		Output	
	X= 0	X= 1	X= 0	X= 1
a	a	b	0	0
b	c	d	0	0
c	a	d	0	0
d	e	d	0	1
e	a	d	0	1

Reduced state table-2

Thus 7 states are reduced into 5 states.

2. Determine a minimal state table equivalent furnished below

Present state	Next state	
	X= 0	X= 1
1	1, 0	1, 0
2	1, 1	6, 1
3	4, 0	5, 0
4	1, 1	7, 0
5	2, 0	3, 0
6	4, 0	5, 0
7	2, 0	3, 0

Soln:

Present state	Next state		Output	
	X= 0	X= 1	X= 0	X= 1
1	1	1	0	0
2	1	6	1	1
3	4	5	0	0
4	1	7	1	0
5	2	3	0	0
6	4	5	0	0
7	2	3	0	0

From the above state table, **5** and **7** generate exactly same next state and same output for every possible set of inputs. The state **5** and **7** go to next states **2** and **3** and have outputs 0 and 0 for x=0 and x=1 respectively. Therefore state **7** can be removed and replaced by **5**.

Similarly, **3** and **6** generate exactly same next state and same output for every possible set of inputs. The state **3** and **6** go to next states **4** and **5** and have outputs 0 and 0 for x=0 and x=1 respectively. Therefore state **6** can be removed and replaced by **3**.

The final reduced state table is shown below.

Present state	Next state		Output	
	X= 0	X= 1	X= 0	X= 1
1	1	1	0	0
2	1	3	1	1
3	4	5	0	0
4	1	5	1	0
5	2	3	0	0

Reduced state table

Thus 7 states are reduced into 5 states.

Synchronous Sequential Circuits

2.11 SYNCHRONOUS COUNTERS

Flip-Flops can be connected together to perform counting operations. Such a group of Flip-Flops is a **counter**. The number of Flip-Flops used and the way in which they are connected determine the number of states (called the modulus) and also the specific sequence of states that the counter goes through during each complete cycle.

Counters are classified into two broad categories according to the way they are clocked:

- 🚩 Asynchronous counters,
- 🚩 Synchronous counters.

In asynchronous (ripple) counters, the first Flip-Flop is clocked by the external clock pulse and then each successive Flip-Flop is clocked by the output of the preceding Flip-Flop.

In synchronous counters, the clock input is connected to all of the Flip-Flops so that they are clocked simultaneously. Within each of these two categories, counters are classified primarily by the type of sequence, the number of states, or the number of Flip-Flops in the counter.

The term 'synchronous' refers to events that have a fixed time relationship with each other. In synchronous counter, the clock pulses are applied to all Flip-Flops simultaneously. Hence there is minimum propagation delay.


S.No	Asynchronous (ripple) counter	Synchronous counter
1	All the Flip-Flops are not clocked simultaneously.	All the Flip-Flops are clocked simultaneously.
2	The delay times of all Flip-Flops are added. Therefore there is considerable propagation delay.	There is minimum propagation delay.
3	Speed of operation is low	Speed of operation is high.
4	Logic circuit is very simple	Design involves complex logic circuit

Synchronous Sequential Circuits

	even for more number of states.	as number of state increases.
5	Minimum numbers of logic devices are needed.	The number of logic devices is more than ripple counters.
6	Cheaper than synchronous counters.	Costlier than ripple counters.

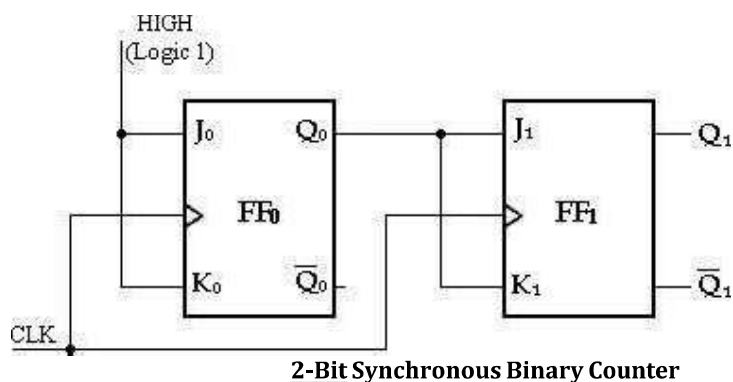2.11.2 2-Bit Synchronous Binary Counter

In this counter the clock signal is connected in parallel to clock inputs of both the Flip-Flops (FF_0 and FF_1). The output of FF_0 is connected to J_1 and K_1 inputs of the second Flip-Flop (FF_1).




Assume that the counter is initially in the binary 0 state: i.e., both Flip-Flops are RESET. When the positive edge of the first clock pulse is applied, FF_0 will toggle because $J_0 = K_0 = 1$, whereas FF_1 output will remain 0 because $J_1 = K_1 = 0$. After the first clock pulse $Q_0 = 1$ and $Q_1 = 0$.

When the leading edge of CLK2 occurs, FF_0 will toggle and Q_0 will go LOW. Since FF_1 has a HIGH ($Q_0 = 1$) on its J_1 and K_1 inputs at the triggering edge of this clock pulse, the Flip-Flop toggles and Q_1 goes HIGH. Thus, after CLK2, $Q_0 = 0$ and $Q_1 = 1$.

When the leading edge of CLK3 occurs, FF_0 again toggles to the SET state ($Q_0 = 1$), and FF_1 remains SET ($Q_1 = 1$) because its J_1 and K_1 inputs are both LOW ($Q_0 = 0$). After this triggering edge, $Q_0 = 1$ and $Q_1 = 1$.


Finally, at the leading edge of CLK4, Q_0 and Q_1 go LOW because they both have a toggle condition on their J_1 and K_1 inputs. The counter has now recycled to its original state, $Q_0 = Q_1 = 0$.

Synchronous Sequential Circuits

 

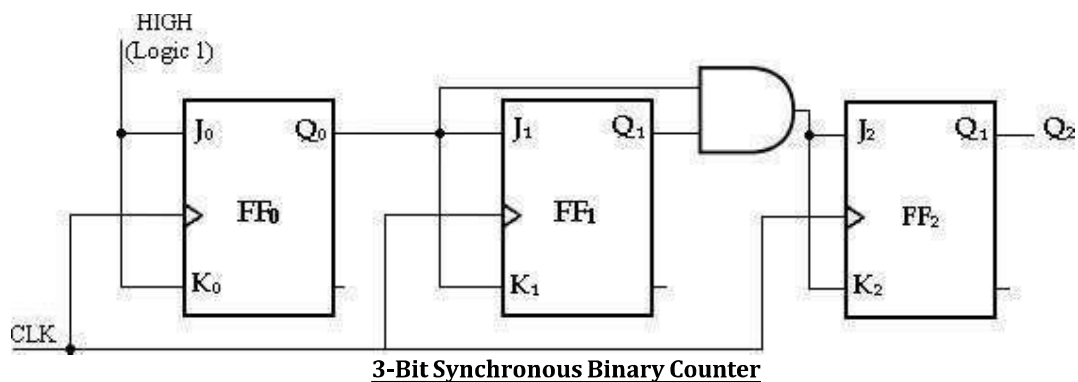2.11.3 3-Bit Synchronous Binary Counter

A 3 bit synchronous binary counter is constructed with three JK Flip-Flops and an AND gate. The output of FF₀ (Q₀) changes on each clock pulse as the counter progresses from its original state to its final state and then back to its original state. To produce this operation, FF₀ must be held in the toggle mode by constant HIGH, on its J₀ and K₀ inputs.




The output of FF₁ (Q₁) goes to the opposite state following each time Q₀= 1. This change occurs at CLK2, CLK4, CLK6, and CLK8. The CLK8 pulse causes the counter to recycle. To produce this operation, Q₀ is connected to the J₁ and K₁ inputs of FF₁. When Q₀= 1 and a clock pulse occurs, FF₁ is in the toggle mode and therefore changes state. When Q₀= 0, FF₁ is in the no-change mode and remains in its present state.

The output of FF₂ (Q₂) changes state both times; it is preceded by the unique condition in which both Q₀ and Q₁ are HIGH. This condition is detected by the AND gate and applied to the J₂ and K₂ inputs of FF₃. Whenever both outputs Q₀= Q₁= 1,

Synchronous Sequential Circuits

the output of the AND gate makes the $J_2= K_2= 1$ and FF_2 toggles on the following clock pulse. Otherwise, the J_2 and K_2 inputs of FF_2 are held LOW by the AND gate output, FF_2 does not change state.


CLOCK Pulse	Q_2	Q_1	Q_0
Initially	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
8 (recycles)	0	0	0

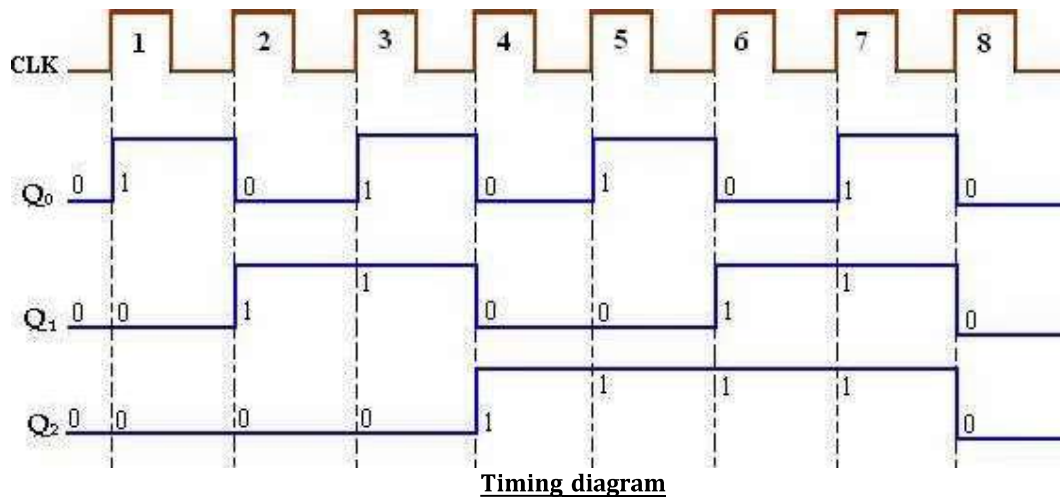


2.11.4 4-Bit Synchronous Binary Counter

This particular counter is implemented with negative edge-triggered Flip-Flops. The reasoning behind the J and K input control for the first three Flip-Flops is the same as previously discussed for the 3-bit counter. For the fourth stage, the Flip-Flop has to change the state when $Q_0= Q_1= Q_2= 1$. This condition is decoded by AND gate G_3 .

Synchronous Sequential Circuits

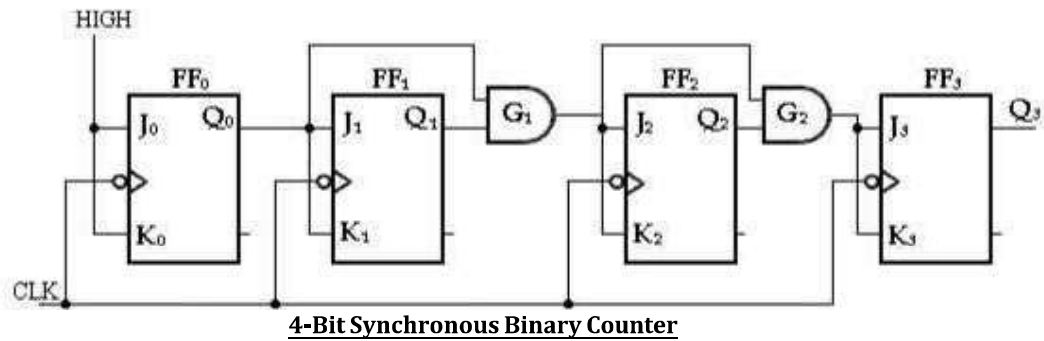

 
Therefore, when $Q_0 = Q_1 = Q_2 = 1$, Flip-Flop FF₃ toggles and for all other times it is in a no-change condition. Points where the AND gate outputs are HIGH are indicated by the shaded areas.



2.11.5 4-Bit Synchronous Decade Counter: (BCD Counter):

BCD decade counter has a sequence from 0000 to 1001 (9). After 1001 state it must recycle back to 0000 state. This counter requires four Flip-Flops and AND/OR logic as shown below.

Synchronous Sequential Circuits

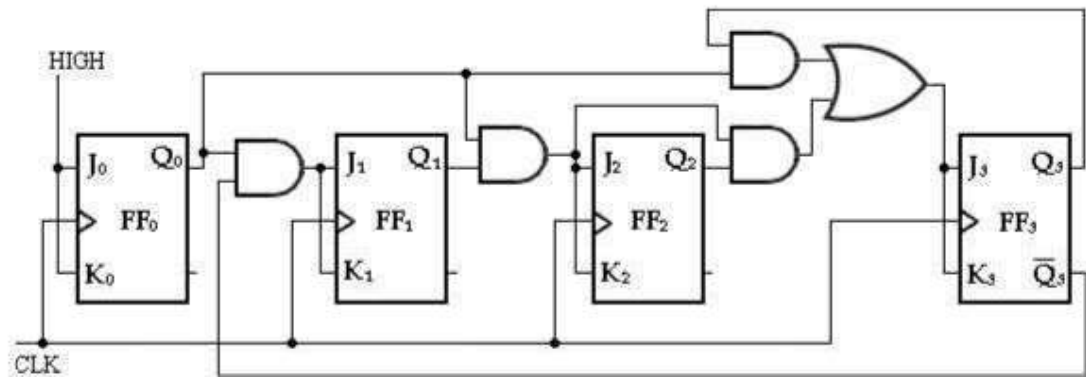

4-Bit Synchronous Decade Counter

CLOCK Pulse	Q ₃	Q ₂	Q ₁	Q ₀
Initially	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10(recycles)	0	0	0	0

- x First, notice that FF₀ (Q₀) toggles on each clock pulse, so the logic equation for its J₀ and K₀ inputs is

$$J_0 = K_0 = 1$$

This equation is implemented by connecting J₀ and K₀ to a constant HIGH level.

- x Next, notice from table, that FF₁ (Q₁) changes on the next clock pulse each time Q₀ = 1 and Q₃ = 0, so the logic equation for the J₁ and K₁ inputs is

$$J_1 = K_1 = Q_0 Q_3'$$

This equation is implemented by ANDing Q₀ and Q₃ and connecting the gate output to the J₁ and K₁ inputs of FF₁.

- x Flip-Flop 2 (Q₂) changes on the next clock pulse each time both Q₀ = Q₁ = 1. This requires an input logic equation as follows:

$$J_2 = K_2 = Q_0 Q_1$$

This equation is implemented by ANDing Q₀ and Q₁ and connecting the gate output to the J₂ and K₂ inputs of FF₂.


Synchronous Sequential Circuits

- x Finally, FF₃ (Q₃) changes to the opposite state on the next clock pulse each time Q₀ = 1, Q₁ = 1, and Q₂ = 1 (state 7), or when Q₀ = 1 and Q₁ = 1 (state 9).

The equation for this is as follows:

$$J_3 = K_3 = Q_0 Q_1 Q_2 + Q_0 Q_3$$

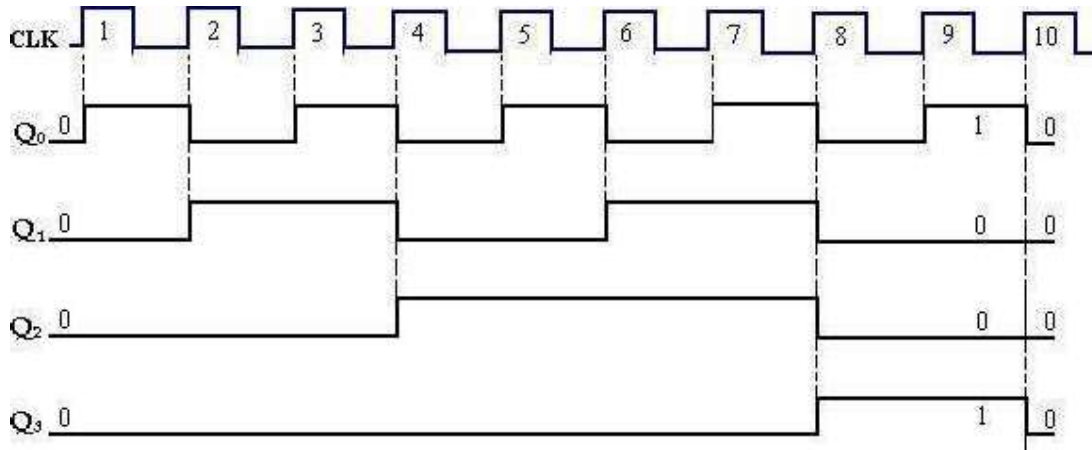This function is implemented with the AND/OR logic connected to the J₃ and K₃ inputs of FF₃.



Timing diagram

2.11.6 Synchronous UP/DOWN Counter

An up/down counter is a bidirectional counter, capable of progressing in either direction through a certain sequence. A 3-bit binary counter that advances upward through its sequence (0, 1, 2, 3, 4, 5, 6, 7) and then can be reversed so that it goes through the sequence in the opposite direction (7, 6, 5, 4, 3, 2, 1, 0) is an illustration of up/down sequential operation.

The complete up/down sequence for a 3-bit binary counter is shown in table below. The arrows indicate the state-to-state movement of the counter for both its UP and its DOWN modes of operation. An examination of Q₀ for both the up and down sequences shows that FF₀ toggles on each clock pulse. Thus, the J₀ and K₀ inputs of FF₀ are,

$$J_0 = K_0 = 1$$

Synchronous Sequential Circuits

CLOCK PULSE	UP	Q ₂	Q ₁	Q ₀	DOWN
0	↕	0	0	0	↕
1	↕	0	0	1	↕
2	↕	0	1	0	↕
3	↕	0	1	1	↕
4	↕	1	0	0	↕
5	↕	1	0	1	↕
6	↕	1	1	0	↕
7	↕	1	1	1	↕


To form a synchronous UP/DOWN counter, the control input (UP/DOWN) is used to allow either the normal output or the inverted output of one Flip-Flop to the J and K inputs of the next Flip-Flop. When UP/DOWN= 1, the MOD 8 counter will count from 000 to 111 and UP/DOWN= 0, it will count from 111 to 000.

When UP/DOWN= 1, it will enable AND gates 1 and 3 and disable AND gates 2 and 4. This allows the Q₀ and Q₁ outputs through the AND gates to the J and K inputs of the following Flip-Flops, so the counter counts up as pulses are applied.

When UP/DOWN= 0, the reverse action takes place.

$$J_1 = K_1 = (Q_0 \cdot UP) + (Q_0' \cdot DOWN)$$
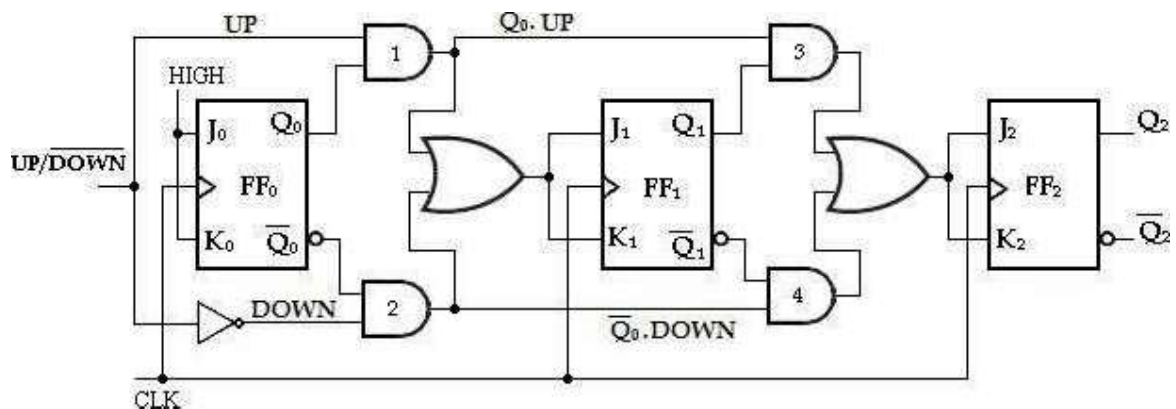
$$J_2 = K_2 = (Q_0 \cdot Q_1 \cdot UP) + (Q_0' \cdot Q_1' \cdot DOWN)$$



3-bit UP/DOWN Synchronous Counter

The counter with 'n' Flip-Flops has maximum MOD number 2_n . Find the number of Flip-Flops (n) required for the desired MOD number (N) using the equation,

$$2_n \geq N$$

- (i) For example, a 3 bit binary counter is a MOD 8 counter. The basic counter can be modified to produce MOD numbers less than 2_n by allowing the counter to skip those are normally part of counting sequence.

$$n = 3$$

$$N = 8$$

$$2_n = 2_3 = 8 = N$$

- (ii) **MOD 5 Counter:**

$$2_n = N$$

$$2_n = 5$$

$$2_2 = 4 \text{ less than } N.$$

$$2_3 = 8 > N(5)$$

Therefore, 3 Flip-Flops are required.

- (iii) **MOD 10 Counter:**

$$2_n = N = 10$$

$$2_3 = 8 \text{ less than } N.$$

$$2_4 = 16 > N(10).$$

To construct any MOD-N counter, the following methods can be used.

1. Find the number of Flip-Flops (n) required for the desired MOD number (N) using the equation,


$$2_n \geq N.$$
2. Connect all the Flip-Flops as a required counter.
3. Find the binary number for N.
4. Connect all Flip-Flop outputs for which Q= 1 when the count is N, as inputs to NAND gate.
5. Connect the NAND gate output to the CLR input of each Flip-Flop.

Synchronous Sequential Circuits

When the counter reaches N_{th} state, the output of the NAND gate goes LOW, resetting all Flip-Flops to 0. Therefore the counter counts from 0 through $N-1$.

For example, MOD-10 counter reaches state 10 (1010). i.e., $Q_3Q_2Q_1Q_0 = 1010$. The outputs Q_3 and Q_1 are connected to the NAND gate and the output of the NAND gate goes LOW and resetting all Flip-Flops to zero. Therefore MOD-10 counter counts from 0000 to 1001. And then recycles to the zero value.

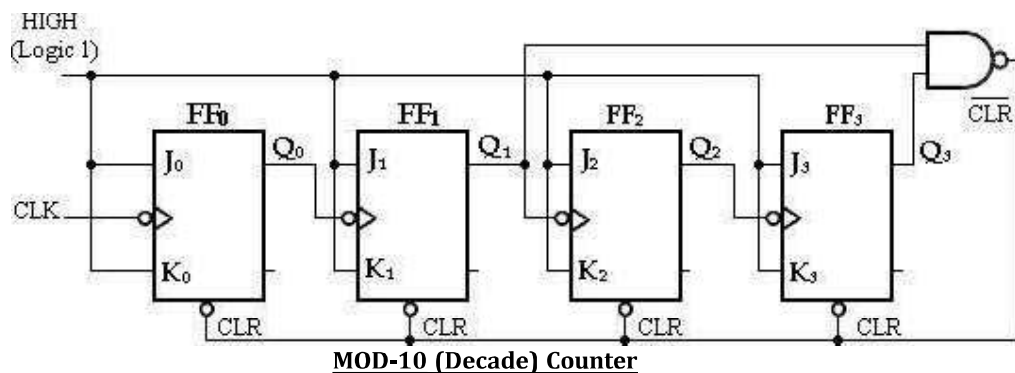The MOD-10 counter circuit is shown below.



2.12 SHIFT REGISTERS:

A register is simply a group of Flip-Flops that can be used to store a binary number. There must be one Flip-Flop for each bit in the binary number. For instance, a register used to store an 8-bit binary number must have 8 Flip-Flops.


The Flip-Flops must be connected such that the binary number can be entered (shifted) into the register and possibly shifted out. A group of Flip-Flops connected to provide either or both of these functions is called a *shift register*.

The bits in a binary number (data) can be removed from one place to another in either of two ways. The first method involves shifting the data one bit at a time in a serial fashion, beginning with either the most significant bit (MSB) or the least significant bit (LSB). This technique is referred to as *serial shifting*. The second method involves shifting all the data bits simultaneously and is referred to as *parallel shifting*.

Synchronous Sequential Circuits


There are two ways to shift into a register (serial or parallel) and similarly two ways to shift the data out of the register. This leads to the construction of four basic register types—

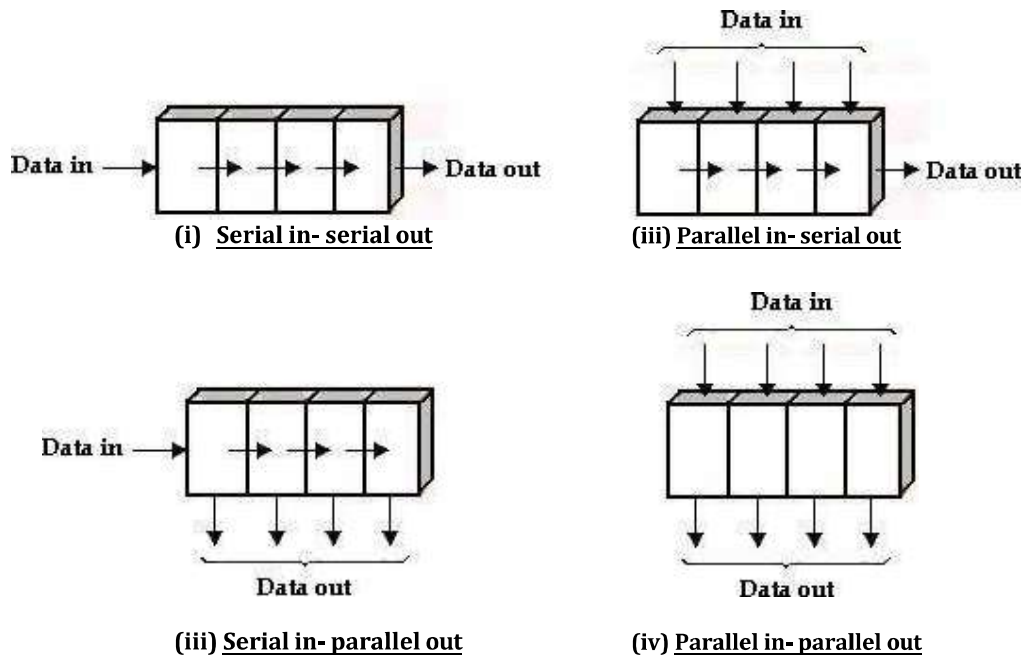- i. Serial in- serial out,
- ii. Serial in- parallel out,
- iii. Parallel in- serial out,
- iv. Parallel in- parallel out.



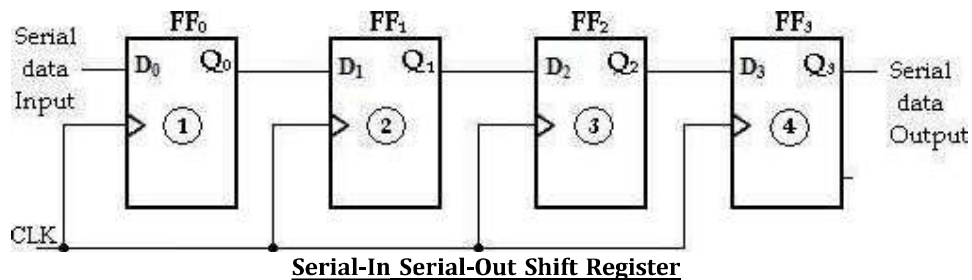2.12.2 Serial-In Serial-Out Shift Register:

The serial in/serial out shift register accepts data serially, i.e., one bit at a time on a single line. It produces the stored information on its output also in serial form.



The entry of the four bits 1010 into the register is illustrated below, beginning with the right-most bit. The register is initially clear. The 0 is put onto the data input line, making $D=0$ for FF_0 . When the first clock pulse is applied, FF_0 is reset, thus storing the 0.


Next the second bit, which is a 1, is applied to the data input, making $D=1$ for FF_0 and $D=0$ for FF_1 because the D input of FF_1 is connected to the Q_0 output. When

Synchronous Sequential Circuits

the second clock pulse occurs, the 1 on the data input is shifted into FF₀, causing FF₀ to set; and the 0 that was in FF₀ is shifted into FF₁.

The third bit, a 0, is now put onto the data-input line, and a clock pulse is applied. The 0 is entered into FF₀, the 1 stored in FF₀ is shifted into FF₁, and the 0 stored in FF₁ is shifted into FF₂.

The last bit, a 1, is now applied to the data input, and a clock pulse is applied. This time the 1 is entered into FF₀, the 0 stored in FF₀ is shifted into FF₁, the 1 stored in FF₁ is shifted into FF₂, and the 0 stored in FF₂ is shifted into FF₃. This completes the serial entry of the four bits into the shift register, where they can be stored for any length of time as long as the Flip-Flops have dc power.

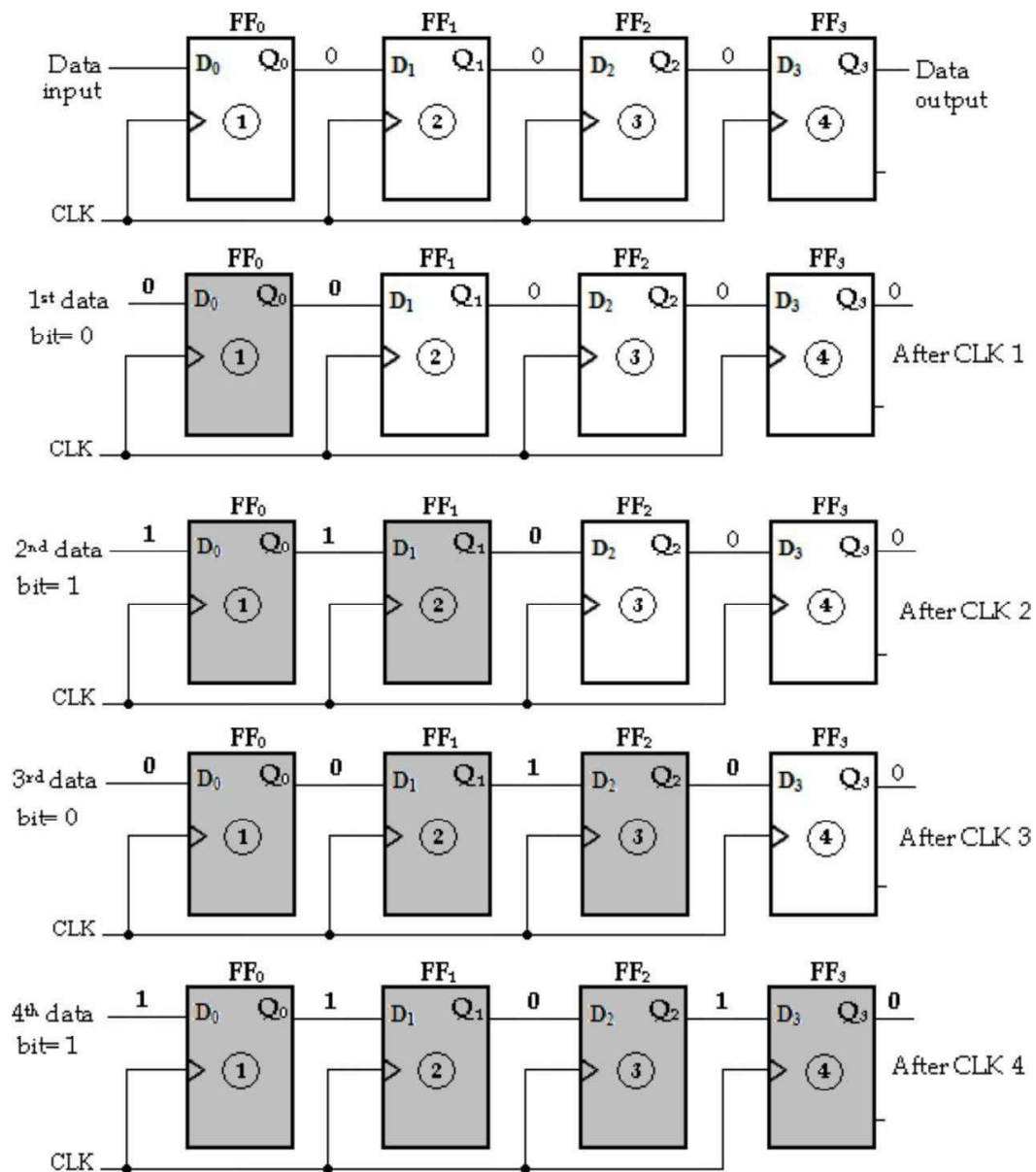


Four bits (1010) being entered serially into the register

Synchronous Sequential Circuits

To get the data out of the register, the bits must be shifted out serially and taken off the Q3 output. After CLK4, the right-most bit, 0, appears on the Q3 output.

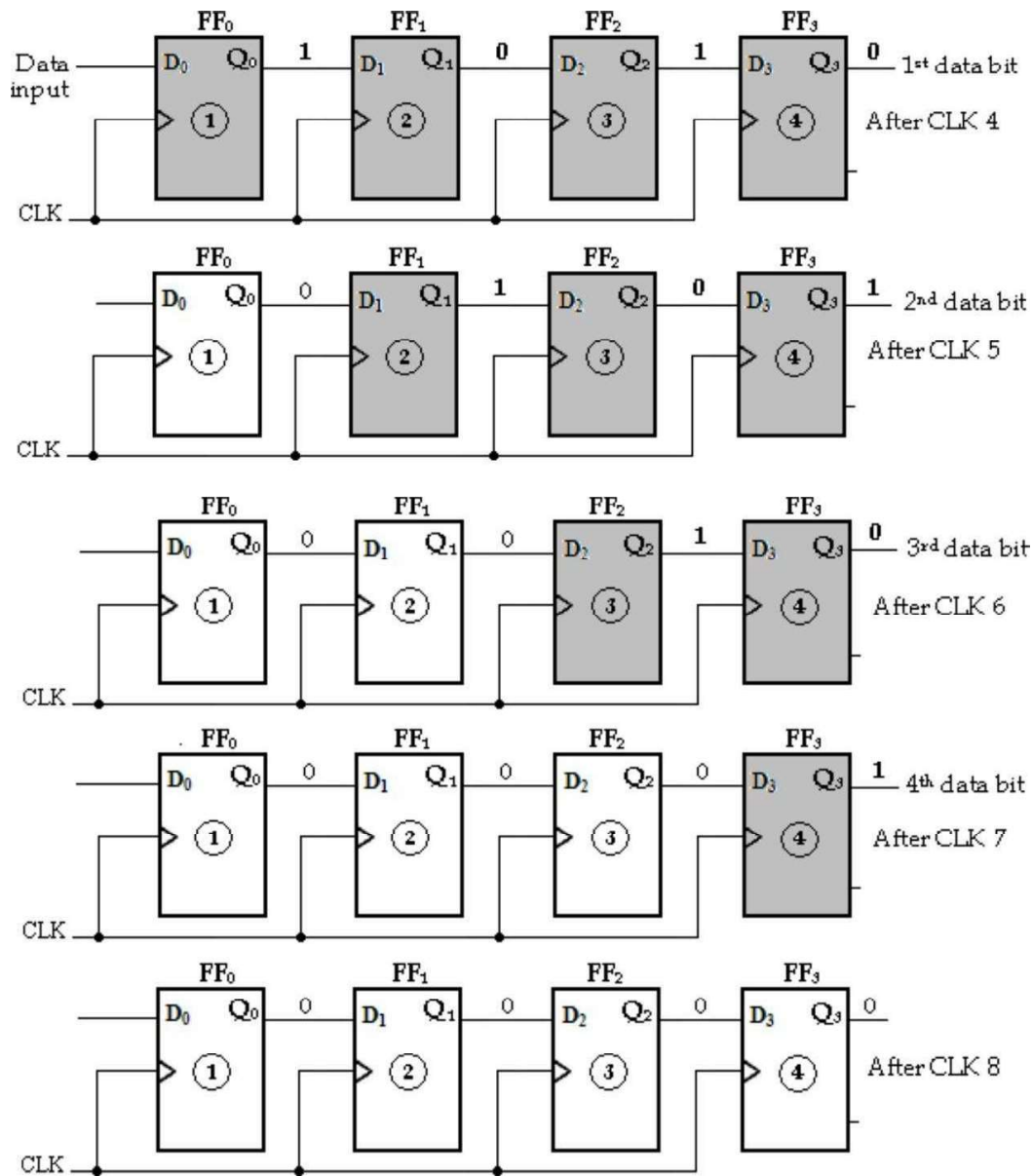When clock pulse CLK5 is applied, the second bit appears on the Q3 output. Clock pulse CLK6 shifts the third bit to the output, and CLK7 shifts the fourth bit to the output. While the original four bits are being shifted out, more bits can be shifted in. All zeros are shown being shifted out, more bits can be shifted in.




Four bits (1010) being entered serially-shifted out of the register and replaced by all zeros

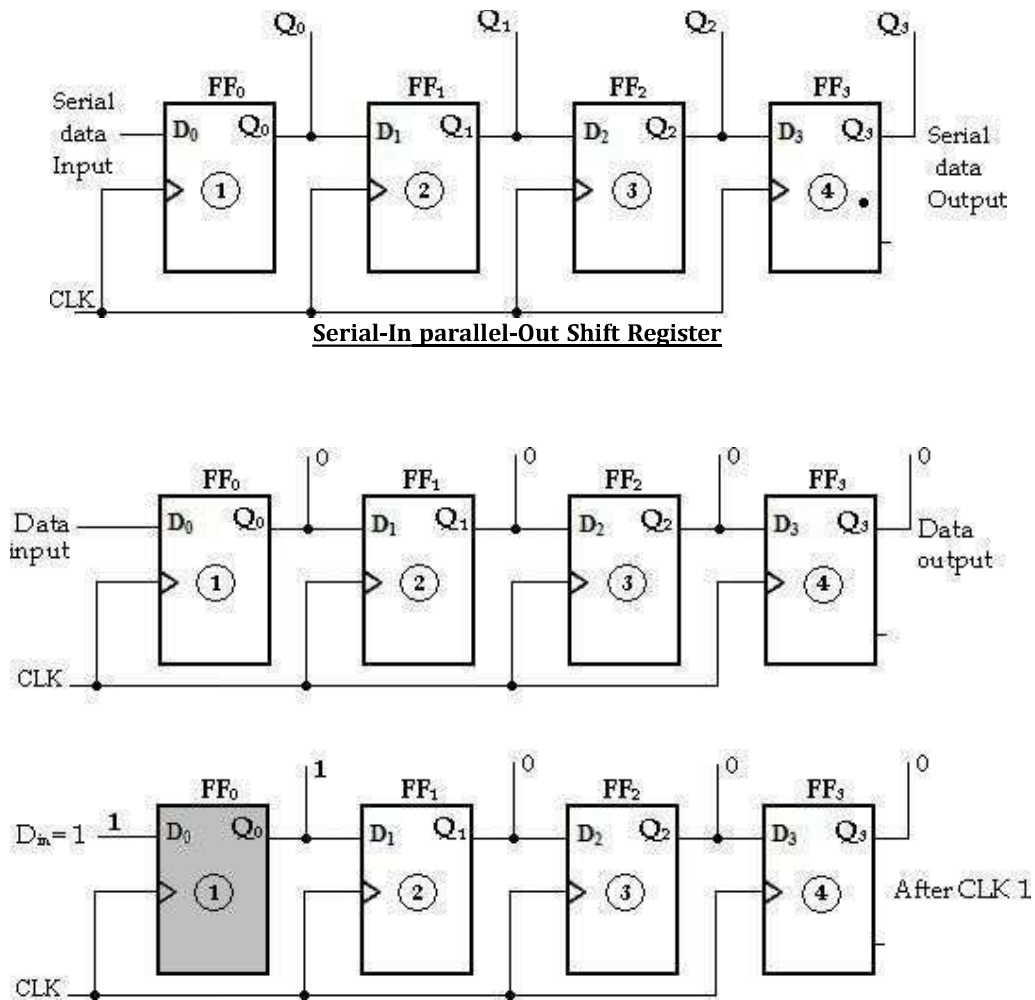
2.12.3 Serial-In Parallel-Out Shift Register:

Synchronous Sequential Circuits

In this shift register, data bits are entered into the register in the same as serial-in serial-out shift register. But the output is taken in parallel. Once the data are stored, each bit appears on its respective output line and all bits are available simultaneously instead of on a bit-by-bit.



Synchronous Sequential Circuits

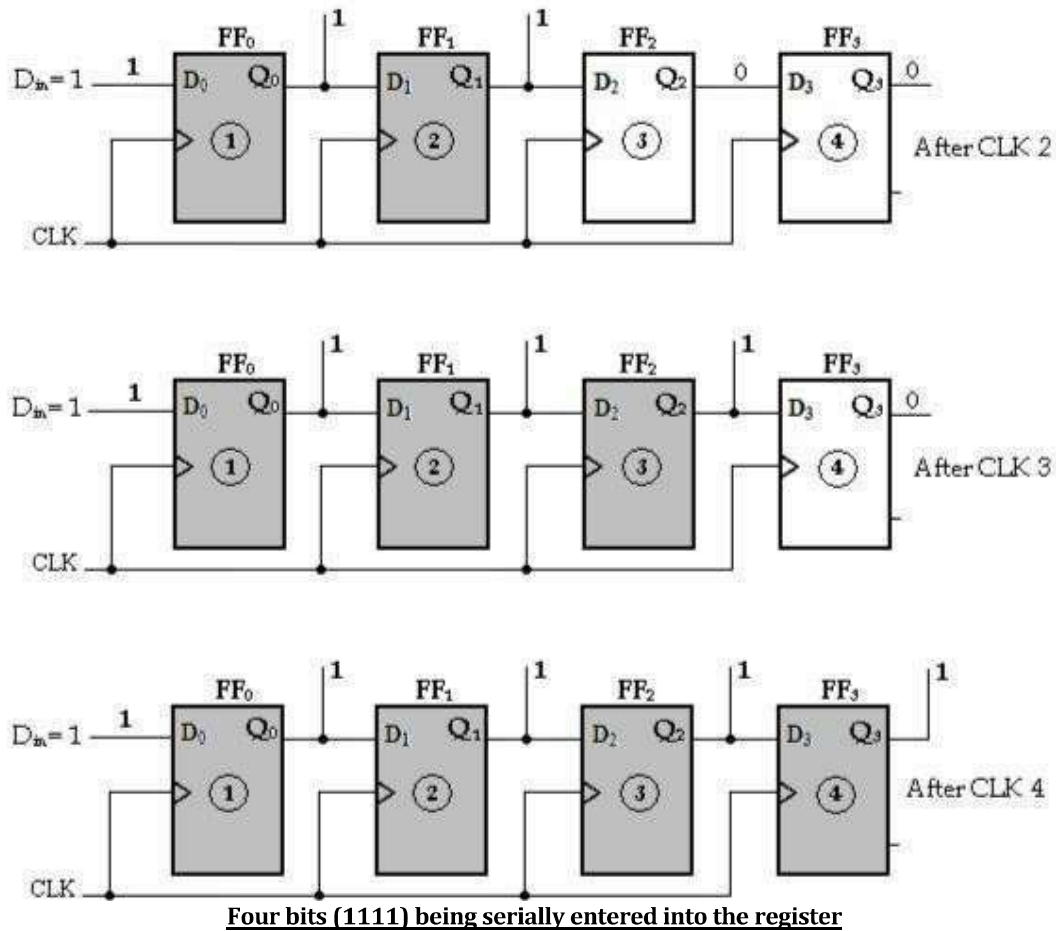


2.12.4 Parallel-In Serial-Out Shift Register:

In this type, the bits are entered in parallel i.e., simultaneously into their respective stages on parallel lines.

A 4-bit parallel-in serial-out shift register is illustrated below. There are four data input lines, X₀, X₁, X₂ and X₃ for entering data in parallel into the register. SHIFT/LOAD input is the control input, which allows four bits of data to **load** in parallel into the register.

When SHIFT/LOAD is LOW, gates G₁, G₂, G₃ and G₄ are enabled, allowing each data bit to be applied to the D input of its respective Flip-Flop. When a clock pulse is applied, the Flip-Flops with D = 1 will **set** and those with D = 0 will **reset**, thereby storing all four bits simultaneously.

Synchronous Sequential Circuits

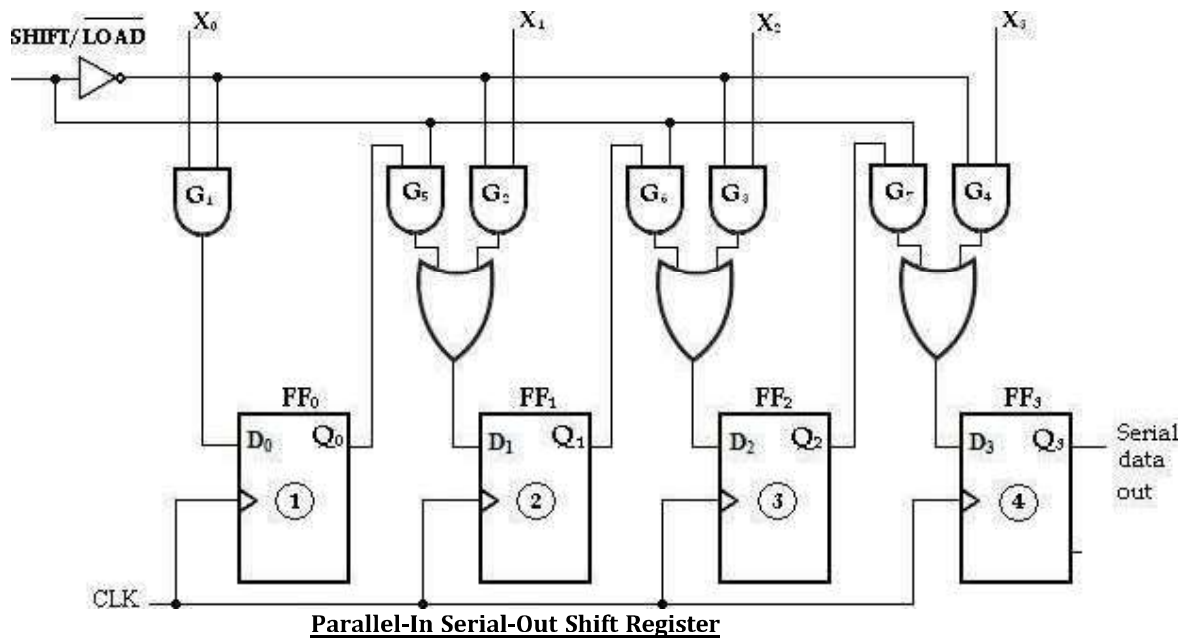


When SHIFT/LOAD is HIGH, gates G_1 , G_2 , G_3 and G_4 are disabled and gates G_5 , G_6 and G_7 are enabled, allowing the data bits to shift right from one stage to the next. The OR gates allow either the normal shifting operation or the parallel data-entry operation, depending on which AND gates are enabled by the level on the SHIFT/LOAD input.

2.12.5 Parallel-In Parallel-Out Shift Register:

In this type, there is simultaneous entry of all data bits and the bits appear on parallel outputs simultaneously.

Synchronous Sequential Circuits

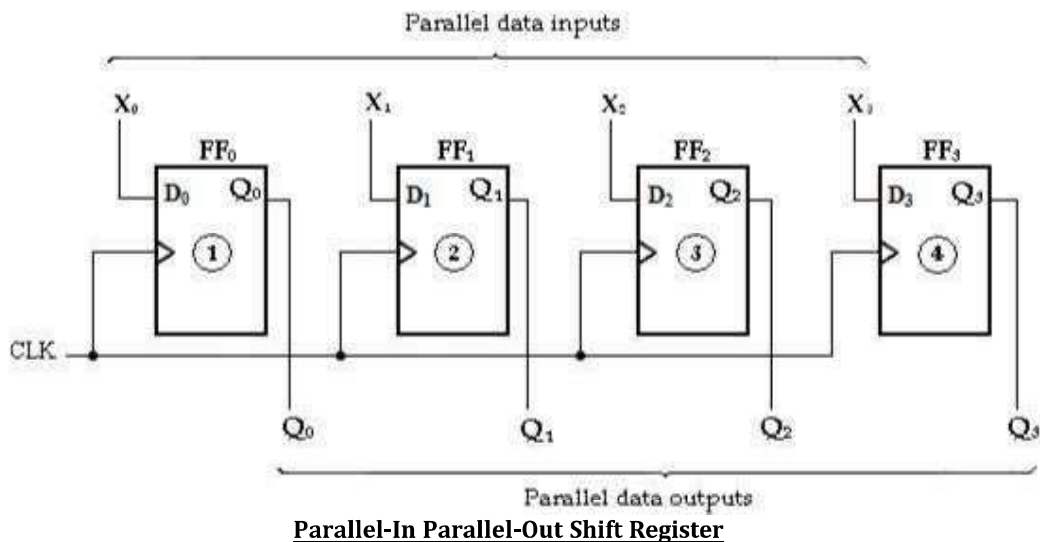


UNIT III COMPUTER FUNDAMENTALS

Functional Units of a Digital Computer: Von Neumann Architecture – Operation and Operands of Computer Hardware Instruction – Instruction Set Architecture (ISA): Memory Location, Address and Operation – Instruction and Instruction Sequencing – Addressing Modes, Encoding of Machine Instruction – Interaction between Assembly and High Level Language.

- Computer hardware consists of electronic circuits, magnetic and optical storage devices, displays, electromechanical devices, and communication facilities.
- Computer architecture encompasses the specification of an instruction set and the functional behaviour of the hardware units that implement the instructions.

FUNCTIONAL UNITS:

- A Computer is a fast electronic calculating machine that accepts digitized information from the user and processes it according to the sequence of instructions and provides the processed information to the user.
- A computer consists of five functionally independent main parts: input, memory, arithmetic and logic, output, and control units, as shown in Figure.
- The input unit accepts coded information from human operators using devices such as keyboards or from other computers over digital communication lines.
- The information received is stored in the computer's memory, either for later use or to be processed immediately by the arithmetic and logic unit. The processing steps are specified by a program that is also stored in the memory.
- Finally, the results are sent back to the outside world through the output unit.
- All of these actions are coordinated by the control unit. An interconnection network provides the means for the functional units to exchange information and coordinate their actions. We refer to the arithmetic and logic circuits, in conjunction with the main control circuits, as the processor. Input and output equipment is often collectively referred to as the input-output (I/O) unit.

 

Basic functional units of a computer.

- It is convenient to categorize this information as either instructions or data. Instructions, or machine instructions, are explicit commands that
 - Govern the transfer of information within a computer as well as between the computer and its I/O devices.
 - Specify the arithmetic and logic operations to be performed.

- The instructions and data handled by a computer must be encoded in a suitable format. Most present-day hardware employs digital circuits that have only two stable states.
- Each instruction, number, or character is encoded as a string of binary digits called *bits*, each having one of two possible values, 0 or 1, represented by the two stable states. Numbers are usually represented in positional binary notation. Alphanumeric characters are also expressed in terms of binary codes.

Input Unit

- Computers accept coded information through input units. The most common input device is the keyboard. Whenever a key is pressed, the corresponding letter or digit is automatically translated into its corresponding binary code and transmitted to the processor.
- Many other kinds of input devices for human-computer interaction are available, including the touchpad, mouse, joystick, and trackball. These are often used as graphic input devices in conjunction with displays.
- Microphones can be used to capture audio input which is then sampled and converted into digital codes for storage and processing. Similarly, cameras can be used to capture video input.
- Digital communication facilities, such as the Internet, can also provide input to a computer from other computers and database servers.

Memory Unit

- The function of the memory unit is to store programs and data. There are two classes of storage, called primary and secondary.

Primary Memory

- Primary memory, also called main memory, is a fast memory that operates at electronic speeds. Programs must be stored in this memory while they are being executed. The memory consists of a large number of semiconductor storage cells, each capable of storing one bit of information. These cells are rarely read or written individually.
- Instead, they are handled in groups of fixed size called words. The memory is organized so that one word can be stored or retrieved in one basic operation. The number of bits in each word is referred to as the word length of the computer, typically 16, 32, or 64 bits.
- To provide easy access to any word in the memory, a distinct address is associated with each word location. Addresses are consecutive numbers, starting from 0, that identify successive locations. A particular word is accessed by specifying its address and issuing a control command to the memory that starts the storage or retrieval process.
- Instructions and data can be written into or read from the memory under the control of the processor. It is essential to be able to access any word location in the memory as quickly as possible.
- A memory in which any location can be accessed in a short and fixed amount of time after specifying its address is called a random-access memory (RAM). The time required to access one word is called the memory access time. This time is independent of the location of the word

circuit chip. The purpose of the cache is to facilitate high instruction execution rates.

- At the start of program execution, the cache is empty. All program instructions and any required data are stored in the main memory. As execution proceeds, instructions are fetched into the processor chip, and a copy of each is placed in the cache. When the execution of an instruction requires data located in the main memory, the data are fetched and copies are also placed in the cache.
- Now, suppose a number of instructions are executed repeatedly as happens in a program loop. If these instructions are available in the cache, they can be fetched quickly during the period of repeated use. Similarly, if the same data locations are accessed repeatedly while copies of their contents are available in the cache, they can be fetched quickly.

Secondary Storage

- Although primary memory is essential, it tends to be expensive and does not retain information when power is turned off. Thus additional, less expensive, permanent secondary storage is used when large amounts of data and many programs have to be stored, particularly for information that is accessed infrequently.
- Access times for secondary storage are longer than for primary memory. A wide selection of secondary storage devices is available, including magnetic disks, optical disks (DVD and CD), and flash memory devices.

Arithmetic and Logic Unit

- Most computer operations are executed in the arithmetic and logic unit (ALU) of the processor. Any arithmetic or logic operation, such as addition, subtraction, multiplication, division, or comparison of numbers, is initiated by bringing the required operands into the processor, where the operation is performed by the ALU.
- For example, if two numbers located in the memory are to be added, they are brought into the processor, and the addition is carried out by the ALU. The sum may then be stored in the memory or retained in the processor for immediate use.
- When operands are brought into the processor, they are stored in high-speed storage elements called registers. Each register can store one word of data. Access times to registers are even shorter than access times to the cache unit on the processor chip.

Output Unit

- The output unit is the counterpart of the input unit. Its function is to send processed results to the outside world. A familiar example of such a device is a printer. Most printers employ either photocopying techniques, as in laser printers, or ink jet streams. Such printers may generate output at speeds of 20 or more pages per minute. However, printers are mechanical devices, and as such are quite slow compared to the electronic speed of a processor.
- Some units, such as graphic displays, provide both an output function, showing text and graphics, and an input function, through touch screen capability. The dual role of such units is the reason for using the single name input/output (I/O) unit in many cases.
- Control circuits are responsible for generating the timing signals that govern the transfers and determine when a given action is to take place.
- Data transfers between the processor and the memory are also managed by the control unit through timing signals. It is reasonable to think of a control unit as a well-defined, physically separate unit that interacts with other parts of the computer.
- Much of the control circuitry is physically distributed throughout the computer. A large set of control lines (wires) carries the signals used for timing and synchronization of events in all units.

The operation of a computer can be summarized as follows:

- The computer accepts information in the form of programs and data through an input unit and stores it in the memory.

- Information stored in the memory is fetched under program control into an arithmetic and logic unit, where it is processed.
- Processed information leaves the computer through an output unit.
- All activities in the computer are directed by the control unit.

BASIC OPERATIONAL CONCEPTS:


- To perform a given task, an appropriate program consisting of a list of instructions is stored in the memory. Individual instructions are brought from the memory into the processor, which executes the specified operations. Data to be used as instruction operands are also stored in the memory.
- A typical instruction might be

Load R2, LOC

- This instruction reads the contents of a memory location whose address is represented symbolically by the label LOC and loads them into processor register R2.
- The original contents of location LOC are preserved, whereas those of register R2 are overwritten.
- Execution of this instruction requires several steps.
 - First, the instruction is fetched from the memory into the processor.
 - Next, the operation to be performed is determined by the control unit.
 - The operand at LOC is then fetched from the memory into the processor.
 - Finally, the operand is stored in register R2.
- After operands have been loaded from memory into processor registers, arithmetic or logic operations can be performed on them. For example, the instruction adds the contents of registers R2 and R3, then places their sum into register R4.

Add R4, R2, R3

- The operands in R2 and R3 are not altered, but the previous value in R4 is overwritten by the sum.
- Figure shows how the memory and the processor can be connected. In addition to the ALU and the control circuitry, the processor contains a number of registers used for several different purposes.
- The instruction register (IR) holds the instruction that is currently being executed. Its output is available to the control circuits, which generate the timing signals that control the various processing elements involved in executing the instruction.
- The program counter (PC) is another specialized register. It contains the memory address of the next instruction to be fetched and executed. During the execution of an instruction, the contents of the PC are updated to correspond to the address of the next instruction to be executed.
- In addition to the IR and PC, Figure shows general-purpose registers R₀ through R_{n-1}, often called processor registers.

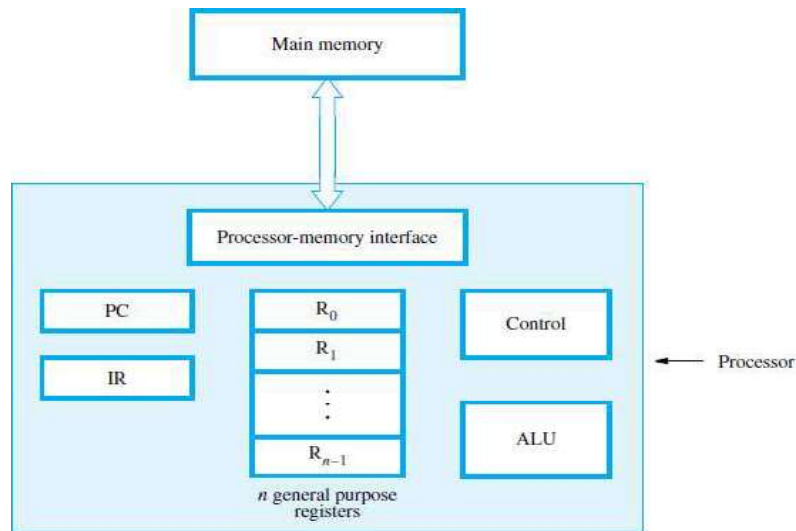

Connection between the processor and the main memory.

- The processor-memory interface is a circuit which manages the transfer of data between the main memory and the processor. If a word is to be read from the memory, the interface sends the address of that word to the memory along with a Read control signal.
- The interface waits for the word to be retrieved, then transfers it to the appropriate processor register.
- If a word is to be written into memory, the interface transfers both the address and the word to the memory along with a Write control signal.
- **Let us now consider some typical operating steps.** A program must be in the main memory in order for it to be executed. It is often transferred there from secondary storage through the input unit.
- Execution of the program begins when the PC is set to point to the first instruction of the program. The contents of the PC are transferred to the memory along with a Read control signal.
- When the addressed word (in this case, the first instruction of the program) has been fetched from the memory it is loaded into register IR. At this point, the instruction is ready to be interpreted and executed.
- Instructions such as Load, Store, and Add perform data transfer and arithmetic operations. If an operand that resides in the memory is required for an instruction, it is fetched by sending its address to the memory and initiating a Read operation.
- When the operand has been fetched from the memory, it is transferred to a processor register. After operands have been fetched in this way, the ALU can perform a desired arithmetic operation, such as Add, on the values in processor registers. The result is sent to a processor register.
- If the result is to be written into the memory with a Store instruction, it is transferred from the processor register to the memory, along with the address of the location where the result is to be stored, then a Write operation is initiated.
- At some point during the execution of each instruction, the contents of the PC are incremented so that the PC points to the next instruction to be executed. Thus, as soon as the execution of the current instruction is completed, the processor is ready to fetch a new instruction.
- In addition to transferring data between the memory and the processor, the computer accepts data from input devices and sends data to output devices. Thus, some machine instructions are provided for the purpose of handling I/O transfers.
- Normal execution of a program may be preempted if some device requires urgent service. In order to respond immediately, execution of the current program must be suspended.
- To cause this, the device raises an interrupt signal, which is a request for service by the

processor. The processor provides the requested service by executing a program called an interrupt-service routine.

- Normally, the information that is saved includes the contents of the PC, the contents of the general-purpose registers, and some control information. When the interrupt-service routine is completed, the state of the processor is restored from the memory so that the interrupted program may continue.

INSTRUCTIONS:

- The words of a computer's language are called instructions, and its vocabulary is called an instruction set. The idea that instructions and data of many type can be stored in memory is known as stored program concept.

OPERATIONS OF THE COMPUTER HARDWARE:

- Every computer must be able to perform arithmetic. The MIPS assembly language notation

add a, b, c

instructs a computer to add the two variables b and c and to put their sum in a.

- Each MIPS arithmetic instruction performs only one operation and must always have exactly three variables. The following sequence of instructions adds the four variables:

add a, b, c # The sum of b and c is placed in a

add a, a, d # The sum of b, c, and d is now in a

add a, a, e # The sum of b, c, d, and e is now in a

- Thus, it takes three instructions to sum the four variables. The words to the right of the sharp symbol (#) on each line above are comments for the human reader, so the computer ignores them.

MIPS operands

Name	Example	Comments
32 registers	\$s0-\$s7, \$t0-\$t9, \$zero, \$a0-\$a3, \$v0-\$v1, \$gp, \$fp, \$sp, \$ra, \$at	Fast locations for data. In MIPS, data must be in registers to perform arithmetic, register \$zero always equals 0, and register \$at is reserved by the assembler to handle large constants.
2 ³⁰ memory words	Memory[0], Memory[4], ..., Memory[4294967292]	Accessed only by data transfer instructions. MIPS uses byte addresses, so sequential word addresses differ by 4. Memory holds data structures, arrays, and spilled registers.

- Figure shows that MIPS use either registers or memory locations as operands. MIPS uses 32 registers for storing data temporarily and for fast access. Memory locations are accessed by data transfer instructions.
- Figure shows that MIPS assembly language. There are five categories of instructions namely, arithmetic, data transfer, logical, conditional branch and unconditional jump.

MIPS assembly language

Category	Instruction	Example	Meaning	Comments
Arithmetic	add	add \$s1,\$s2,\$s3	$\$s1 = \$s2 + \$s3$	Three register operands
	subtract	sub \$s1,\$s2,\$s3	$\$s1 = \$s2 - \$s3$	Three register operands
	add immediate	addi \$s1,\$s2,20	$\$s1 = \$s2 + 20$	Used to add constants
Data transfer	load word	lw \$s1,20(\$s2)	$\$s1 = \text{Memory}[\$s2 + 20]$	Word from memory to register
	store word	sw \$s1,20(\$s2)	$\text{Memory}[\$s2 + 20] = \$s1$	Word from register to memory
	load half	lh \$s1,20(\$s2)	$\$s1 = \text{Memory}[\$s2 + 20]$	Halfword memory to register
	load half unsigned	lhu \$s1,20(\$s2)	$\$s1 = \text{Memory}[\$s2 + 20]$	Halfword memory to register
	store half	sh \$s1,20(\$s2)	$\text{Memory}[\$s2 + 20] = \$s1$	Halfword register to memory
	load byte	lb \$s1,20(\$s2)	$\$s1 = \text{Memory}[\$s2 + 20]$	Byte from memory to register
	load byte unsigned	lbu \$s1,20(\$s2)	$\$s1 = \text{Memory}[\$s2 + 20]$	Byte from memory to register
	store byte	sb \$s1,20(\$s2)	$\text{Memory}[\$s2 + 20] = \$s1$	Byte from register to memory
	load linked word	ll \$s1,20(\$s2)	$\$s1 = \text{Memory}[\$s2 + 20]$	Load word as 1st half of atomic swap
	store condition. word	sc \$s1,20(\$s2)	$\text{Memory}[\$s2 + 20] = \$s1; \$s1 = 0 \text{ or } 1$	Store word as 2nd half of atomic swap
	load upper immed.	lui \$s1,20	$\$s1 = 20 * 2^{16}$	Loads constant in upper 16 bits
Logical	and	and \$s1,\$s2,\$s3	$\$s1 = \$s2 \& \$s3$	Three reg. operands; bit-by-bit AND
	or	or \$s1,\$s2,\$s3	$\$s1 = \$s2 \$s3$	Three reg. operands; bit-by-bit OR
	nor	nor \$s1,\$s2,\$s3	$\$s1 = \sim (\$s2 \$s3)$	Three reg. operands; bit-by-bit NOR
	and immediate	andi \$s1,\$s2,20	$\$s1 = \$s2 \& 20$	Bit-by-bit AND reg with constant
	or immediate	ori \$s1,\$s2,20	$\$s1 = \$s2 20$	Bit-by-bit OR reg with constant
	shift left logical	sll \$s1,\$s2,10	$\$s1 = \$s2 \ll 10$	Shift left by constant
	shift right logical	srl \$s1,\$s2,10	$\$s1 = \$s2 \gg 10$	Shift right by constant
Conditional branch	branch on equal	beq \$s1,\$s2,25	If $(\$s1 == \$s2)$ go to PC + 4 + 100	Equal test; PC-relative branch
	branch on not equal	bne \$s1,\$s2,25	If $(\$s1 \neq \$s2)$ go to PC + 4 + 100	Not equal test; PC-relative
	set on less than	slt \$s1,\$s2,\$s3	If $(\$s2 < \$s3)$ $\$s1 = 1$; else $\$s1 = 0$	Compare less than; for beq, bne
	set on less than unsigned	sltu \$s1,\$s2,\$s3	If $(\$s2 < \$s3)$ $\$s1 = 1$; else $\$s1 = 0$	Compare less than unsigned
	set less than immediate	slti \$s1,\$s2,20	If $(\$s2 < 20)$ $\$s1 = 1$; else $\$s1 = 0$	Compare less than constant
	set less than immediate unsigned	sltiu \$s1,\$s2,20	If $(\$s2 < 20)$ $\$s1 = 1$; else $\$s1 = 0$	Compare less than constant unsigned
Unconditional jump	jump	j 2500	go to 10000	Jump to target address
	jump register	jr \$ra	go to \$ra	For switch, procedure return
	jump and link	jal 2500	$\$ra = PC + 4$; go to 10000	For procedure call

OPERANDS OF THE COMPUTER HARDWARE:

- In MIPS instruction set architecture, operand can either in register or memory. Most of the arithmetic and logical instructions use register operands.
- Three types of operands are used in MIPS: register operands, memory operands and constant or immediate operands.

Register operands

- Unlike programs in high-level languages, the operands of arithmetic instructions are restricted; they must be from a limited number of special locations built directly in hardware called registers.
- The size of a register in the MIPS architecture is 32 bits; groups of 32 bits occur so frequently that they are given the name **word** in the MIPS architecture.
- We will use \$s0, \$s1, . . . for registers that correspond to variables in C and Java programs and \$t0, \$t1, . . . for temporary registers needed to compile the program into MIPS instructions.


add \$t0,\$s1,\$s2

- Data is more useful when in register. A MIPS arithmetic instruction can read two registers, operate on them, and write the result. A MIPS data transfer instruction only reads one operand or writes one operand, without operating on it. Thus, registers take less time to access and have

higher throughput than memory.

Memory operands

- The processor can keep only a small amount of data in registers, but computer memory contains billions of data elements. Hence, data structures (arrays and structures) are kept in memory.
- Arithmetic operations occur only on registers in MIPS instructions; thus, MIPS must include instructions that transfer data between memory and registers. Such instructions are called **data transfer instructions**.
- To access a word in memory, the instruction must supply the memory **address**. Memory is just a large, single-dimensional array, with the address acting as the index to that array, starting at 0. For example, in Figure, the address of the third data element is 2, and the value of Memory [2] is 10.

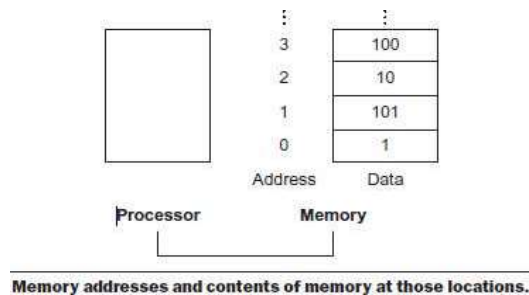

- The data transfer instruction that copies data from memory to a register is traditionally called load. The format of the load instruction is the name of the operation followed by the register to be loaded, then a constant and register used to access memory. The sum of the constant portion of the instruction and the contents of the second register forms the memory address. The actual MIPS name for this instruction is `lw`, standing for load word.

`lw $t0,8($s3)`

- Computers divide into those that use the address of the left most or “**big end**” byte as the word address versus those that use the rightmost or “**little end**” byte. MIPS is in the big-endian camp.
- The instruction complementary to load is traditionally called store; it copies data from a register to memory. The actual MIPS name is `sw`, standing for store word.
- The process of putting less commonly used variables (or those needed later) into memory is called spilling registers.

Constant or Immediate Operands

- Many times a program will use a constant in an operation—for example, incrementing an index to point to the next element of an array.
- For example, to add the constant 4 to register `$s3`, we could use the code

`addi $s3,$s3,4` `# $s3 = $s3 + 4`

- Constant operands occur frequently, and by including constants inside arithmetic instructions, operations are much faster and use less energy than if constants were loaded from memory.

INSTRUCTION REPRESENTATION:


- Instructions are kept in the computer as a series of high and low electronic signals and may be represented as numbers. In fact, each piece of an instruction can be considered as an individual

number, and placing these numbers side by side forms the instruction.

- In MIPS assembly language, registers \$s0 to \$s7 map onto registers 16 to 23, and registers \$t0 to \$t7 map onto registers 8 to 15.
- Hence, \$s0 means register 16, \$s1 means register 17, \$s2 means register 18, . . . , \$t0 means register 8, \$t1 means register 9, and so on.
- Two types of instruction formats are used in MIPS. They are
 - R-type (register) or R-format
 - I-type (immediate) or I-format

R-type

 
- MIPS fields are given names to make them easier to discuss:



- Here is the meaning of each name of the fields in MIPS instructions:
 - op: Basic operation of the instruction, traditionally called the **opcode**.
 - rs: The first register source operand.
 - rt: The second register source operand.
 - rd: The register destination operand. It gets the result of the operation.
 - shamt: Shift amount.


- funct: Function. This field, oft en called the function code, selects the specific variant of the operation in the op field.

 
```
add $t0,$s1,$s2 # Temporary reg $t0=$s2+$s1
```



I-type

- The field of I-format are

 

- The 16-bit address means a load word instruction can load any word with in a region of $\pm 2^{15}$ or 32,768 bytes ($\pm 2^{13}$ or 8192 words) of the address in the base register rs. Similarly, add immediate is limited to constants no larger than $\%2^{15}$.

`lw $t0,32($s3) # Temporary reg $t0 gets A[8]`

- Here, 19 (for \$s3) is placed in the rs field,
- 8 (for \$t0) is placed in the rt field, and
- 32 is placed in the address field.
- 35 is placed in op field for lw instruction.
- The meaning of the rt field has changed for this instruction: in a load word instruction, the rt field specifies the destination register, which receives the result of the load.

LOGICAL OPERATIONS:

- Logical operations work on bits. The following is the list of logical operations supported in MIPS:

Logical operations	C operators	Java operators	MIPS instructions
Shift left	<<	<<	sll
Shift right	>>	>>>	srl
Bit-by-bit AND	&	&	and, andi
Bit-by-bit OR			or, ori
Bit-by-bit NOT	~	~	nor

C and Java logical operators and their corresponding MIPS instructions. MIPS implements NOT using a NOR with one operand being zero.

Sll and srl

- The first class of such operations is called shift s. They move all the bits in a word to the left or right, filling the emptied bits with 0s. The actual name of the two MIPS shift instructions are called shift left logical (sll) and shift right logical (srl).

sll \$t2,\$s0,4 # reg \$t2 = reg \$s0 << 4 bits

- The shamt field in the R-format is used in shift instructions, it stands for shift amount. Hence, the machine language version of the instruction above is

op	rs	rt	rd	shamt	funct
0	0	16	10	4	0

- The encoding of sll is 0 in both the op and funct fields, rd contains 10 (register \$t2), rt contains 16 (register \$s0), and shamt contains 4. The rs field is unused and thus is set to 0.

and

- AND is a bit by-bit operation that leaves a 1 in the result only if both bits of the operands are 1. For example, if register \$t2 contains
- For example, if register \$t1 contains

0000 0000 0000 0000 0000 1101 1100 0000_{two}

and register \$t1 contains

0000 0000 0000 0000 0011 1100 0000 0000_{two}

then, after executing the MIPS instruction

and \$t0,\$t1,\$t2 # reg \$t0 = reg \$t1 & reg \$t2

the value of register \$t0 would be

0000 0000 0000 0000 0000 1100 0000 0000_{two}

- AND can apply a bit pattern to a set of bits to force 0s where there is a 0 in the bit pattern. Such a bit pattern in conjunction with AND is traditionally called a mask, since the mask “conceals” some bits.

- It is a bit-by-bit operation that places a 1 in the result if either operand bit is a 1. To elaborate, if the registers \$t1 and \$t2 are unchanged from the preceding example, the result of the MIPS instruction

or \$t0,\$t1,\$t2 # reg \$t0 = reg \$t1 | reg \$t2

is this value in register \$t0:

0000 0000 0000 0000 0011 1101 1100 0000_{two}

not

- A logical bit-by bit operation with one operand that inverts the bits; that is, it replaces every 1 with a 0, and every 0 with a 1.

Nor

- A logical bit-by bit operation with two operands that calculates the NOT of the OR of the two operands. That is, it calculates a 1 only if there is a 0 in both operands.
- If the register \$t1 is unchanged from the preceding example and register \$t3 has the value 0, the result of the MIPS instruction

nor \$t0,\$t1,\$t3 # reg \$t0 = ~ (reg \$t1 | reg \$t3)

is this value in register \$t0:

1111 1111 1111 1111 1100 0011 1111 1111_{two}

- Constants are useful in AND and OR logical operations as well as in arithmetic operations, so MIPS also provides the instructions and immediate (andi) and or immediate (ori). Constants are rare for NOR, since its main use is to invert the bits of a single operand; thus, the MIPS instruction set architecture has no immediate version of NOR.

DECISION MAKING:

- Decision making is commonly represented in programming languages using the if statement, sometimes combined with go to statements and labels. MIPS assembly language includes two decision-making instructions, similar to an if statement with a go to. The first instruction is

beq register1, register2, L1

- This instruction means go to the statement labeled L1 if the value in register1 equals the value in register2. The mnemonic beq stands for branch if equal. The second instruction is

bne register1, register2, L1

- It means go to the statement labeled L1 if the value in register1 does not equal the value in register2. The mnemonic bne stands for branch if not equal. These two instructions are traditionally called **conditional branches**.

Loops

- Decisions are important both for choosing between two alternatives—found in if statements—and for iterating a computation—found in loops. The same assembly instructions are the building blocks for both cases.
- In MIPS assembly language with an instruction that compares two registers and sets a third

register to 1 if the first is less than the second; otherwise, it is set to 0. The MIPS instruction is called **set on less than, or slt**. For example,

slt \$t0, \$s3, \$s4 # \$t0 = 1 if \$s3 < \$s4
in register \$s4; otherwise, register \$t0 is set to 0.

- Constant operands are popular in comparisons, so there is an immediate version of the set on less than instruction. To test if register \$s2 is less than the constant 10, we can just write

slti \$t0,\$s2,10 # \$t0 = 1 if \$s2 < 10

Case/Switch Statement


- Most programming languages have a case or switch statement that allows the programmer to select one of many alternatives depending on a single value. The simplest way to implement switch is via a sequence of conditional tests, turning the switch statement into a chain of if-then-else statements.
- Sometimes the alternatives may be more efficiently encoded as a table of addresses of alternative instruction sequences, called a **jump address table** or **jump table**, and the program needs only to index into the table and then jump to the appropriate sequence.
- The jump table is then just an array of words containing addresses that correspond to labels in the code. The program loads the appropriate entry from the jump table into a register. It then needs to jump using the address in the register.
- To support such situations, computers like MIPS include a jump register instruction (jr), meaning an unconditional jump to the address specified in a register.
- In addition to allocating these registers, MIPS assembly language includes an instruction just for the procedures: it jumps to an address and simultaneously saves the address of the following instruction in register \$ra. The **jump-and-link instruction** (jal) is simply written
jal Procedure Address
- The link portion of the name means that an address or link is formed that points to the calling site to allow the procedure to return to the proper address. This “link,” stored in register \$ra (register 31), is called the **return address**. The return address is needed because the same procedure could be called from several parts of the program.
- To support such situations, computers like MIPS use jump register instruction (jr), introduced above to help with case statements, meaning an unconditional jump to the address specified in a register:

MIPS ADDRESSING:

32-Bit Immediate Operands

- The MIPS instruction set includes the instruction load upper immediate (lui) specifically to set the upper 16 bits of a constant in a register, allowing a subsequent instruction to specify the lower 16 bits of the constant. Figure 2.17 shows the operation of lui.

 The machine language version of `lui $t0, 255 # $t0 is register 8:`



Contents of register `$t0` after executing `lui $t0, 255:`



The effect of the lui instruction. The instruction lui transfers the 16-bit immediate constant field value into the leftmost 16 bits of the register, filling the lower 16 bits with 0s.

Addressing in Branches and Jumps

- The MIPS jump instructions have the simplest addressing. They use the final MIPS instruction format, called the J-type, which consists of 6 bits for the operation field and the rest of the bits for the address field. Thus,

`j 10000 # go to location 10000`

could be assembled into this format




where the value of the jump opcode is 2 and the jump address is 10000.

- Unlike the jump instruction, the conditional branch instruction must specify two operands in addition to the branch address. Thus,

`bne $s0,$s1,Exit # go to Exit if $s0 ≠ $s1`

 is assembled into this instruction, leaving only 16 bits for the branch address:




MIPS addressing modes:

- Multiple forms of addressing are generically called addressing modes. The MIPS addressing modes are the following:

1. Immediate addressing:

- Immediate addressing, where the operand is a constant within the instruction itself.

1. Immediate addressing

 

- **Example:** `lui $s0,61 #decimal 61 is loaded into upper 16 bits of $s0.`

2. Register addressing:

- Register addressing, where the operand is a register

2. Register addressing




- **Example:** `add $t1,$s1,$s2 # $t1=$s1+$s2`. In the above instruction, \$s1, \$s2 are source registers rs and rt, \$t1 is the destination register rd.

3. Base or Displacement addressing:

- Base or displacement addressing, where the operand is at the memory location whose address is the sum of a register and a constant in the instruction.

3. Base addressing

 


- **Example:** `lw $t0,32($t1) # Temp reg $t0=save[i]`. In the above example, \$t1 is the base register and the operand is available in memory whose memory address is sum of base register \$t1 and offset 32.

4. PC relative addressing:

- PC-relative addressing, where the branch address is the sum of the PC and a constant in the instruction.

4. PC-relative addressing

 


- **Example:** `bne $s0,$s1,Exit # go to Exit if $s0 != $s1`. In the above example branch address is calculated by adding the PC value with the constant in the instruction.

5. Pseudo-direct addressing:

- Pseudo-direct addressing, where the jump address is the 26 bits of the instruction concatenated with the upper bits of the PC


5. Pseudodirect addressing

 

- **Example:** `j 2500 # go to location 1000010`

 6. Indirect mode:

- The effective address of the operand is the contents of a register that is specified in the instruction.




Register indirect addressing.


- To execute the Load instruction in Figure 2.7, the processor uses the value B, which is in register R5, as the effective address of the operand. It requests a Read operation to fetch the contents of location B in the memory. The value from the memory is the desired operand, which the processor loads into register R2.

 7. Index mode:

- The effective address of the operand is generated by adding a constant value to the contents of a register.



(a) Offset is given as a constant

 

(b) Offset is in the index register

Indexed addressing.

- In Figure a, the index register, R5, contains the address of a memory location, and the value X defines an *offset* (also called a *displacement*) from this address to the location where the operand is found.
- An alternative use is illustrated in Figure b. Here, the constant X corresponds to a memory address, and the contents of the index register define the offset to the operand. In either case, the effective address is the sum of two values; one is given explicitly in the instruction, and the other is held in a register.

8. Auto increment/ decrement mode:

- The effective address of the operand is the contents of a register specified in the instruction. After accessing the operand, the contents of this register are automatically incremented / decremented to point to the next item in a list.

IV PROCESSOR


Instruction Execution – Building a Data Path – Designing a Control Unit – Hardwired Control, Microprogrammed Control – Pipelining – Data Hazard – Control Hazards.

A BASIC MIPS IMPLEMENTATION:

- We will be examining an implementation that includes a subset of the core MIPS instruction set:
 - The memory-reference instructions load word (lw) and store word (sw)
 - The arithmetic-logical instructions add, sub, AND, OR, and slt
 - The instructions branch equal (beq) and jump (j), which we add last


An Overview of the Implementation

- For every instruction, the first two steps are identical:
 1. Send the program counter (PC) to the memory that contains the code and fetch the instruction from that memory.
 2. Read one or two registers, using fields of the instruction to select the registers to read.
 3. After these two steps, the actions required to complete the instruction depend on the instruction class. all instruction classes, except jump, use the arithmetic-logical unit (ALU) after reading the registers.
 - The memory-reference instructions use the ALU for an address calculation,
 - the arithmetic-logical instructions for the operation execution, and
 - branches for comparison.
 4. After using the ALU, the actions required to complete various instruction classes differ.
 - A memory-reference instruction will need to access the memory either to read data for a load or write data for a store.
 - An arithmetic-logical or load instruction must write the data from the ALU or memory back into a register.
 - Lastly, for a branch instruction, we may need to change the next instruction address based on the comparison; otherwise, the PC should be incremented by 4 to get the address of the next instruction.
 5. Finally, the result from ALU is stored back in memory or to a register.
- Figure shows the high-level view of a MIPS implementation, focusing on the various functional units and their interconnection.

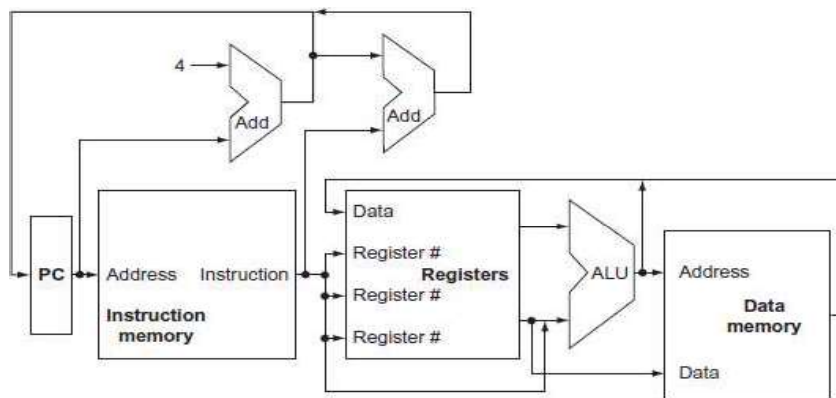

An abstract view of the implementation of the MIPS subset showing the major functional units and the major connections between them.

- All instructions start by using the program counter to supply the instruction address to the instruction memory.
- After the instruction is fetched, the register operands used by an instruction are specified by fields of that instruction. Once the register operands have been fetched, they can be operated on to compute a memory address (for a load or store), to compute an arithmetic result (for an integer arithmetic-logical instruction), or a compare (for a branch).
- If the instruction is an arithmetic-logical instruction, the result from the ALU must be written to a register. If the operation is a load or store, the ALU result is used as an address to either store a value from the registers or load a value from memory into the registers.
- The result from the ALU or memory is written back into the register file. Branches require the use of the ALU output to determine the next instruction address, which comes either from the ALU (where the PC and branch offset are summed) or from an adder that increments the current PC by 4.
- Figure shows data going to a particular unit as coming from two different sources. For example,
 - The value written into the PC can come from one of two adders,
 - The data written into the register file can come from either the ALU or the data memory, and the second input to the ALU can come from a register or the immediate field of the instruction.
 - The selection is commonly done with a device called a multiplexor although this device

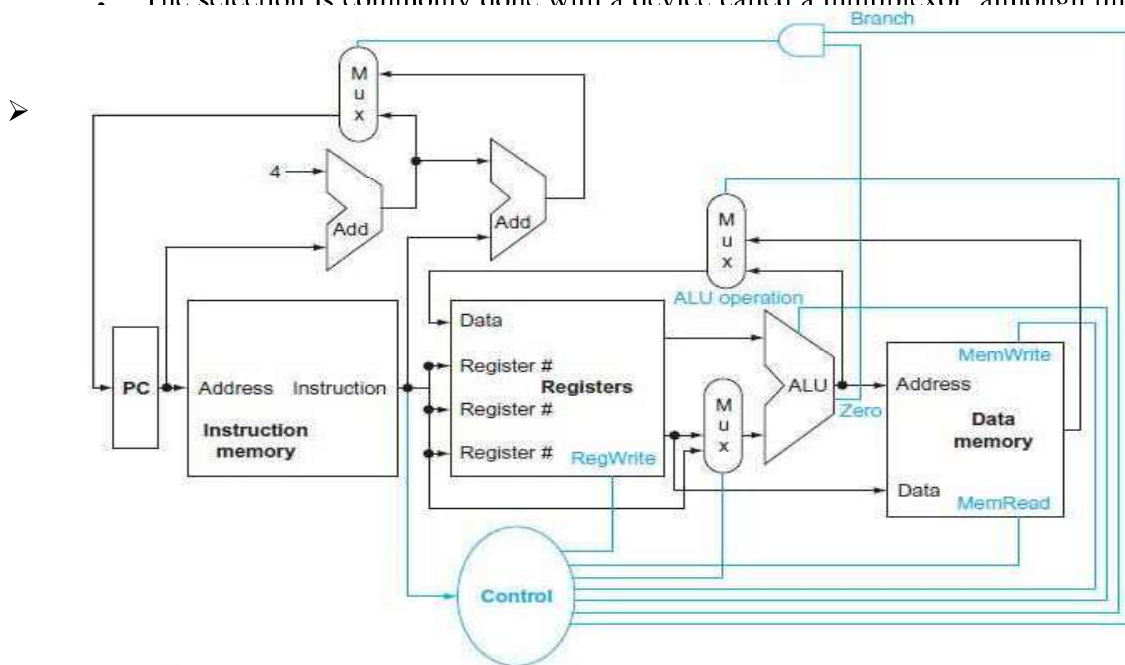

The basic implementation of the MIPS subset, including the necessary multiplexors and control lines.


- A control unit, which has the instruction as an input, is used to determine how to set the control lines for the functional units and two of the multiplexors.
- The top multiplexor (“Mux”) controls what value replaces the PC (PC + 4 or the branch destination address)
 - The middle multiplexor, whose output returns to the register file, is used to steer the output of the ALU (in the case of an arithmetic-logical instruction) or the output of the data memory (in the case of a load)
 - Finally, the bottommost multiplexor is used to determine whether the second ALU input is from the registers (for an arithmetic-logical instruction or a branch) or from the offset field of the instruction (for a load or store).

BUILDING A DATAPATH:

- A unit used to operate on or hold data within a processor. In the MIPS implementation, the datapath elements include the instruction and data memories, the register file, the ALU, and adders.

 1. program counter:


- Program counter (PC) is a 32-bit register. It holds the address of the current instruction. It does not need a write control signal.



b. Program counter

 2. Instruction memory:


- Instruction memory is a memory unit that is used to store the instructions of a program. It get address as input and outputs the instruction which is stored in the given address.
- The instruction memory need only provide read access because the datapath does not write instructions. Since the instruction memory only reads, no read control signal is needed.



a. Instruction memory

 
3. Adder:

- The adder is an ALU wired to always add its two 32-bit inputs and place the sum on its output. The adder is also used to increment the PC to the address of the next instruction. It is combinational circuit that can built from the ALU.



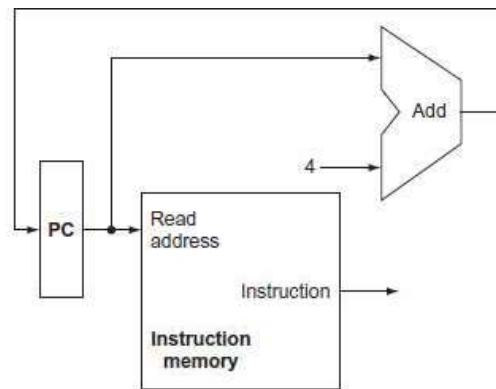c. Adder

- To execute any instruction, we must start by fetching the instruction from memory. To prepare for executing the next instruction, we must also increment the program counter so that it points at the next instruction, 4 bytes later.
- Figure shows how to combine the three elements from above Figure to form a datapath that fetches instructions and increments the PC to obtain the address of the next sequential instruction. The fetched instruction is used by other parts of the datapath.



A portion of the datapath used for fetching instructions and incrementing the program counter.

4. Register file:


- The processor's 32 general-purpose registers are stored in a structure called a register file. A register file is a collection of registers in which any register can be read or written by specifying the number of the register in the file.
- The register file contains the register state of the computer. In addition, we will need an ALU to operate on the values read from the registers.

Read

- For each data word to be read from the registers, we need an input to the register file that specifies the register number to be read and an output from the register file that will carry the value that has been read from the registers. No other control lines are needed.

Write

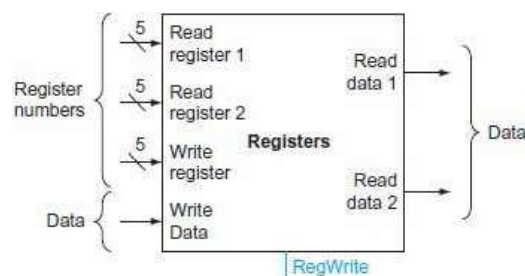To write a data word, we will need two inputs: one to specify the register number to be written and one to supply the data to be written into the register. The write operation needs a write control signal.




a. Registers

- We need a total of four inputs (three for register numbers and one for data) and two outputs (both for data). The register number inputs are 5 bits wide to specify one of 32 registers ($32 = 2^5$), whereas the data input and two data output buses are each 32 bits wide.

 5. ALU:

- ALU, which takes two 32-bit inputs and produces a 32-bit result, as well as a 1-bit signal if the result is 0. The operation to be performed by the
- ALU is controlled with the ALU operation signal, which will be 4 bits wide. We will use the


Zero detection output of the ALU shortly to implement branches.



b. ALU

 6. Data memory:


- The memory unit is a state element with two inputs, an address and a write data and a single output called read data. There are separate read (MemRead) and write control signals (MemWrite)



a. Data memory unit

 7. Sign extended:

- It is used to increase the size of a data item by replicating the high-order sign bit of the original data item in the high order bits of the larger, destination data item.
- It is used to sign-extend the 16-bit offset field in the instruction to a 32-bit signed value.



b. Sign extension unit

Data path elements for branches:

- In MIPS architecture the branch target is given by the sum of the offset field of the instruction and the address of the instruction following the branches.
- The address specified in a branch, which becomes the new program counter (PC) if the branch is taken.
- The data path for a branch uses the ALU to evaluate the branch condition and a separate adder to compute the branch target as the sum of the incremented PC and the sign-extended, lower 16 bits of the instruction (the branch displacement), shifted left 2 bits.
- Control logic is used to decide whether the incremented PC or branch target should replace the PC, based on the Zero output of the ALU.

CONTROL IMPLEMENTATION SCHEME:

- This simple implementation covers load word (lw), store word (sw), branch equal (beq), and the arithmetic-logical instructions add, sub, AND, OR, and set on less than. We will later enhance the design to include a jump instruction (j).

ALU control:

- The MIPS ALU defines the 6 following combinations of four control inputs:

ALU control lines	Function
0000	AND
0001	OR
0010	add
0110	subtract
0111	set on less than
1100	NOR

- Depending on the instruction class, the ALU will need to perform one of these first five functions.
- For load word and store word instructions, ALU is used to compute the memory address by addition.
- For the R-type instructions, the ALU needs to perform one of the five actions (AND, OR, subtract, add, or set on less than), depending on the value of the 6-bit funct (or function) field.
- For branch equal, the ALU must perform a subtraction.
- We can generate the 4-bit ALU control input using a small control unit that has as inputs the function field of the instruction and a 2-bit control field, called ALUOp. ALUOp indicates whether the operation to be performed:
 - 00- add for loads and stores,
 - 01- subtract for beq,
 - 10- determined by the operation encoded in the funct field.
 - The output of the ALU control unit is a 4-bit signal that directly controls the ALU by generating one of the 4-bit combinations.
- The following table shows the ALU control inputs based on the 2-bit ALUOp control and the 6-bit function code. The opcode, listed in the first column, determines the setting of the ALUOp bits.


Instruction opcode	ALUOp	Instruction operation	Funct field	Desired ALU action	ALU control input
LW	00	load word	XXXXXX	add	0010
SW	00	store word	XXXXXX	add	0010
Branch equal	01	branch equal	XXXXXX	subtract	0110
R-type	10	add	100000	add	0010
R-type	10	subtract	100010	subtract	0110
R-type	10	AND	100100	AND	0000
R-type	10	OR	100101	OR	0001
R-type	10	set on less than	101010	set on less than	0111

- ALUOp code is 00 or 01, the desired ALU action does not depend on the function code field; in this case, we say that we “don’t care” about the value of the function code, and the funct field is

shown as XXXXXX. When the ALUOp value is 10, then the function code is used to set the ALU control input.

Designing the Main Control Unit

 - To understand how to connect the fields of an instruction to the data path, it is useful to review the formats of the three instruction classes: the R-type, branch, and load-store instructions. Figure shows these formats.



R-type instruction:

- Instruction format for R-format instructions, which all have an opcode of 0.
- These instructions have three register operands: rs, rt, and rd. Fields rs and rt are sources, and rd is the destination.
- The ALU function is in the funct field and is decoded by the ALU control design in the previous section.
- The R-type instructions that we implement are add, sub, AND, OR, and slt.
- The shamt field is used only for shifts.

Load and store instruction:

- Instruction format for load (opcode = 35_{10}) and store (opcode = 43_{10}) instructions.
- The register rs is the base register that is added to the 16-bit address field to form the memory address.
- For loads, rt is the destination register for the loaded value.
- For stores, rt is the source register whose value should be stored into memory.


Branch instruction:

- Instruction format for branch equal (opcode = 4).
- The registers rs and rt are the source registers that are compared for equality.
- The 16-bit address field is sign-extended, shifted, and added to the PC + 4 to compute the branch target address.

There are several major observations about this instruction format that we will rely on:

- The op field is always contained in bits 31:26.
- The two registers to be read are always specified by the rs and rt fields, at positions 25:21 and 20:16. This is true for the R-type instructions, branch equal, and store.
- The base register for load and store instructions is always in bit positions 25:21 (rs).

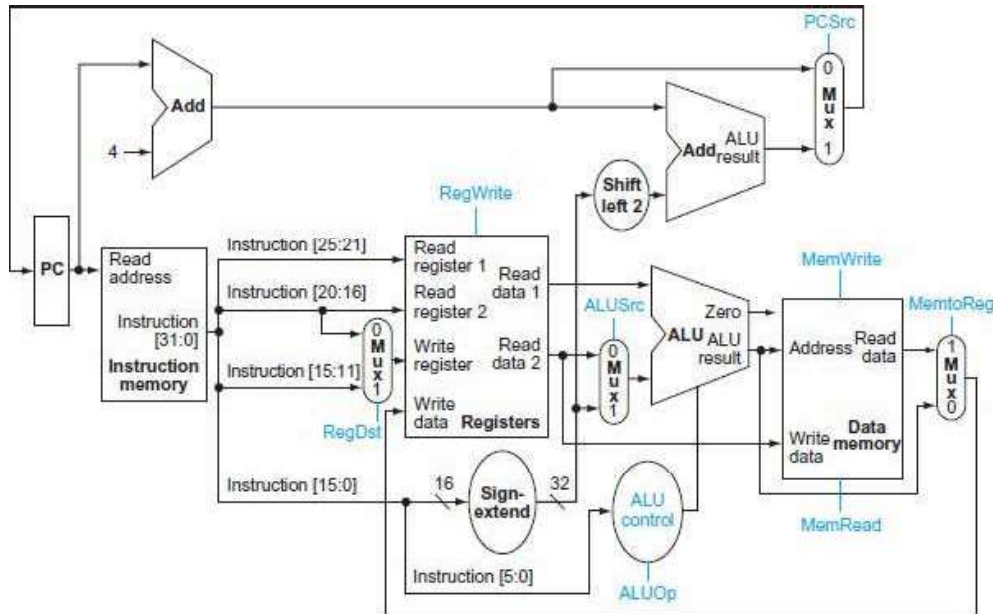- The 16-bit off set for branch equal, load, and store is always in positions 15:0.
- The destination register is in one of two places. For a load it is in bit positions 20:16 (rt), while for an R-type instruction it is in bit positions 15:11 (rd). Thus, we will need to add a multiplexor to select which field of the instruction is used to indicate the register number to be written.




Simple data path with multiplexors and control lines

Control signals:

- The following table shows the effect of each of the seven control signals when asserted and deasserted.


Signal name	Effect when deasserted	Effect when asserted
RegDst	The register destination number for the Write register comes from the rt field (bits 20:16).	The register destination number for the Write register comes from the rd field (bits 15:11).
RegWrite	None.	The register on the Write register input is written with the value on the Write data input.
ALUSrc	The second ALU operand comes from the second register file output (Read data 2).	The second ALU operand is the sign-extended, lower 16 bits of the instruction.
PCSrc	The PC is replaced by the output of the adder that computes the value of PC + 4.	The PC is replaced by the output of the adder that computes the branch target.
MemRead	None.	Data memory contents designated by the address input are put on the Read data output.
MemWrite	None.	Data memory contents designated by the address input are replaced by the value on the Write data input.
MemtoReg	The value fed to the register Write data input comes from the ALU.	The value fed to the register Write data input comes from the data memory.

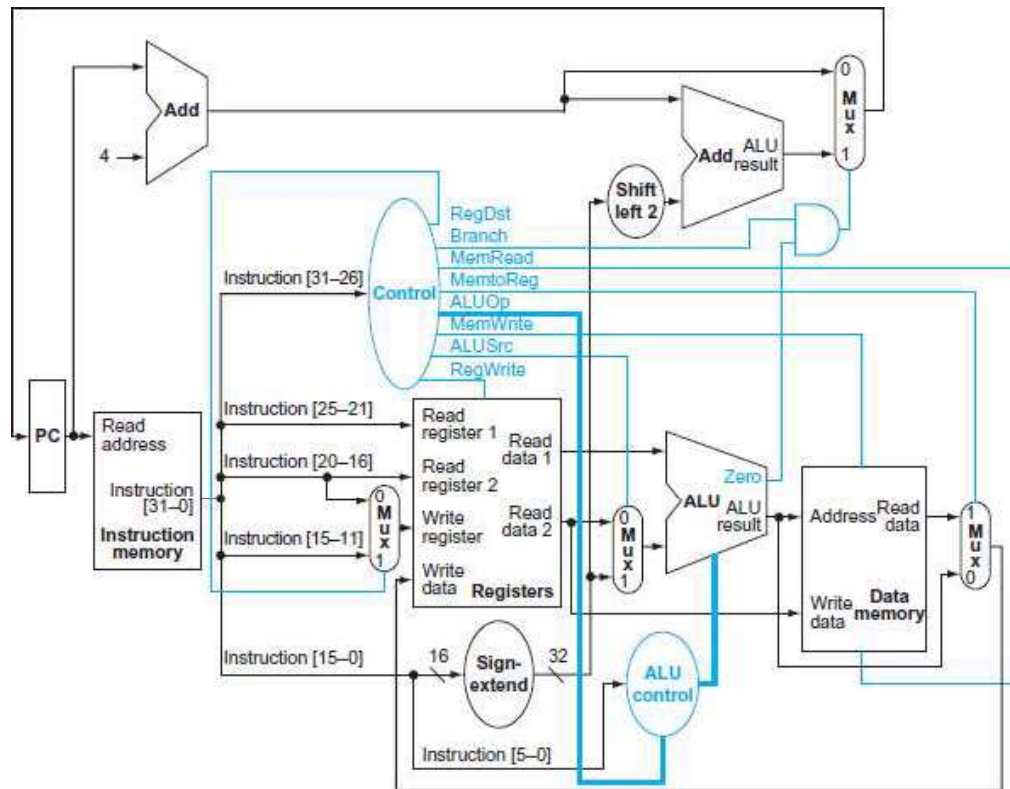


The simple data path with control unit

PIPELINING:

- Pipelining is an implementation technique in which multiple instructions are overlapped in execution. It exploits parallelism among the instructions in a sequential instruction stream. It has an important advantage that is basically invisible to the programmer.
- Pipelining increases the number of simultaneously executing instructions and the rate at which instructions are started and completed. Pipelining does not reduce the time it takes to complete an individual instruction.
- It improves the instruction throughput rather than individual instruction execution time or latency.
- The concept of pipelining can be understood by Laundry analogy. The non-pipelined approach to laundry would be as follows:
 - Place one dirty load of clothes in the washer.
 - When the washer is finished, place the wet load in the dryer
 - When the dryer is finished, place the dry load on a table and fold.
 - When folding is finished, ask your roommate to put the clothes away.
- When your roommate is done, start over with the next dirty load.
- The pipelined approach takes much less time, as Figure shows. As soon as the washer is finished with the first load and placed in the dryer, you load the washer with the second dirty load.
- When the first load is dry, you place it on the table to start folding, move the wet load to the dryer, and put the next dirty load into the washer.
- Next you have your roommate put the first load away, you start folding the second load, the dryer has the third load, and you put the fourth load into the washer.
- At this point all steps—called stages in pipelining—are operating concurrently. As long as we have separate resources for each stage, we can pipeline the tasks.

 


- Pipelining improves throughput of our laundry system. Hence, pipelining would not decrease the time to complete one load of laundry, but when we have many loads of laundry to do, the improvement in throughput decreases the total time to complete the work.
- The washer, dryer, “folder,” and “storer” each take 30 minutes for their task. Sequential laundry takes 8 hours for 4 loads of wash, while pipelined laundry takes just 3.5 hours.
- The same principles apply to processors where we pipeline instruction-execution. MIPS instructions classically take five steps:
 1. Fetch instruction from memory.
 2. Read registers while decoding the instruction. The regular format of MIPS instructions allows reading and decoding to occur simultaneously.
 3. Execute the operation or calculate an address.
 4. Access an operand in data memory.
 5. Write the result into a register.

 

Single-cycle, nonpipelined execution in top versus pipelined execution in bottom.

PIPELINED DATA PATH AND CONTROL


- Figure shows the single-cycle data path with the pipeline stages identified. The division of an instruction into five stages means a five-stage pipeline, which in turn means that up to five instructions will be in execution during any single clock cycle. Thus, we must separate the data path into five pieces, with each piece named corresponding to a stage of instruction execution:
 1. IF: Instruction fetch
 2. ID: Instruction decode and register file read
 3. EX: Execution or address calculation
 4. MEM: Data memory access
 5. WB: Write back
- Instructions and data move generally from left to right through the five stages as they complete execution. There are, however, two exceptions to this left-to-right flow of instructions:
 - The write-back stage, which places the result back into the register file in the middle of the data path
 - The selection of the next value of the PC, choosing between the incremented PC and the branch address from the MEM stage.

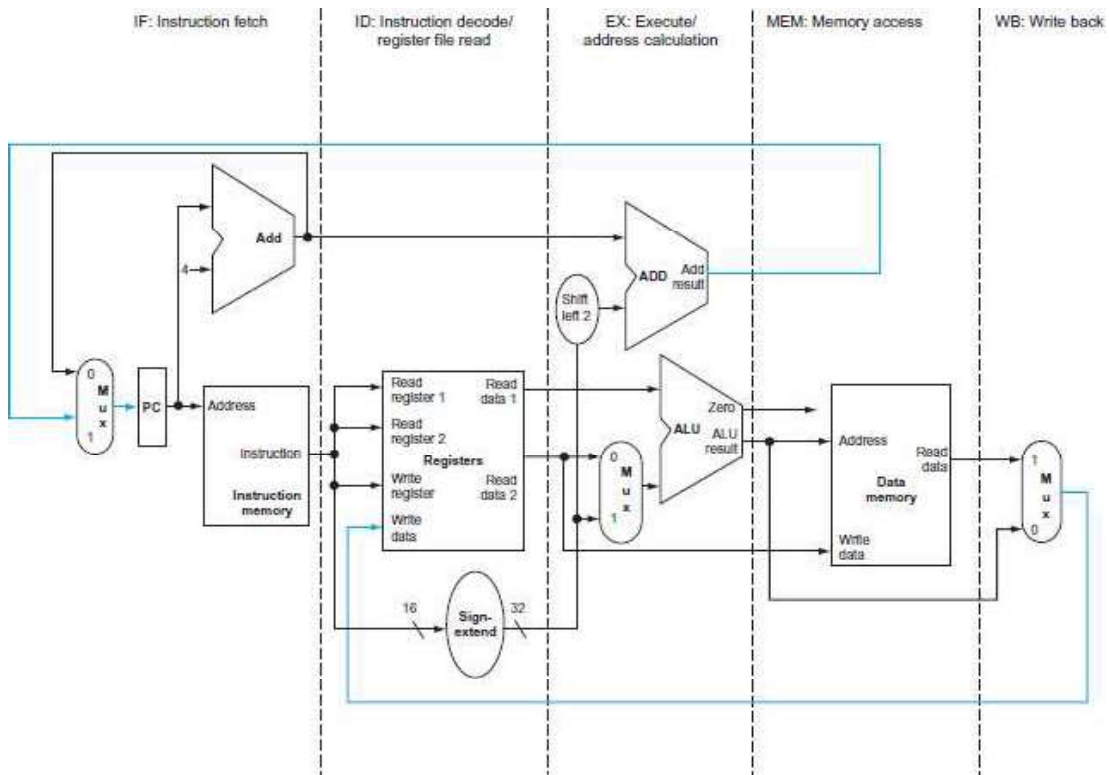

Single cycle data path with pipeline stages

Pipelined data path:

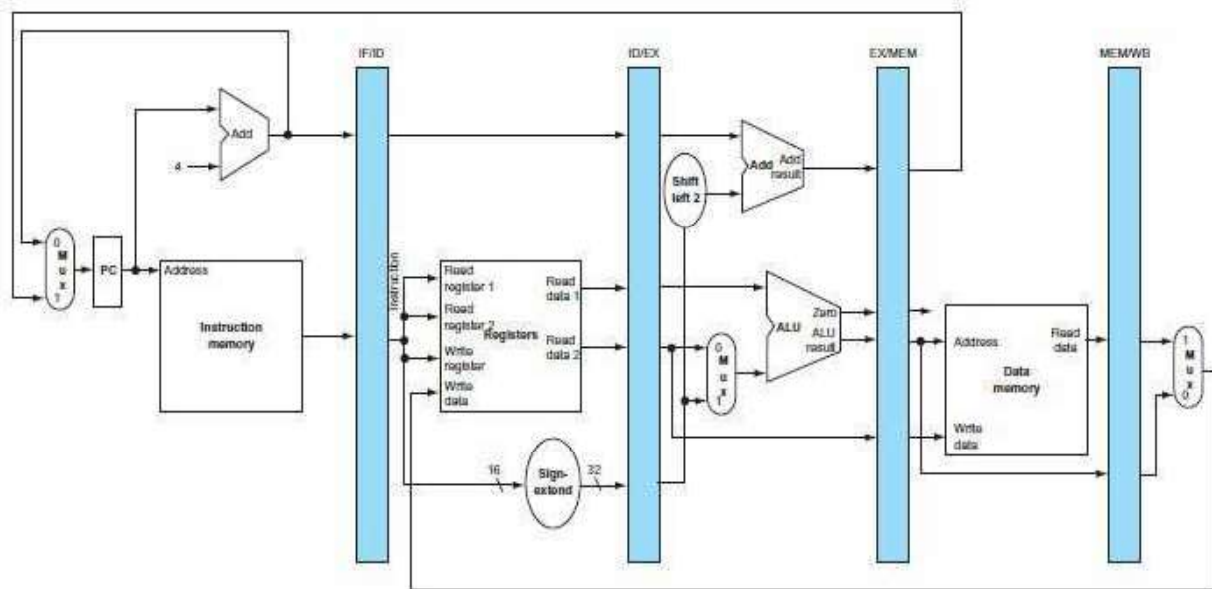- Figure 4.35 shows the pipelined data path with the pipeline registers highlighted. All instructions advance during each clock cycle from one pipeline register to the next. The registers are named for the two stages separated by that register. For example, the pipeline register between the IF and ID stages is called IF/ID. There is no pipeline register at the end of the write-back stage.



Pipelined data path

- The pipeline registers, separate each pipeline stage. They are labelled by the stages that they separate; for example, the first is labelled IF/ID because it separates the instruction fetch and instructions decode stages.
- The registers must be wide enough to store all the data corresponding to the lines that go through them.
- For example, the IF/ID register must be 64 bits wide, because it must hold both the 32-bit instruction fetched from memory and the incremented 32-bit PC address.

Five stages of load instruction:


- The five stages of load instruction are the following:
 - 1. Instruction fetch:**
 - The instruction is read from memory using the address in the PC and then being placed in the IF/ID pipeline register.
 - The PC address is incremented by 4 and then written back into the PC to be ready for the next clock cycle. This incremented address is also saved in the IF/ID pipeline register in case it is needed later for an instruction, such as beq.
 - The computer cannot know which type of instruction is being fetched, so it must prepare for any instruction, passing potentially needed information down the pipeline.
 - 2. Instruction decode and register file read:**
 - The IF/ID pipeline register supplying the 16-bit immediate field, which is sign-extended to 32 bits, and the register numbers to read the two registers.
 - All three values are stored in the ID/EX pipeline register, along with the incremented PC address.
 - 3. Execute or address calculation:**
 - The load instruction reads the contents of register 1 and the sign-extended immediate from the ID/EX pipeline register and adds them using the ALU.
 - That sum is placed in the EX/MEM pipeline register.

4. Memory access:

- The load instruction reading the data memory using the address from the EX/MEM pipeline register and loading the data into the MEM/WB pipeline register.

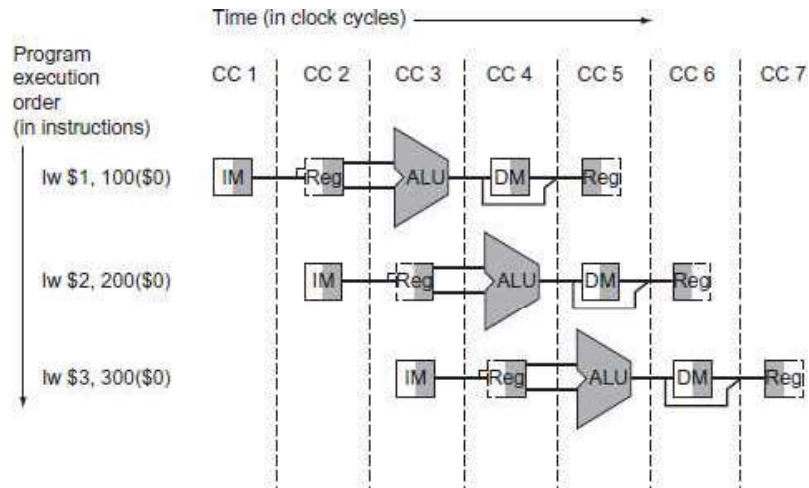5. Write-back:

- The final step is reading the data from the MEM/WB pipeline register and writing it into the register file in the middle of the figure.



Five stages of store instruction:

1. Instruction fetch:

- The instruction is read from memory using the address in the PC and then is placed in the IF/ID pipeline register. This stage occurs before the instruction is identified.

2. Instruction decode and register file read:

- The instruction in the IF/ID pipeline register supplies the register numbers for reading two registers and extends the sign of the 16-bit immediate. These three 32-bit values are all stored in the ID/EX pipeline register.

3. Execute and address calculation:

- In the third step, the effective address is placed in the EX/MEM pipeline register.

4. Memory access:

- The data being written to memory. Note that the register containing the data to be stored was read in an earlier stage and stored in ID/EX.
- The only way to make the data available during the MEM stage is to place the data into the EX/MEM pipeline register in the EX stage, just as we stored the effective address into EX/MEM.

5. Write-back:

- For this instruction, nothing happens in the write-back stage. Since every instruction behind the store is already in progress, we have no way to accelerate those instructions.

Graphically Representing Pipelines

- Pipelining can be difficult to understand, since many instructions are simultaneously executing in a single data path in every clock cycle. To aid understanding, there are two basic styles of pipeline figures: multiple-clock-cycle pipeline diagrams.

- For example, consider the following five-instruction sequence:

lw \$10, 20(\$1)


sub \$11, \$2, \$3

add \$12, \$3, \$4


lw \$13, 24(\$1)

add \$14, \$5, \$6

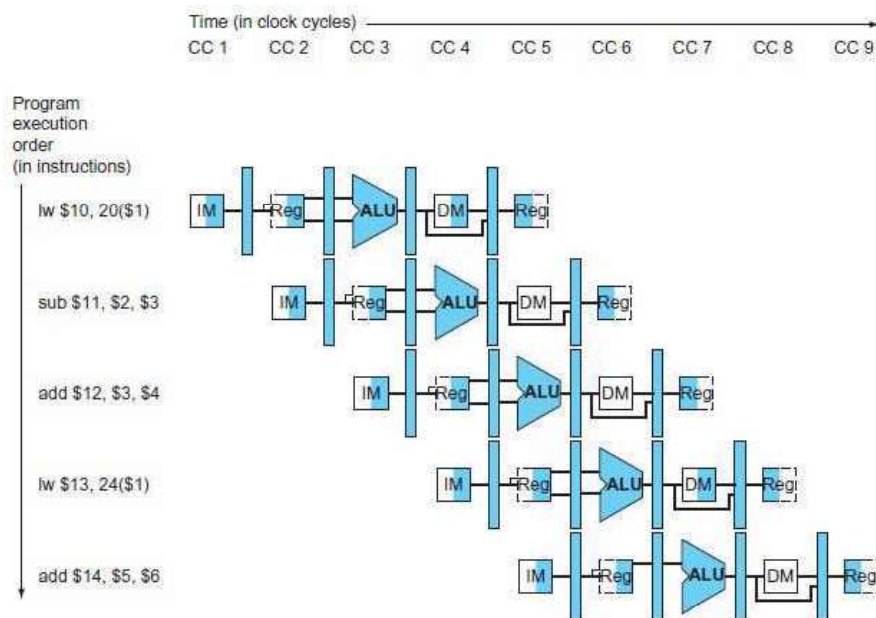- Figure shows the multiple-clock-cycle pipeline diagram for these instructions. Time advances from left to right across the page in these diagrams, and instructions advance from the top to the bottom of the page.



Multiple clock cycle pipeline diagrams

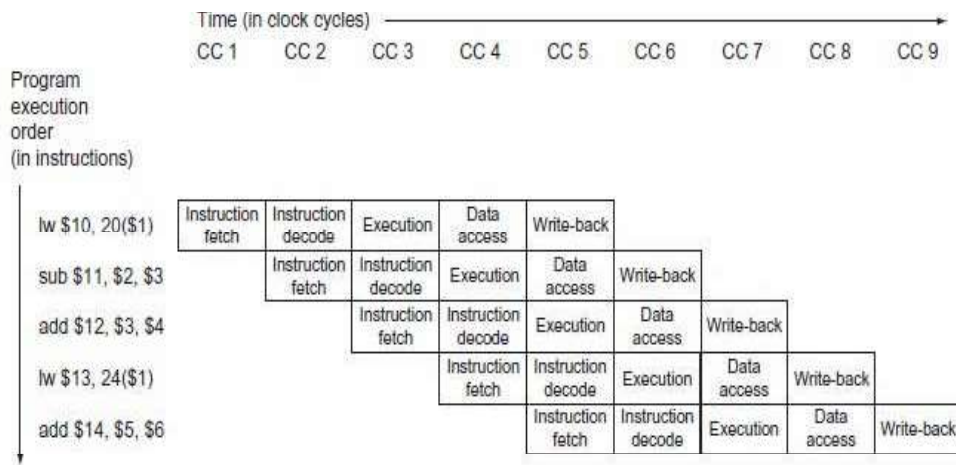

Traditional multiple-clock-cycle pipeline diagram of five instructions


HANDLING DATA HAZARDS AND CONTROL HAZARDS:

Pipeline Hazards

- There are situations in pipelining when the next instruction cannot execute in the following clock cycle. These events are called hazards, and there are three different types.
 - Structural hazard
 - Data hazard
 - Control hazard

Structural hazard:

- The first hazard is called a structural hazard. It means that the hardware cannot support the combination of instructions that we want to execute in the same clock cycle.
- The MIPS instruction set was designed to be pipelined, making it fairly easy for designers to avoid structural hazards when designing a pipeline. Suppose, however, that we had a single memory instead of two memories.
- If the pipeline in Figure had a fourth instruction, we would see that in the same clock cycle the first instruction is accessing data from memory while the fourth instruction is fetching an instruction from that same memory. Without two memories, our pipeline could have a structural hazard.

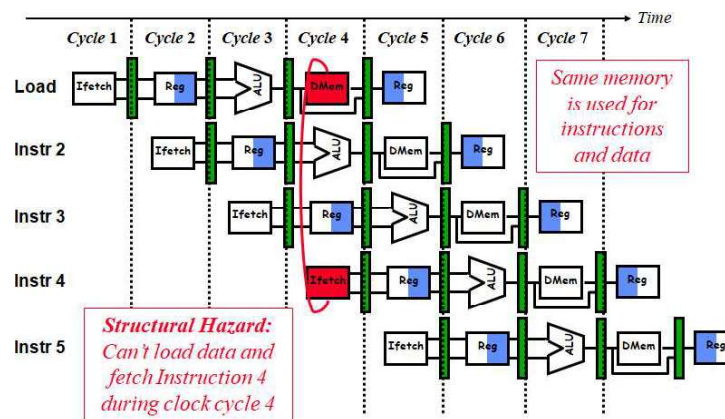


Data hazard:

- Data hazards occur when the pipeline must be stalled because one step must wait for another to complete. When a planned instruction cannot execute in the proper clock cycle because data that is needed to execute the instruction is not yet available.
- In a computer pipeline, data hazards arise from the dependence of one instruction on an earlier one that is still in the pipeline (a relationship that does not really exist when doing laundry). For example, suppose we have an add instruction followed immediately by a subtract instruction that uses the sum (\$s0):

add \$s0, \$t0, \$t1

sub \$t2, \$s0, \$t3

 


Graphical representation of the instruction pipeline


- In the above example, a data hazard could severely stall the pipeline. The add instruction doesn't write its result until the fifth stage, meaning that we would have to waste three clock cycles in the pipeline.
- There are some solutions to rectify data hazard. They are
 - Forwarding or Bypassing
 - Hazard detection unit
 - Reordering code to avoid pipeline stalls
 - Hazard detection by software

Forwarding or Bypassing:

- The primary solution is based on the observation that we don't need to wait for the instruction to complete before trying to resolve the data hazard.
- For the code sequence above, as soon as the ALU creates the sum for the add, we can supply it as an input for the subtract.
- Adding extra hardware to retrieve the missing item early from the internal resources is called **forwarding** or **bypassing**.

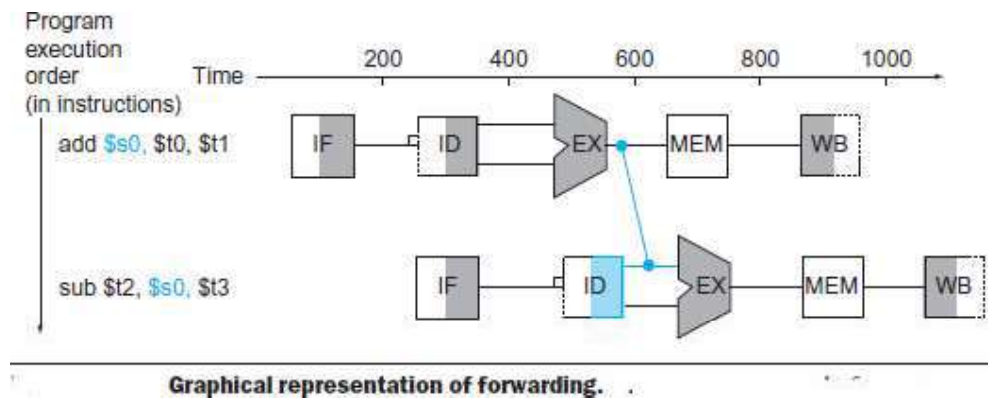

- The connection shows the forwarding path from the output of the EX stage of add to the input of the EX stage for sub, replacing the value from register \$s0 read in the second stage of sub.
- Forwarding works very well but cannot prevent all pipeline stalls, however. For example, suppose the first instruction was a load of \$s0 instead of an add. The desired data would be available only after the fourth stage of the first instruction in the dependence, which is too late for the input of the third stage of sub. Hence, even with forwarding, we would have to stall one stage for a **load-use data hazard**.
- It is a specific form of data hazard in which the data being loaded by a load instruction has not yet become available when it is needed by another instruction.

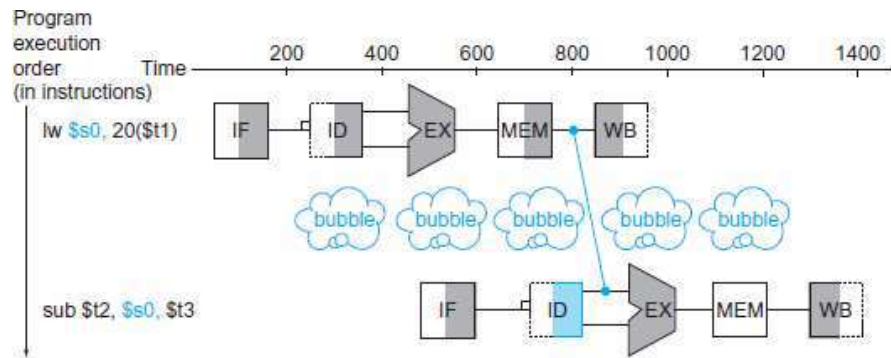

Stall even with forwarding

- Figure shows that we need a stall even with forwarding when an R-format instruction following a load tries to use the data. Without the stall, the path from memory access stage output to execution stage input would be going backward in time, which is impossible.
- This figure shows an important pipeline concept, officially called a **pipeline stall**, but often given the nickname **bubble**.

Data Hazards: Forwarding versus Stalling


- Data hazards arise when an instruction depends on the results of a previous instruction in a way that is exposed by the overlapping of instructions in the pipeline.
- Consider the following instructions:

```

sub $2, $1,$3      # Register $2 written by sub
and $12,$2,$5     # 1st operand($2) depends on sub
or $13,$6,$2      # 2nd operand($2) depends on sub
add $14,$2,$2     # 1st($2) & 2nd($2) depend on sub
sw $15,100($2)    # Base ($2) depends on sub

```

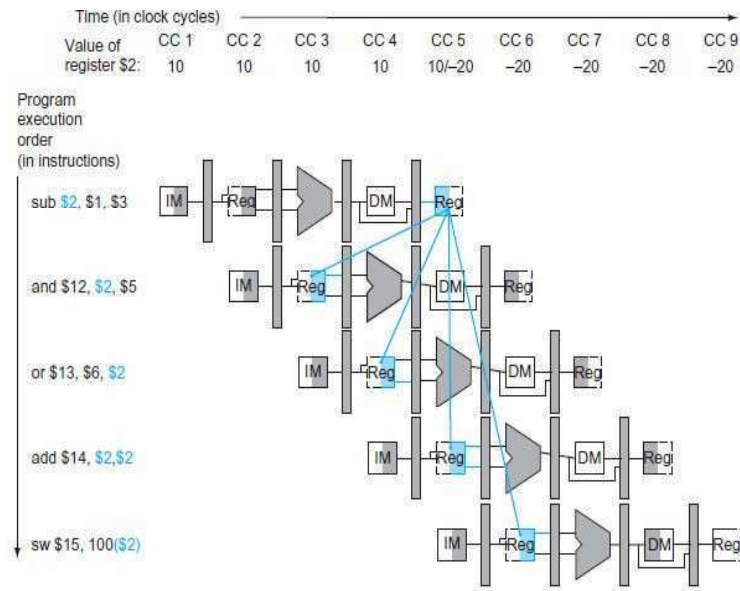- The last four instructions are all dependent on the result in register \$2 of the first instruction. If register \$2 had the value 10 before the subtract instruction and -20 afterwards, the programmer intends that -20 will be used in the following instructions that refer to register \$2.
- Fig. Illustrates the execution of these instructions using a multiple clock cycle pipeline representation.




- In figure, the data from the sub instruction actually produced at the end of the EX stage or clock cycle 3. The data actually needed by the and & or instruction is the beginning of the EX stage, or clock cycles 4 & 5 respectively.
- Thus, we can execute this segment without stalls if we simply forward the data as soon as it is available to any units that need it before it is available to read from the register file.
- Data forwarding is effective to an operation in the EX stage, which may be either an ALU operation or an effective address calculation.
- This means that when an instruction tries to use a register in its EX stage that an earlier instruction intends to write in its WB stage. We actually need the values as inputs to the ALU.
- Using this notation, the two pairs of hazard conditions are

1a. $EX/MEM.RegisterRd = ID/EX.RegisterRs$

1b. $EX/MEM.RegisterRd = ID/EX.RegisterRt$

2a. $MEM/WB.RegisterRd = ID/EX.RegisterRs$

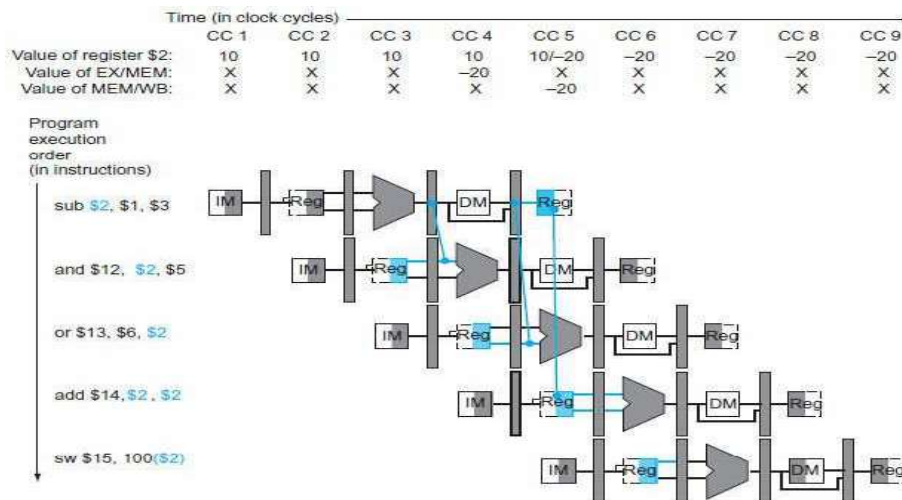2b. $MEM/WB.RegisterRd = ID/EX.RegisterRt$



Data forwarding to avoid stalls

- Let's now write both the conditions for detecting hazards and the control signals to resolve them:

1. EX hazard:

if (EX/MEM.RegWrite

and (EX/MEM.RegisterRd \neq 0)

and (EX/MEM.RegisterRd = ID/EX.RegisterRs)) ForwardA = 10

if (EX/MEM.RegWrite

and (EX/MEM.RegisterRd \neq 0)

and (EX/MEM.RegisterRd = ID/EX.RegisterRt)) ForwardB = 10

2. MEM hazard:

if (MEM/WB.RegWrite

and (MEM/WB.RegisterRd \neq 0)


and (MEM/WB.RegisterRd = ID/EX.RegisterRs)) ForwardA = 01

if (MEM/WB.RegWrite

and (MEM/WB.RegisterRd \neq 0)

and (MEM/WB.RegisterRd = ID/EX.RegisterRt)) ForwardB = 01

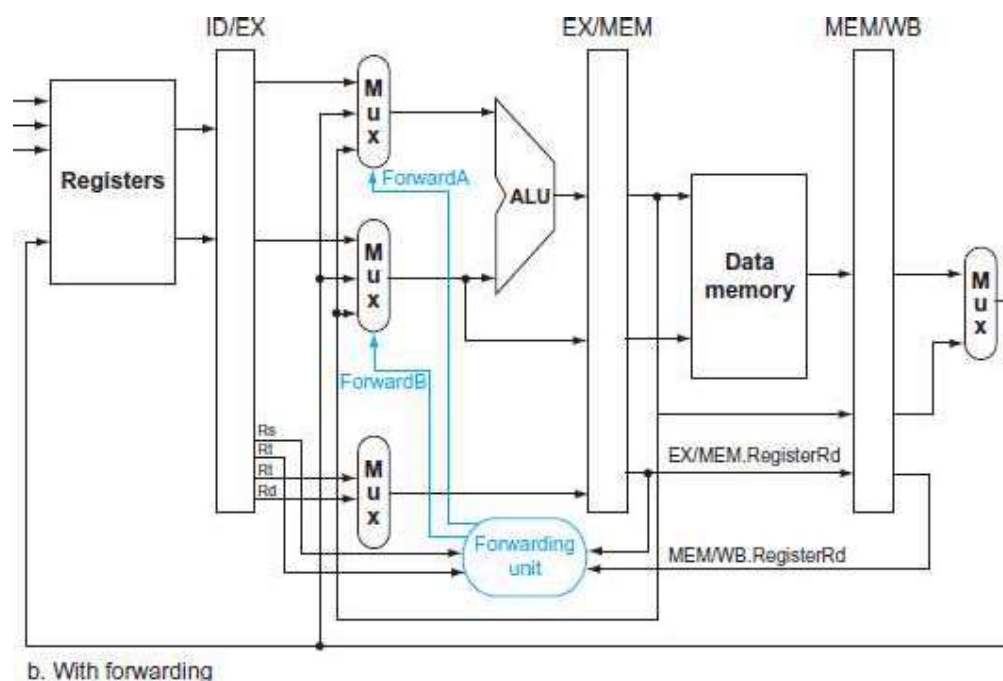- As mentioned above, there is no hazard in the WB stage, because we assume that the register file supplies the correct result if the instruction in the ID stage reads the same register written by the instruction in the WB stage. Such a register file performs another form of forwarding, but it occurs within the register file.




Mux control	Source	Explanation
ForwardA = 00	ID/EX	The first ALU operand comes from the register file.
ForwardA = 10	EX/MEM	The first ALU operand is forwarded from the prior ALU result.
ForwardA = 01	MEM/WB	The first ALU operand is forwarded from data memory or an earlier ALU result.
ForwardB = 00	ID/EX	The second ALU operand comes from the register file.
ForwardB = 10	EX/MEM	The second ALU operand is forwarded from the prior ALU result.
ForwardB = 01	MEM/WB	The second ALU operand is forwarded from data memory or an earlier ALU result.

The control values for the forwarding multiplexors


Data Hazards and Stalls:

- The dependence between the load and the following instruction (and) goes backward in time, this hazard cannot be solved by forwarding. Hence, this combination must result in a stall by the hazard detection unit. It operates during the ID stage so that it can insert the stall between the load and its use. Checking for load instructions, the control for the hazard detection unit is this single condition:

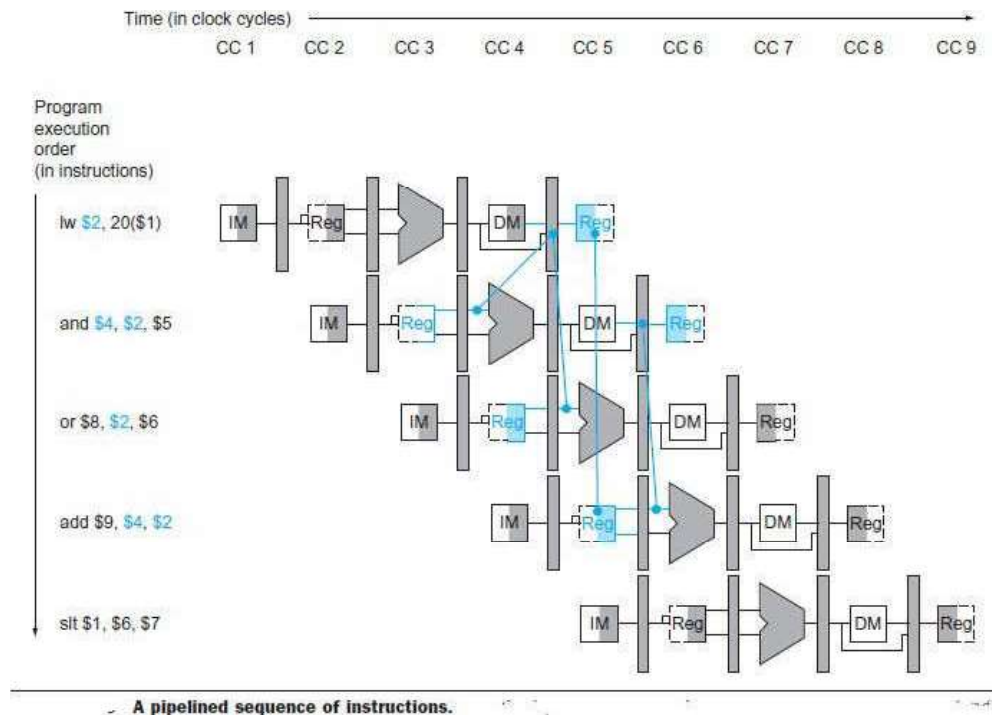
if (ID/EX.MemRead and
 ((ID/EX.RegisterRt = IF/ID.RegisterRs) or
 (ID/EX.RegisterRt = IF/ID.RegisterRt)))
 stall the pipeline



- If the instruction in the ID stage is stalled, then the instruction in the IF stage must also be stalled, otherwise we would lose the fetched instruction. Below figure highlights the pipeline connections for both the hazard detection unit and the forwarding unit.
- The forwarding unit controls the ALU multipliers to replace the value from a general-purpose register with the value nop instruction.
- By identifying the hazard in the ID stage, we can insert a bubble into the pipeline by changing the EX, MEM and WB control fields of the ID/EX pipeline register to 0.

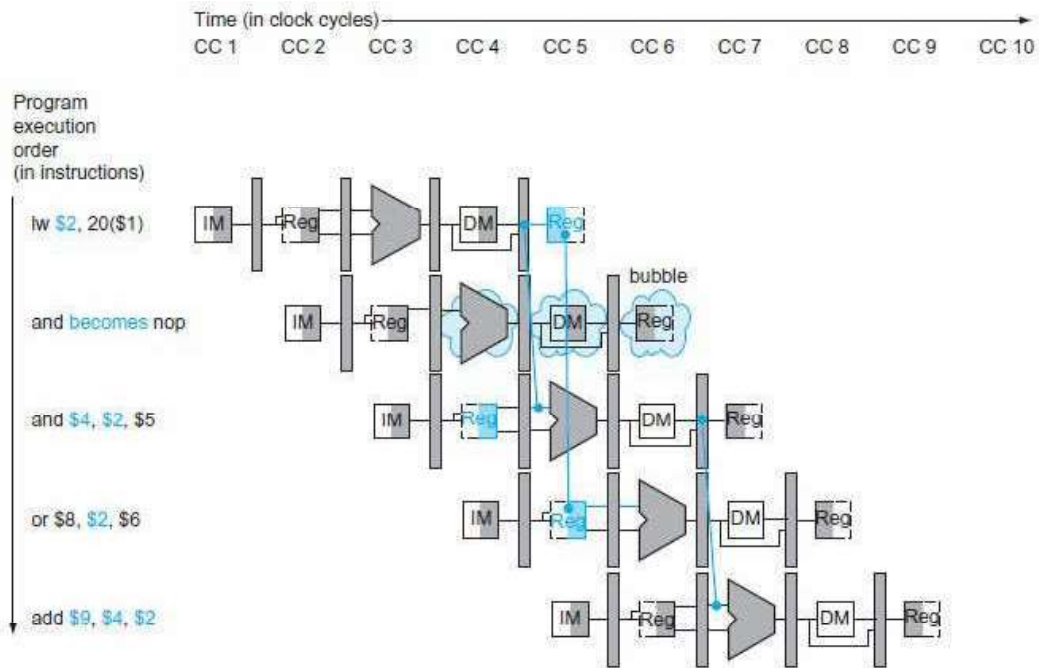

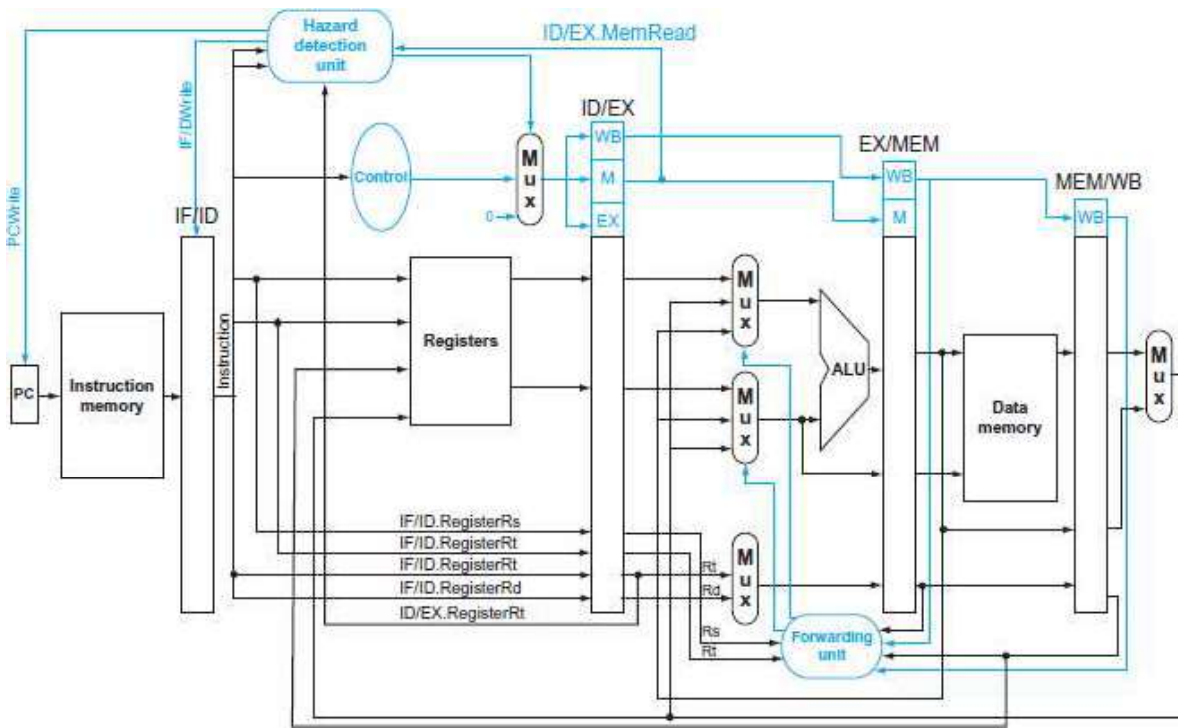The way stalls are really inserted into the pipeline




The hazard detection unit

- Figure highlights the pipeline connections for both the hazard detection unit and the forwarding unit. As before, the forwarding unit controls the ALU multiplexors to replace the value from a general-purpose register with the value from the proper pipeline register. The hazard detection unit controls the writing of the PC and IF/ID registers plus the multiplexor that chooses between the real control values and all 0s.

Control hazard:

- Control hazard is also called branch hazard. When the proper instruction cannot execute in the proper pipeline clock cycle because the instruction that was fetched is not the one that is needed; that is, the flow of instruction addresses is not what the pipeline expected.
- Fig. shows a sequence of instructions and indicates when the branch would occur in this pipeline. An instruction must be fetched at every clock cycle to sustain the pipeline, yet in our design the decision about whether to branch doesn't occur until the MEM pipeline stage. This delay in determining the proper instruction to fetch is called a control hazard or branch hazard.

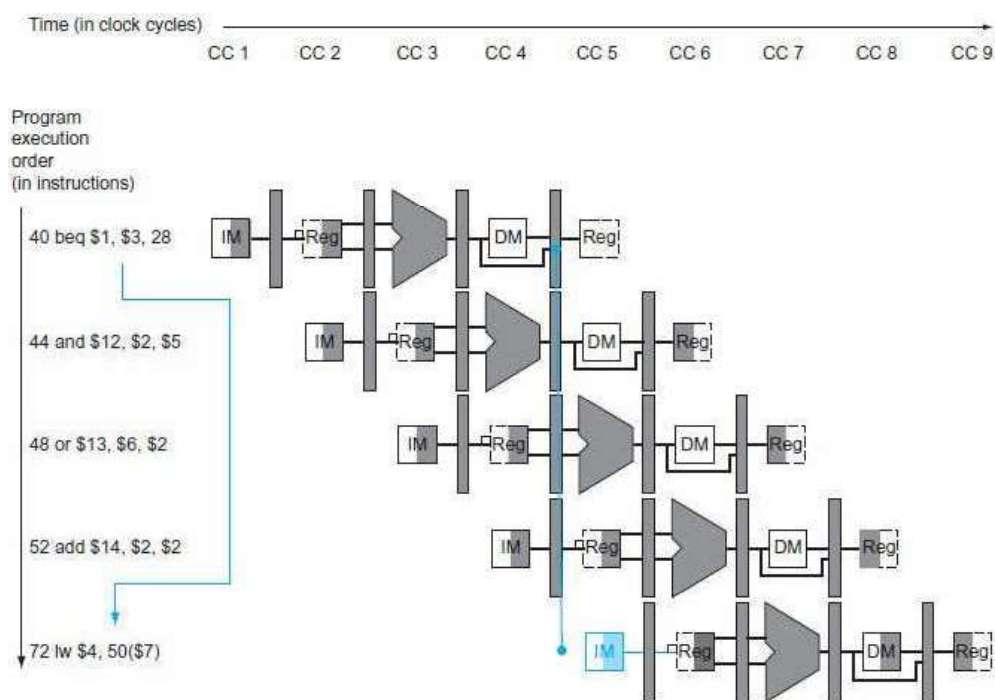


The impact of the pipeline on the branch instruction


- This section on control hazards is shorter than the previous sections on data hazards. The reasons are that
 - control hazards are relatively simple to understand,
 - they occur less frequently than data hazards,
 - There is nothing as effective against control hazards as forwarding is against data hazards. Hence, we use simpler schemes.

Assume Branch Not Taken:

- A common improvement over branch stalling is to assume that the branch will not be taken and thus continue execution down the sequential instruction stream.
- If the branch is taken, the instructions that are being fetched and decoded must be discarded. Execution continues at the branch target.
- If branches are untaken half the time, and if it costs little to discard the instructions, the optimization halves the cost of control hazards.
- To discard instructions, we merely change the original control values to 0s. Discarding the instructions in the pipeline is called as flushing.

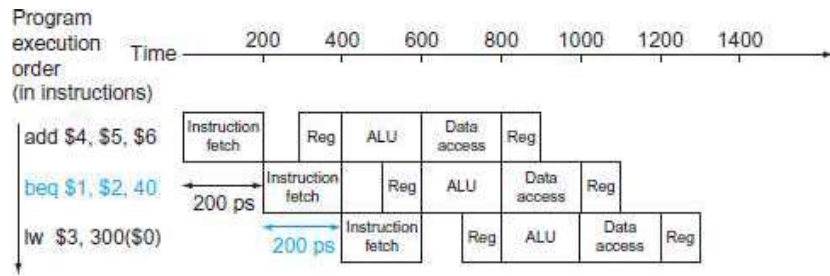

Pipelining that branches are not taken

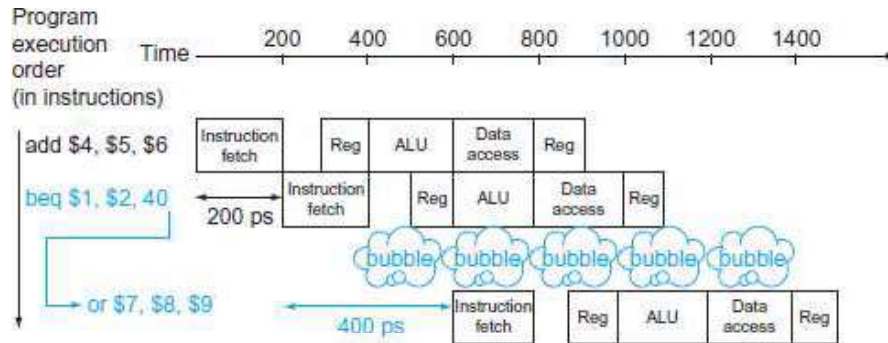

Pipelining that branch is taken

EXCEPTIONS:

- Exceptions are also called **interrupt**. It is an unscheduled event that disrupts program execution; used to detect overflow. Events other than branches or jumps that change the normal flow of instruction execution come under exception.
- They were initially created to handle unexpected events from within the processor, like arithmetic overflow.
- In MIPS convention, the term exception to refer to any unexpected change in control flow without distinguishing whether the cause is internal or external; we use the term interrupt only when the event is externally caused.
- Here are five examples showing whether the situation is internally generated by the processor or externally generated:

Type of event	From where?	MIPS terminology
I/O device request	External	Interrupt
Invoke the operating system from user program	Internal	Exception
Arithmetic overflow	Internal	Exception
Using an undefined instruction	Internal	Exception
Hardware malfunctions	Either	Exception or interrupt

- Detecting exceptional conditions and taking the appropriate action is often on the critical timing path of a processor, which determines the clock cycle time and thus performance.

Exceptions handling in MIPS architecture:


- The two types of exceptions that our current implementation can generate are execution of an **undefined instruction** and an **arithmetic overflow**. The basic action that the processor must perform when an exception occurs is to save the address of the off ending instruction in the exception program counter (EPC) and then transfer control to the operating system at some specified address.
- The operating system can then take the appropriate action, which may involve providing some service to the user program, taking some predefined action in response to an overflow, or stopping the execution of the program and reporting an error.
- After performing whatever action is required because of the exception, the operating system can terminate the program or may continue its execution, using the EPC to determine where to restart the execution of the program.
- For the operating system to handle the exception, it must know the reason for the exception, in addition to the instruction that caused it. There are two main methods used to communicate the reason for an exception.
- **Status register (called the Cause register)** - which holds a field that indicates the reason for the exception.
- **Vectored interrupts-** In a vectored interrupt; the address to which control is transferred is determined by the cause of the exception.
- For example, to accommodate the two exception types listed above, we might define the following two exception vector addresses:

Exception type	Exception vector address (in hex)
Undefined instruction	8000 0000 _{hex}
Arithmetic overflow	8000 0180 _{hex}

- The operating system knows the reason for the exception by the address at which it is initiated. When the exception is not vectored, a single entry point for all exceptions can be used, and the operating system decodes the status register to find the cause.
- We can implement exception handling by adding the following two additional registers to our simple MIPS implementation:
 - **EPC:** A 32-bit register used to hold the address of the affected instruction.
 - **Cause:** A register used to record the cause of the exception. It is also this 32 bits wide.

MEMORY HIERARCHY:

- An ideal memory would be fast, large, and inexpensive. It is clear that a very fast memory can be implemented using static RAM chips. But, these chips are not suitable for implementing large memories, because their basic cells are larger and consume more power than dynamic RAM cells.
- Although dynamic memory units with gigabyte capacities can be implemented at a reasonable cost, the affordable size is still small compared to the demands of large programs with voluminous data.
- A solution is provided by using secondary storage, mainly magnetic disks, to provide the required memory space. Disks are available at a reasonable cost, and they are used extensively in computer systems. However, they are much slower than semiconductor memory units.
- In summary, a very large amount of cost-effective storage can be provided by magnetic disks, and a large and considerably faster, yet affordable, main memory can be built with dynamic RAM technology. This leaves the more expensive and much faster static RAM technology to be used in smaller units where speed is of the essence, such as in cache memories.
- All of these different types of memory units are employed effectively in a computer system. The entire computer memory can be viewed as the hierarchy depicted in Figure The fastest access is to data held in processor registers. Therefore, if we consider the registers to be part of the memory hierarchy, then the processor registers are at the top in terms of speed of access. Of course, the registers provide only a minuscule portion of the required memory.

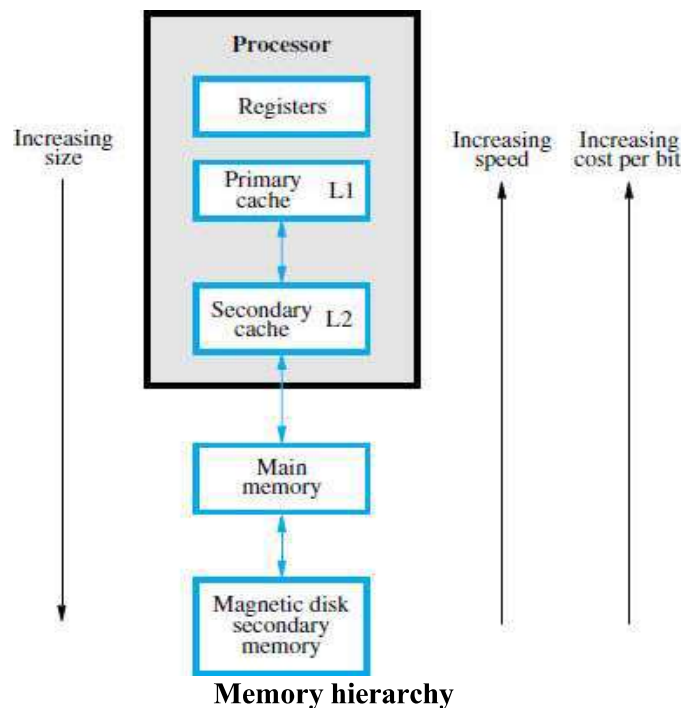

- At the next level of the hierarchy is a relatively small amount of memory that can be implemented directly on the processor chip. This memory, called a processor cache, holds copies of the instructions and data stored in a much larger memory that is provided externally.
- There are often two or more levels of cache. A primary cache is always located on the processor chip. This cache is small and its access time is comparable to that of processor registers. The primary cache is referred to as the level 1 (L1) cache. A larger, and hence somewhat slower, secondary cache is placed between the primary cache and the rest of the memory. It is referred to as the level 2 (L2) cache. Often, the L2 cache is also housed on the processor chip.
- Some computers have a level 3 (L3) cache of even larger size, in addition to the L1 and L2 caches. An L3 cache, also implemented in SRAM technology, may or may not be on the same chip with the processor and the L1 and L2 caches.
- The next level in the hierarchy is the main memory. This is a large memory implemented using dynamic memory components, typically assembled in memory modules such as DIMMs.
- The main memory is much larger but significantly slower than cache memories. In a computer with a processor clock of 2 GHz or higher, the access time for the main memory can be as much as 100 times longer than the access time for the L1 cache.
- Disk devices provide a very large amount of inexpensive memory, and they are widely used as secondary storage in computer systems. They are very slow compared to the main memory. They represent the bottom level in the memory hierarchy.
- If the data requested by the processor appears in some block in the upper level, this is called a **hit**. If the data is not found in the upper level, the request is called a **miss**.
- The lower level in the hierarchy is then accessed to retrieve the block containing the requested data. The **hit rate, or hit ratio, is the fraction of memory accesses** found in the upper level; it is often used as a measure of the performance of the memory hierarchy.
- The **miss rate (1–hit rate) is the fraction of memory accesses** not found in the upper level.
- **Hit time is the time to access the upper level** of the memory hierarchy, which includes the time needed to determine whether the access is a hit or a miss (that is, the time needed to look through the books on the desk).
- **Miss penalty: The time** required to fetch a block into a level of the memory hierarchy from the lower level, including the time to access the block, transmit it from one level to the other, insert it in the level that experienced the miss, and then pass the block to the requestor.

MEMORY TECHNOLOGIES:

- There are four primary technologies used today in memory hierarchies. Main memory is implemented from DRAM (dynamic random access memory), while levels closer to the processor (caches) use SRAM (static random access memory).
- DRAM is less costly per bit than SRAM, although it is substantially slower. The price difference arises because DRAM uses significantly less area per bit of memory, and DRAMs thus have larger capacity for the same amount of silicon.
- The third technology is flash memory. This nonvolatile memory is the secondary memory in Personal Mobile Devices.
- The fourth technology, used to implement the largest and slowest level in the hierarchy in servers, is magnetic disk. The access time and price per bit vary widely among these technologies, as the table below shows, using typical values for 2012:

Memory technology	Typical access time	\$ per GiB in 2012
SRAM semiconductor memory	0.5–2.5 ns	\$500–\$1000
DRAM semiconductor memory	50–70 ns	\$10–\$20
Flash semiconductor memory	5,000–50,000 ns	\$0.75–\$1.00
Magnetic disk	5,000,000–20,000,000 ns	\$0.05–\$0.10

SRAM Technology


- SRAMs are simply integrated circuits that are memory arrays with (usually) a single access port that can provide either a read or a write.
- SRAMs have a fixed access time to any datum, though the read and write access times may differ.
- SRAMs don't need to refresh and so the access time is very close to the cycle time. SRAMs typically use six to eight transistors per bit to prevent the information from being disturbed when read.
- SRAM needs only minimal power to retain the charge in standby mode.
- Memories that consist of circuits capable of retaining their state as long as power is applied are known as static memories.
- Figure illustrates how a static RAM (SRAM) cell may be implemented. Two inverters are cross-connected to form a latch. The latch is connected to two bit lines by transistors T_1 and T_2 . These transistors act as switches that can be opened or closed under control of the word line. When the word line is at ground level, the transistors are turned off and the latch retains its state.

Read Operation

- In order to read the state of the SRAM cell, the word line is activated to close switches T_1 and T_2 . If the cell is in state 1, the signal on bit line b is high and the signal on bit line b' is low. The opposite is true if the cell is in state 0. Thus, b and b' are always complements of each other. The Sense/Write circuit at the end of the two bit lines monitors their state and sets the corresponding output accordingly.

Write Operation

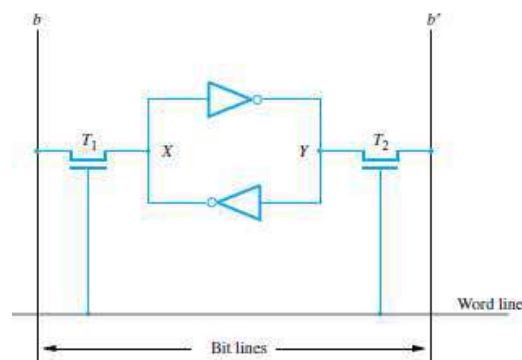
- During a Write operation, the Sense/Write circuit drives bit lines b and b' , instead of sensing their state. It places the appropriate value on bit line b and its complement on b' and activates the word line. This forces the cell into the corresponding state, which the cell retains when the word line is deactivated.



A static RAM cell

CMOS Cell

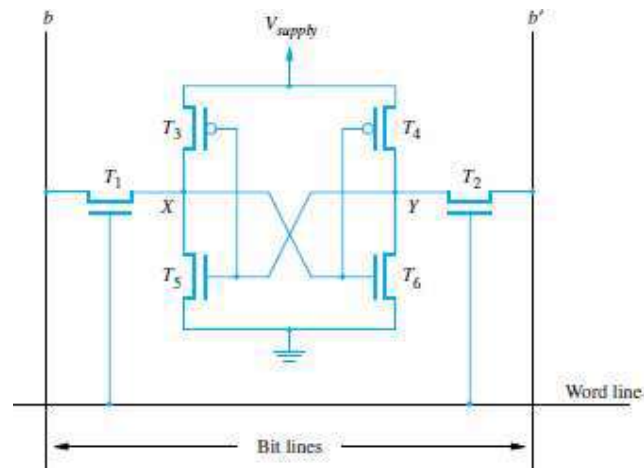
- Transistor pairs (T_3, T_5) and (T_4, T_6) form the inverters in the latch. The state of the cell is read or written as just explained. For example, in state 1, the voltage at point X is maintained high by having transistors T_3 and T_6 on, while T_4 and T_5 are off. If T_1 and T_2 are turned on, bit lines b and b' will have high and low signals, respectively.




An example of a CMOS memory cell

Dynamic RAM:

- Static RAMs are fast, but their cells require several transistors. Less expensive and higher density RAMs can be implemented with simpler cells. But, these simpler cells do not retain their state for a long period, unless they are accessed frequently for Read or Write operations. Memories that use such cells are called dynamic RAMs (DRAMs).
- Information is stored in a dynamic memory cell in the form of a charge on a capacitor, but this charge can be maintained for only tens of milliseconds. Since the cell is required to store information for a much longer time, its contents must be periodically refreshed by restoring the capacitor charge to its full value. This occurs when the contents of the cell are read or when new information is written into it.
- An example of a dynamic memory cell that consists of a capacitor, C , and a transistor, T , is shown in Figure. To store information in this cell, transistor T is turned on and an appropriate voltage is applied to the bit line. This causes a known amount of charge to be stored in the capacitor.
- After the transistor is turned off, the charge remains stored in the capacitor, but not for long. The capacitor begins to discharge.
- A single transistor is then used to access this stored charge, either to read the value or to overwrite the charge stored there. Because DRAMs use only a single transistor per bit of storage, they are much denser and cheaper per bit than SRAM.
- As DRAMs store the charge on a capacitor, it cannot be kept indefinitely and must periodically be refreshed.

 


- Figure shows the internal organization of a DRAM, Modern DRAMs are organized in banks, typically four for DDR3. Each bank consists of a series of rows.
- Sending a PRE (precharge) command opens or closes a bank. A row address is sent with an Act (activate), which causes the row to transfer to a buffer.
- When the row is in the buffer, it can be transferred by successive column addresses at whatever the width of the DRAM is (typically 4, 8, or 16 bits in DDR3) or by specifying a block transfer and the starting address.
- Each command, as well as block transfers, is synchronized with a clock.

 

ROM

- A memory is called a read-only memory, or ROM, when information can be written into it only once at the time of manufacture. Figure shows a possible configuration for a ROM cell. A logic value 0 is stored in the cell if the transistor is connected to ground at point *P*; otherwise, a 1 is stored.
- The bit line is connected through a resistor to the power supply. To read the state of the cell, the word line is activated to close the transistor switch. As a result, the voltage on the bit line drops to near zero if there is a connection between the transistor and ground.
- If there is no connection to ground, the bit line remains at the high voltage level, indicating a 1. A sense circuit at the end of the bit line generates the proper output value.
- The state of the connection to ground in each cell is determined when the chip is manufactured, using a mask with a pattern that represents the information to be stored.

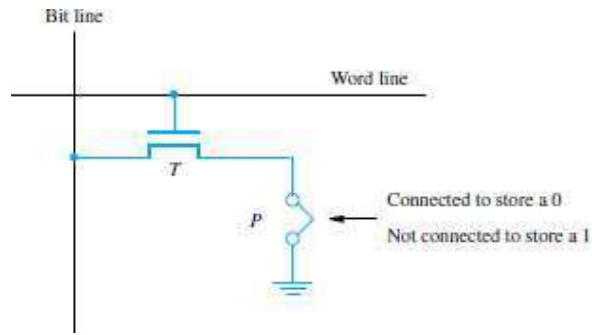

A ROM cell

PROM

- Some ROM designs allow the data to be loaded by the user, thus providing a programmable ROM (PROM). Programmability is achieved by inserting a fuse at point P in Figure. Before it is programmed, the memory contains all 0s. The user can insert 1s at the required locations by burning out the fuses at these locations using high-current pulses. Of course, this process is irreversible.
- PROMs provide flexibility and convenience not available with ROMs. The cost of preparing the masks needed for storing a particular information pattern makes ROMs cost effective only in large volumes. The alternative technology of PROMs provides a more convenient and considerably less expensive approach, because memory chips can be programmed directly by the user.

EPROM

- Another type of ROM chip provides an even higher level of convenience. It allows the stored data to be erased and new data to be written into it. Such an erasable, reprogrammable ROM is usually called an EPROM. It provides considerable flexibility during the development phase of digital systems. Since EPROMs are capable of retaining stored information for a long time, they can be used in place of ROMs or PROMs while software is being developed.
- In this way, memory changes and updates can be easily made. An EPROM cell has a structure similar to the ROM cell in Figure. However, the connection to ground at point P is made through a special transistor. The transistor is normally turned off, creating an open switch. It can be turned on by injecting charge into it that becomes trapped inside.
- Erasure requires dissipating the charge trapped in the transistors that form the memory cells. This can be done by exposing the chip to ultraviolet light, which erases the entire contents of the chip. To make this possible, EPROM chips are mounted in packages that have transparent windows.

EEPROM

- An EPROM must be physically removed from the circuit for reprogramming. Also, the stored information cannot be erased selectively. The entire contents of the chip are erased when exposed to ultraviolet light.
- Another type of erasable PROM can be programmed, erased, and reprogrammed electrically. Such a chip is called an electrically erasable PROM, or EEPROM. It does not have to be removed for erasure. Moreover, it is possible to erase the cell contents selectively.
- One disadvantage of EEPROMs is that different voltages are needed for erasing, writing, and reading the stored data, which increases circuit complexity. However, this disadvantage is outweighed by the many advantages of EEPROMs. They have replaced EPROMs in practice.


Flash Memory

- An approach similar to EEPROM technology has given rise to *flash memory* devices. A flash cell is based on a single transistor controlled by trapped charge, much like an EEPROM cell. Also like an EEPROM, it is possible to read the contents of a single cell.
- The key difference is that, in a flash device, it is only possible to write an entire block of cells. Prior to writing, the previous contents of the block are erased.
- Flash devices have greater density, which leads to higher capacity and a lower cost per bit. They require a single power supply voltage, and consume less power in their operation.
- The low power consumption of flash memories makes them attractive for use in portable, battery-powered equipment. Typical applications include hand-held computers, cell phones, digital cameras, and MP3 music players.
- In hand-held computers and cell phones, a flash memory holds the software needed to operate the equipment, thus obviating the need for a disk drive. A flash memory is used in digital cameras to store picture data.
- In MP3 players, flash memories store the data that represent sound. Cell phones, digital cameras, and MP3 players are good examples of embedded systems.
- Larger memory modules consisting of a number of chips are used where needed. There are two popular choices for the implementation of such modules: flash cards and flash drives

CACHE MEMORY:


- The cache is a small and very fast memory, interposed between the processor and the main memory. Its purpose is to make the main memory appear to the processor to be much faster than it actually is. The effectiveness of this approach is based on a property of computer programs called locality of reference.
- If programs are executed repeatedly during some time period, this behaviour manifests itself in two ways: temporal and spatial.
- Figure shows such a simple cache, before and after requesting a data item that is not initially in the cache. Before the request, the cache contains a collection of recent references X_1, X_2, \dots, X_{n-1} , and the processor requests a word X_n that is not in the cache. This request results in a miss, and the word X_n is brought from memory into the cache.
- If each word can go in exactly one place in the cache, then it is straightforward to find the word if it is in the cache. The simplest way to assign a location in the cache for each word in memory is to assign the cache location based on the address of the word in memory.
- This cache structure is called **direct mapped**, since each memory location is mapped directly to exactly one location in the cache. The typical mapping between addresses and cache locations for a direct mapped cache is usually simple.
- For example, almost all direct-mapped caches use this mapping to find a block:

 (Block address) modulo (Number of blocks in the cache)



The cache just before and just after a reference to a word X_n that is not initially in the cache

- Consider the arrangement in Figure. When the processor issues a Read request, the contents of a block of memory words containing the location specified are transferred into the cache. Subsequently, when the program references any of the locations in this block, the desired contents are read directly from the cache.
- Usually, the cache memory can store a reasonable number of blocks at any given time, but this number is small compared to the total number of blocks in the main memory. The correspondence between the main memory blocks and those in the cache is specified by a mapping function.
- When the cache is full and a memory word (instruction or data) that is not in the cache is referenced, the cache control hardware must decide which block should be removed to create space for the new block that contains the referenced word. The collection of rules for making this decision constitutes the cache's replacement algorithm.

 

Use of a cache memory


Mapping Functions

- There are several possible methods for determining where memory blocks are placed in the cache. It is instructive to describe these methods using a specific small example.
- Consider a cache consisting of 128 blocks of 16 words each, for a total of 2048 (2K) words, and assume that the main memory is addressable by a 16-bit address.
- The main memory has 64K words, which we will view as 4K blocks of 16 words each. For simplicity, we have assumed that consecutive addresses refer to consecutive words.

Direct Mapping


- The simplest way to determine cache locations in which to store memory blocks is the direct-mapping technique. In this technique, block j of the main memory maps onto block j modulo 128 of the cache, as depicted in Figure.
- Thus, whenever one of the main memory blocks 0, 128, 256 . . . are loaded into the cache, it is stored in cache block 0.

- Blocks 1, 129, 257 . . . are stored in cache block 1, and so on. Since more than one memory block is mapped onto a given cache block position, contention may arise for that position even when the cache is not full.
- For example, instructions of a program may start in block 1 and continue in block 129, possibly after a branch. As this program is executed, both of these blocks must be transferred to the block-1 position in the cache. Contention is resolved by allowing the new block to overwrite the currently resident block.
- With direct mapping, the replacement algorithm is trivial. Placement of a block in the cache is determined by its memory address. The memory address can be divided into three fields, as shown in Figure. The low-order 4 bits select one of 16 words in a block.
- When a new block enters the cache, the 7-bit cache block field determines the cache position in which this block must be stored. The high-order 5 bits of the memory address of the block are stored in 5 tag bits associated with its location in the cache.
- The tag bits identify which of the 32 main memory blocks mapped into this cache position is currently resident in the cache.

 

Direct-mapped cache


- As execution proceeds, the 7-bit cache block field of each address generated by the processor points to a particular block location in the cache.
- The high-order 5 bits of the address are compared with the tag bits associated with that cache location. If they match, then the desired word is in that block of the cache.
- If there is no match, then the block containing the required word must first be read from the main memory and loaded into the cache. The direct-mapping technique is easy to implement, but it is not very flexible.
- Consider the example shown in figure. The address from the processor is divided into two fields, a tag and an index. The tag consists of the higher significant bits of the address, which are stored with the data. The index is the lower significant bits of the address used to address the cache.
- When the memory is referenced, the index is first used to access a word in the cache. Then the tag stored in the accessed word is read and compared with the tag in the address. If the two tags are the same, indicating that the word is the one required, access is made to the addressed cache word.
- If the tags are not the same, indicating that the required word is not in the cache, reference is made to the main memory to find it.

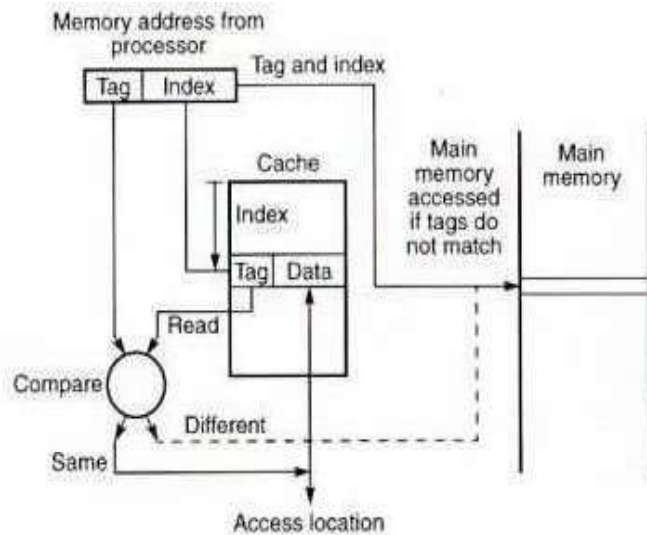

Cache with direct mapping

Associative Mapping


- Figure shows the most flexible mapping method, in which a main memory block can be placed into any cache block position. In this case, 12 tag bits are required to identify a memory block when it is resident in the cache.
- The tag bits of an address received from the processor are compared to the tag bits of each block of the cache to see if the desired block is present. This is called the associative-mapping technique. It gives complete freedom in choosing the cache location in which to place the memory block, resulting in a more efficient use of the space in the cache.

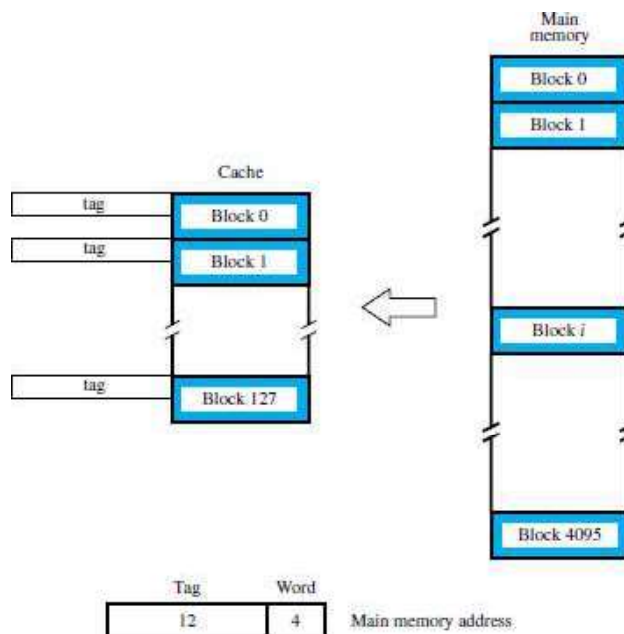

Associative-mapped cache

- When a new block is brought into the cache, it replaces (ejects) an existing block only if the cache is full. In this case, we need an algorithm to select the block to be replaced. Many replacement algorithms are possible.


- The complexity of an associative cache is higher than that of a direct-mapped cache, because of the need to search all 128 tag patterns to determine whether a given block is in the cache. To avoid a long delay, the tags must be searched in parallel. A search of this kind is called an associative search.
- A fully associative cache requires the cache to be composed of associative memory holding both the memory address and the data for each cached line. The incoming memory address is simultaneously compared with all stored addresses using the internal logic of associative memory, as shown in figure.
- If the match is found, the corresponding data is read out. Single words from anywhere within the main memory could be held in cache, if the associative part of the cache is capable of holding a full address.

 


Cache with fully associative mapping

Set-Associative Mapping

- Another approach is to use a combination of the direct- and associative-mapping techniques. The blocks of the cache are grouped into sets, and the mapping allows a block of the main memory to reside in any block of a specific set. Hence, the contention problem of the direct method is eased by having a few choices for block placement. At the same time, the hardware cost is reduced by decreasing the size of the associative search.
- An example of this set-associative-mapping technique is shown in Figure for a cache with two blocks per set. In this case, memory blocks 0, 64, 128, . . . 4032 map into cache set 0, and they can occupy either of the two block positions within this set. Having 64 sets means that the 6-bit set field of the address determines which set of the cache might contain the desired block.
- The tag field of the address must then be associatively compared to the tags of the two blocks of the set to check if the desired block is present. This two-way associative search is simple to implement.
- The number of blocks per set is a parameter that can be selected to suit the requirements of a particular computer. For the main memory and cache sizes in Figure, four blocks per set can be accommodated by a 5-bit set field, eight blocks per set by a 4-bit set field, and so on.
- The extreme condition of 128 blocks per set requires no set bits and corresponds to the fully-associative technique, with 12 tag bits. The other extreme of one block per set is the direct-mapping method. A cache that has k blocks per set is referred to as a k -way set-associative cache.

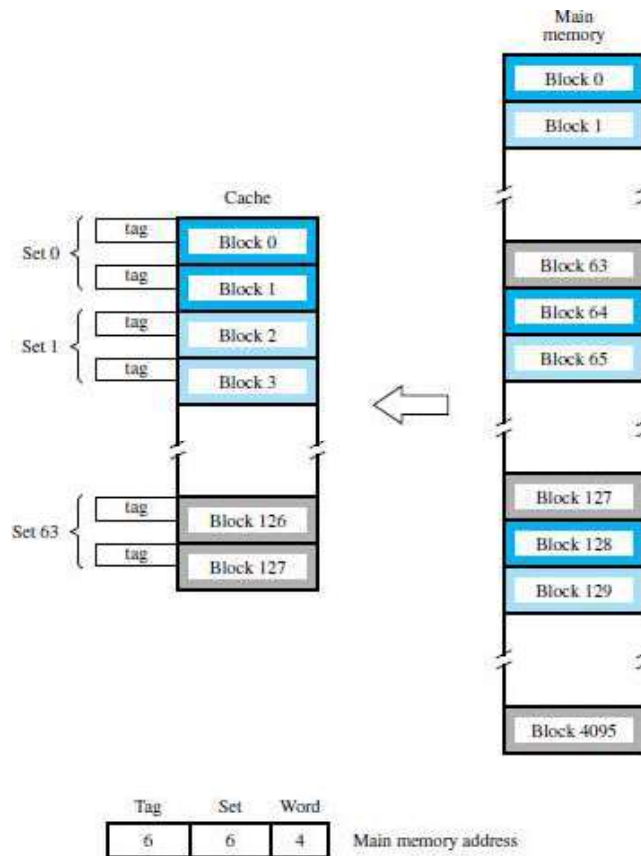

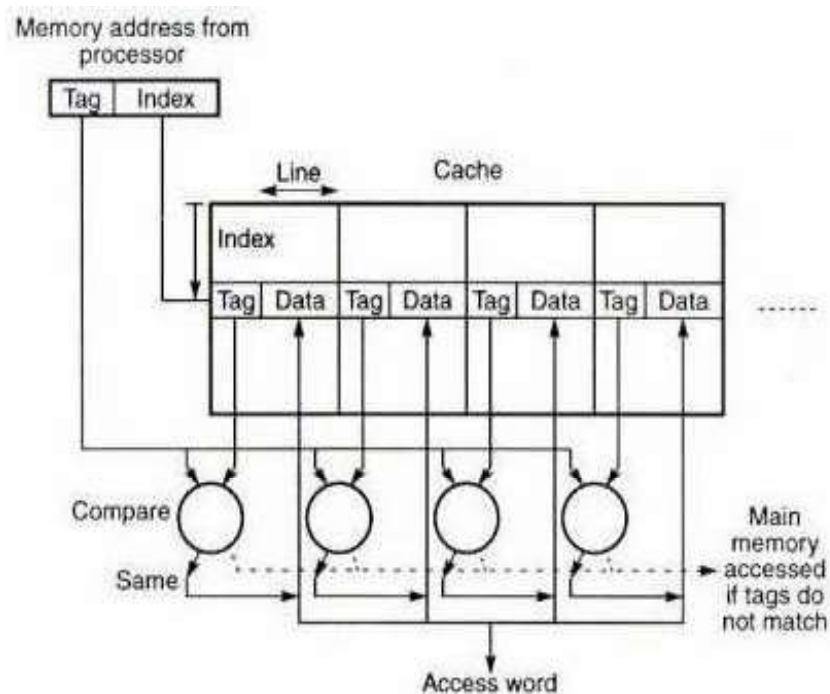Set-associative-mapped cache with two blocks per set



Cache with set associative mapping


- The cache is divided into sets of blocks. Each block in each set has a stored tag which, together with the index, completes the identification of the block. First, the index of the address from the processor is used to access the set. Then, comparators are used to compare all the tags of the selected set with the incoming tag. If a match is found, the corresponding location is accessed, otherwise, as before; an access to the main memory is made.

Replacement Algorithms

- In a direct-mapped cache, the position of each block is predetermined by its address; hence, the replacement strategy is trivial.
- In associative and set-associative caches there exists some flexibility. When a new block is to be brought into the cache and all the positions that it may occupy are full, the cache controller must decide which of the old blocks to overwrite.
- In general, the objective is to keep blocks in the cache that are likely to be referenced in the near future. But, it is not easy to determine which blocks are about to be referenced.
- Therefore, when a block is to be overwritten, it is sensible to overwrite the one that has gone the longest time without being referenced. This block is called the least recently used (LRU) block, and the technique is called the LRU replacement algorithm

VIRTUAL MEMORY:

- In most modern computer systems, the physical main memory is not as large as the address space of the processor. For example, a processor that issues 32-bit addresses has an addressable space of 4G bytes. The size of the main memory in a typical computer with a 32-bit processor may range from 1G to 4G bytes.
- If a program does not completely fit into the main memory, the parts of it not currently being executed are stored on a secondary storage device, typically a magnetic disk. As these parts are needed for execution, they must first be brought into the main memory, possibly replacing other parts that are already in the memory. These actions are performed automatically by the operating system, using a scheme known as virtual memory.
- Application programmers need not be aware of the limitations imposed by the available main memory. They prepare programs using the entire address space of the processor.
- Under a virtual memory system, programs, and hence the processor, reference instructions and data in an address space that is independent of the available physical main memory space. The binary addresses that the processor issues for either instructions or data are called virtual or logical addresses. These addresses are translated into physical addresses by a combination of hardware and software actions.
- If a virtual address refers to a part of the program or data space that is currently in the physical memory, then the contents of the appropriate location in the main memory are accessed immediately. Otherwise, the contents of the referenced address must be brought into a suitable location in the memory before they can be used.
- Figure shows a typical organization that implements virtual memory. A special hardware unit, called the Memory Management Unit (MMU), keeps track of which parts of the virtual address space are in the physical memory.
- When the desired data or instructions are in the main memory, the MMU translates the virtual address into the corresponding physical address. Then, the requested memory access proceeds in the usual manner. If the data are not in the main memory, the MMU causes the operating system to transfer the data from the disk to the memory.

 

Virtual memory organization


Address Translation

- A virtual-memory address-translation method based on the concept of fixed-length pages is shown schematically in Figure. Each virtual address generated by the processor is interpreted as a virtual page number (high-order bits) followed by an offset (low-order bits) that specifies the location of a particular byte (or word) within a page.
- Information about the main memory location of each page is kept in a **page table**. This information includes the main memory address where the page is stored and the current status of the page. An area in the main memory that can hold one page is called a **page frame**.
- The starting address of the page table is kept in a page table base register. By adding the virtual page number to the contents of this register, the address of the corresponding entry in the page table is obtained. The contents of this location give the starting address of the page if that page currently resides in the main memory.
- Each entry in the page table also includes some control bits that describe the status of the page while it is in the main memory.
- One bit indicates the validity of the page, that is, whether the page is actually loaded in the main memory. It allows the operating system to invalidate the page without actually removing it. (Valid bit)
- Another bit indicates whether the page has been modified during its residency in the memory. As in cache memories, this information is needed to determine whether the page should be written back to the disk before it is removed from the main memory to make room for another page. (Modify bit)
- Other control bits indicate various restrictions that may be imposed on accessing the page. For example, a program may be given full read and write permission, or it may be restricted to read accesses only. (Access control bits)

The following steps are used in address translation:

1. Virtual address generated by the processor is divided into two parts as virtual page number and offset.
2. The virtual page number in the address is added with the contents of page table base register to get the required entry in the page table.

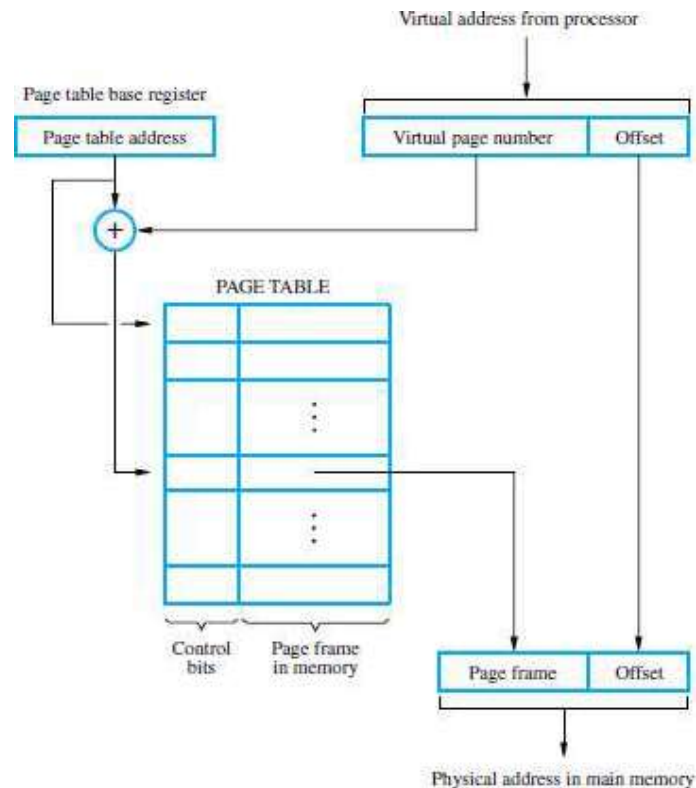3. The page table entry provides the address of page in memory.
4. Physical address is generated by combining the page frame address with the offset field of the virtual address.



Virtual-memory address translation


TRANSLATION LOOKASIDE BUFFER

- The page table information is used by the MMU for every read and write access. Ideally, the page table should be situated within the MMU. Unfortunately, the page table may be rather large. Since the MMU is normally implemented as part of the processor chip, it is impossible to include the complete table within the MMU. Instead, a copy of only a small portion of the table is accommodated within the MMU, and the complete table is kept in the main memory.
- The portion maintained within the MMU consists of the entries corresponding to the most recently accessed pages. They are stored in a small table, usually called the Translation Lookaside Buffer (TLB).
- The TLB functions as a cache for the page table in the main memory. Each entry in the TLB includes a copy of the information in the corresponding entry in the page table. In addition, it includes the virtual address of the page, which is needed to search the TLB for a particular page. Figure shows a possible organization of a TLB that uses the associative-mapping technique. Set-associative mapped TLBs are also found in commercial products.

Address translation proceeds as follows:

1. Processor generates a virtual address,
2. MMU looks in the TLB for the referenced page.
3. If the page table entry for this page is found in the TLB, the physical address is obtained immediately.

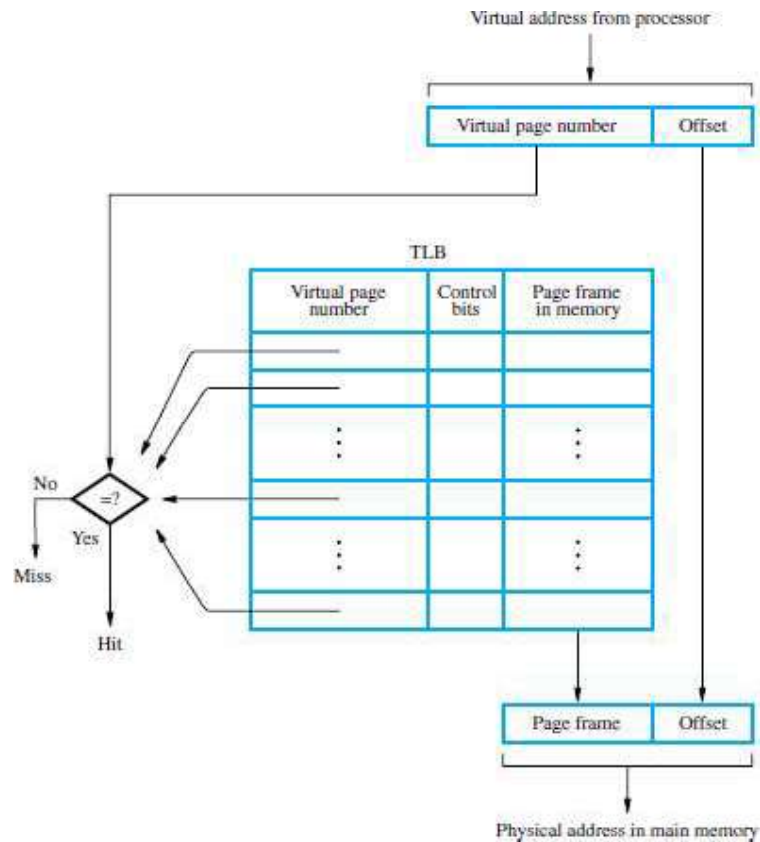4. If there is a miss in the TLB, then the required entry is obtained from the page table in the main memory and the TLB is updated.
5. Then TLB is updated accordingly.



Use of an associative-mapped TLB

Page Faults:

- When a program generates an access request to a page that is not in the main memory, a page fault is said to have occurred. The entire page must be brought from the disk into the memory before access can proceed.
- When it detects a page fault, the MMU asks the operating system to intervene by raising an exception (interrupt). Processing of the program that generated the page fault is interrupted, and control is transferred to the operating system.
- The operating system copies the requested page from the disk into the main memory and transfers the control back to the interrupted task.

Page replacement:


- If a new page is brought from the disk when the main memory is full, it must replace one of the resident pages. Concepts similar to the LRU replacement algorithm can be applied to page replacement, and the control bits in the page table entries can be used to record usage history.
- One simple scheme is based on a control bit that is set to 1 whenever the corresponding page is referenced (accessed). The operating system periodically clears this bit in all page table entries, thus providing a simple way of determining which pages have not been used recently.

Write operation:

- A modified page has to be written back to the disk before it is removed from the main memory. It is important to note that the write-through protocol, which is useful in the framework of cache memories, is not suitable for virtual memory. The access time of the disk is so long that it does not make sense to access it frequently to write small amounts of data.

ACCESSING I/O DEVICES:

- The components of a computer system communicate with each other through an interconnection network, as shown in Figure. The interconnection network consists of circuits needed to transfer information between the processor, the memory unit, and a number of I/O devices.
- Load and Store instructions use addressing modes to generate effective addresses that identify the desired locations. This idea of using addresses to access various locations in the memory can be extended to deal with the I/O devices as well.

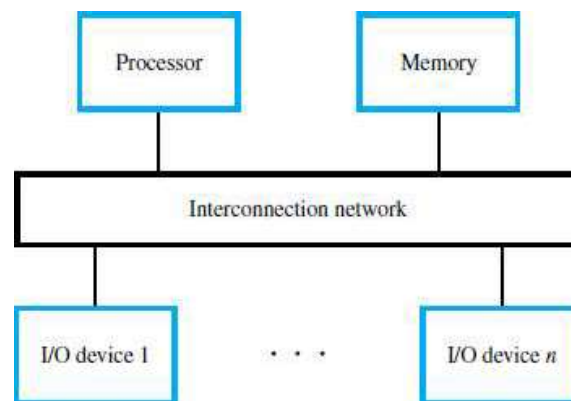

A computer system

- For this purpose, each I/O device must appear to the processor as consisting of some addressable locations, just like the memory. Some addresses in the address space of the processor are assigned to these I/O locations, rather than to the main memory.
- These locations are usually implemented as bit storage circuits (flip-flops) organized in the form of registers. It is customary to refer to them as I/O registers. Since the I/O devices and the memory share the same address space, this arrangement is called memory-mapped I/O. It is used in most computers.
- With memory-mapped I/O, any machine instruction that can access memory can be used to transfer data to or from an I/O device. For example, if DATAIN is the address of a register in an input device, the instruction

Load R2, DATAIN

reads the data from the DATAIN register and loads them into processor register R2.


- Similarly, the instruction

Store R2, DATAOUT

sends the contents of register R2 to location DATAOUT, which is a register in an output device.

I/O Device Interface

- An I/O device is connected to the interconnection network by using a circuit, called the device interface, which provides the means for data transfer and for the exchange of status and control information needed to facilitate the data transfers and govern the operation of the device. The interface includes some registers that can be accessed by the processor.
- One register may serve as a buffer for data transfers, another may hold information about the current status of the device, and yet another may store the information that controls the operational behaviour of the device. These data, status, and control registers are accessed by program instructions as if they were memory locations. Typical transfers of information are between I/O registers and the registers in the processor.
- Figure illustrates how the keyboard and display devices are connected to the processor from the software point of view.

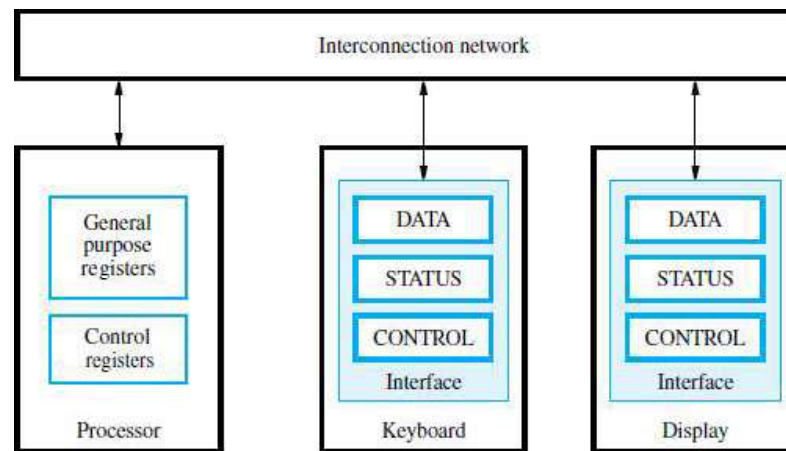


The connection for processor, keyboard, and display


Program-Controlled I/O

- Let us begin the discussion of input/output issues by looking at two essential I/O devices for human-computer interaction—keyboard and display.
- Consider a task that reads characters typed on a keyboard, stores these data in the memory, and displays the same characters on a display screen. A simple way of implementing this task is to write a program that performs all functions needed to realize the desired action. This method is known as program-controlled I/O.
- In addition to transferring each character from the keyboard into the memory, and then to the display, it is necessary to ensure that this happens at the right time. An input character must be read in response to a key being pressed.
- For output, a character must be sent to the display only when the display device is able to accept it. The rate of data transfer from the keyboard to a computer is limited by the typing speed of the user, which is unlikely to exceed a few characters per second.
- The rate of output transfers from the computer to the display is much higher. It is determined by the rate at which characters can be transmitted to and displayed on the display device, typically several thousand characters per second.
- However, this is still much slower than the speed of a processor that can execute billions of instructions per second. The difference in speed between the processor and I/O devices creates the need for mechanisms to synchronize the transfer of data between them.

- One solution to this problem involves a signaling protocol. On output, the processor sends the first character and then waits for a signal from the display that the next character can be sent. It then sends the second character, and so on. An input character is obtained from the keyboard in a similar way.
- The processor waits for a signal indicating that a key has been pressed and that a binary code that represents the corresponding character is available in an I/O register associated with the keyboard. Then the processor proceeds to read that code.
- The keyboard includes a circuit that responds to a key being pressed by producing the code for the corresponding character that can be used by the computer. We will assume that ASCII code is used, in which each character code occupies one byte.
- Let KBD_DATA be the address label of an 8-bit register that holds the generated character. Also, let a signal indicating that a key has been pressed be provided by setting to 1 a flip-flop called KIN, which is a part of an eight-bit status register, KBD_STATUS.
- The processor can read the status flag KIN to determine when a character code has been placed in KBD_DATA. When the processor reads the status flag to determine its state, we say that the processor polls the I/O device.
- The display includes an 8-bit register, which we will call DISP_DATA, used to receive characters from the processor. It also must be able to indicate that it is ready to receive the next character; this can be done by using a status flag called DOUT, which is one bit in a status register, DISP_STATUS.

 

(a) Keyboard interface

 

(b) Display interface

Registers in the keyboard and display interfaces

- A program is needed to perform the task of reading the characters produced by the keyboard, storing these characters in the memory, and sending them to the display. To perform I/O transfers, the processor must execute machine instructions that check the state of the status flags and transfer data between the processor and the I/O devices.

INTERRUPTS:

- Data transfer between the CPU and the peripherals is initiated by the CPU. But the CPU cannot start the transfer unless the peripheral is ready to communicate with the CPU. When a device is ready to communicate with the CPU, it generates an interrupt signal. A number of input-output devices are attached to the computer and each device is able to generate an interrupt request.
- The main job of the interrupt system is to identify the source of the interrupt. There is also a possibility that several devices will request simultaneously for CPU communication. Then, the interrupt system has to decide which device is to be serviced first.

Priority Interrupt

- A priority interrupt is a system which decides the priority at which various devices, which generates the interrupt signal at the same time, will be serviced by the CPU. The system has authority to decide which conditions are allowed to interrupt the CPU, while some other interrupt is being serviced. Generally, devices with high speed transfer such as magnetic disks are given high priority and slow devices such as keyboards are given low priority.
- When two or more devices interrupt the computer simultaneously, the computer services the device with the higher priority first.

Types of Interrupts:

Hardware Interrupts

- When the signal for the processor is from an external device or hardware then this interrupt is known as hardware interrupt. Let us consider an example: when we press any key on our keyboard to do some action, then this pressing of the key will generate an interrupt signal for the processor to perform certain action. Such an interrupt can be of two types:

Maskable Interrupt

- The hardware interrupts which can be delayed when a much high priority interrupt has occurred at the same time.

Non Maskable Interrupt

- The hardware interrupts which cannot be delayed and should be processed by the processor immediately.

Software Interrupts

- The interrupt that is caused by any internal system of the computer system is known as a software interrupt. It can also be of two types:

Normal Interrupt


- The interrupts that are caused by software instructions are called normal software interrupts.

Exception

- Unplanned interrupts which are produced during the execution of some program are called exceptions, such as division by zero.

DIRECT MEMORY ACCESS:

- Blocks of data are often transferred between the main memory and I/O devices such as disks. This section discusses a technique for controlling such transfers without frequent, program-controlled intervention by the processor.
- Data are transferred from an I/O device to the memory by first reading them from the I/O device using an instruction such as Load R2, DATAIN which loads the data into a processor register. Then, the data read are stored into a memory location. The reverse process takes place for transferring data from the memory to an I/O device.
- An instruction to transfer input or output data is executed only after the processor determines that the I/O device is ready, either by polling its status register or by waiting for an interrupt request.
- In either case, considerable overhead is incurred, because several program instructions must be executed involving many memory accesses for each data word transferred. When transferring a block of data, instructions are needed to increment the memory address and keep track of the word count.
- The use of interrupts involves operating system routines which incur additional overhead to save and restore processor registers, the program counter, and other state information.
- An alternative approach is used to transfer blocks of data directly between the main memory and I/O devices, such as disks.
- A special control unit is provided to manage the transfer, without continuous intervention by the processor. This approach is called direct memory access, or DMA. The unit that controls DMA transfers is referred to as a DMA controller. It may be part of the I/O device interface, or it may be a separate unit shared by a number of I/O devices.
- The DMA controller performs the functions that would normally be carried out by the processor when accessing the main memory.
- For example, in the case of a disk, the processor provides the disk controller with information to identify where the data is located on the disk.

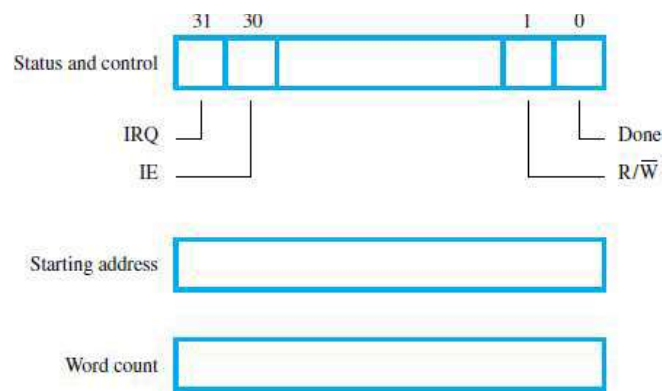


Typical registers in a DMA controller

- When the controller has completed transferring a block of data and is ready to receive another command, it sets the Done flag to 1. Bit 30 is the Interrupt-enable flag, IE.
- When this flag is set to 1, it causes the controller to raise an interrupt after it has completed transferring a block of data. Finally, the controller sets the IRQ bit to 1 when it has requested an interrupt.
- Figure shows how DMA controllers may be used in a computer system. One DMA controller connects a high-speed Ethernet to the computer's I/O bus.

- The disk controller, which controls two disks, also has DMA capability and provides two DMA

channels. It can perform two independent DMA operations, as if each disk had its own DMA controller.

- The registers needed to store the memory address, the word count, and so on, are duplicated, so that one set can be used with each disk.
- To start a DMA transfer of a block of data from the main memory to one of the disks, an OS routine writes the address and word count information into the registers of the disk controller. The DMA controller proceeds independently to implement the specified operation.
- When the transfer is completed, this fact is recorded in the status and control register of the DMA channel by setting the Done bit.
- At the same time, if the IE bit is set, the controller sends an interrupt request to the processor and sets the IRQ bit. The status register may also be used to record other information, such as whether the transfer took place correctly or errors occurred.

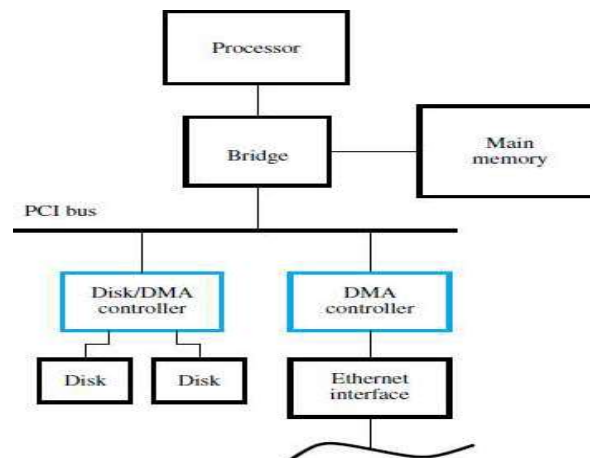


Use of DMA controllers in a computer system

Bus Arbitration

- The device that is allowed to initiate data transfers on the bus at any given time is called bus master.
- Bus Arbitration is the process by which the next device to become the bus master is selected and bus master ship is transferred to it. The selection bus master is usually done on the priority basis. Approaches to bus Arbitration:
 - Centralized Bus Arbitration
 - Distributed bus arbitration Centralized Bus Arbitration Scheme:
- In centralized bus arbitration, a single bus arbiter performs the required arbitration. The bus arbiter may be the processor or a separate controller connected to the bus.
 - There are different arbitration scheme that use centralized bus arbitration approach. These schemes are: Daisy chaining, Polling method, Independent request

Daisy chaining:

- Daisy chain method uses three lines.
- **Bus Request Line (BR):** This is a wired-OR line. The controller only knows that a request has been made by a device, but doesn't know which device made the request.
- **Bus Grant Line (BG):** Bus grant signal is propagated through all the devices through this line.
- **Bus Busy (BBSY):** The current bus master indicates to all devices that it is using the bus by activating this open-collector line called Bus Busy.

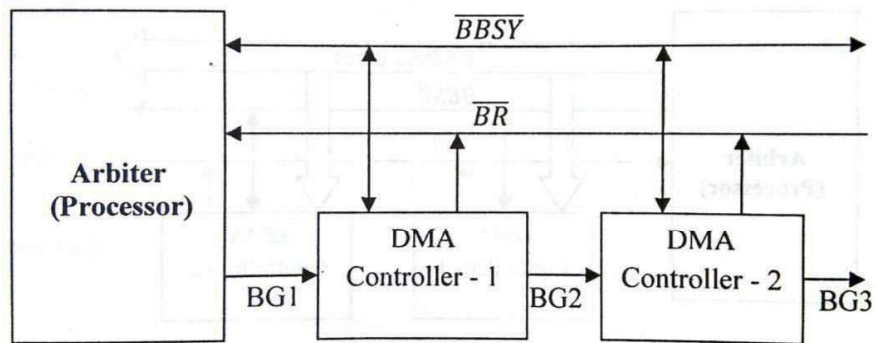

- In daisy chaining method, all masters use the same bus request line for requesting the bus. In response to the bus request, the controller sends a bus grant signal BG if the bus is free. This grant signal is propagated to the masters until it reaches the master which requests the bus. This master blocks the bus grant signal, activates the bus busy line and gets the control of the bus. If more than one device makes a request at the same time, then the device that is closer to the arbiter will get the bus. This is known as daisy chaining.


Advantages:

- It is a simple and cheaper method.
- It requires the least number of lines and this number is independent of the number of masters in the system.

Disadvantages:

- The propagation delay of bus grant signal is proportional to the number of masters in the system. This makes arbitration time slow and hence limits the number of masters in the system.
- The priority of the master is fixed by its physical location.
- Failure of any one master causes the whole system to fail.

Polling Method:

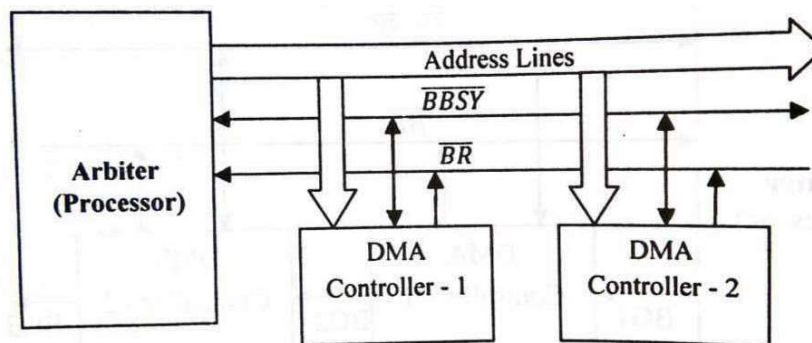


- Similar to daisy chain method, in polling method also all masters use the same line for bus request. In this method the controller assigns addresses for the masters in the system. All the masters are connected to a local address bus.
- In response to bus request, the controller places the address of the bus master on the address bus. The requesting master recognizes its address, activates the busy line and gets the control of the bus.

Advantages:

- The priority can be changed by altering the polling sequence stored in the controller.
- If one module fails, the entire system does not fail.

Independent Request Method:

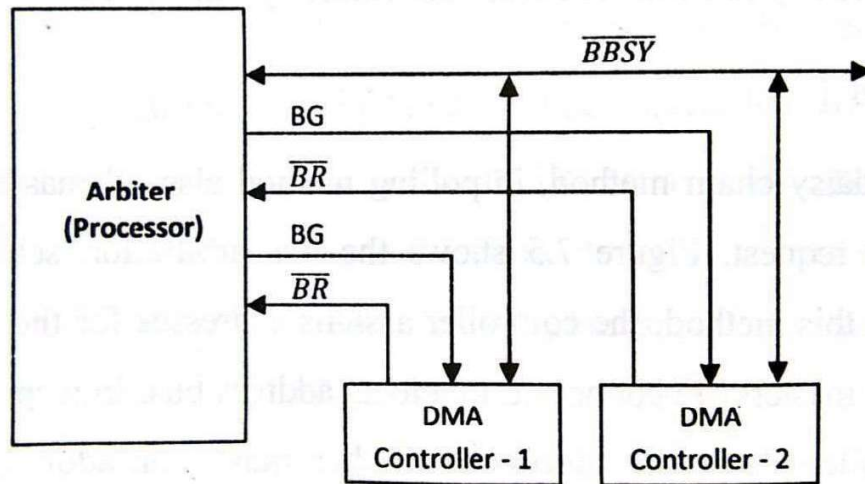- In this scheme each master has a separate pair of bus request and bus grant lines and each pair has a priority assigned to it.
- The built in priority decoder within the controller selects the highest priority request and asserts the corresponding grant signal.




Advantage:

- Due to separate pairs of bus request and bus grant signals, arbitration is fast and is independent of the number of masters in the system.

Disadvantage:

- It requires more bus request and grant signals.

Distributed bus arbitration:

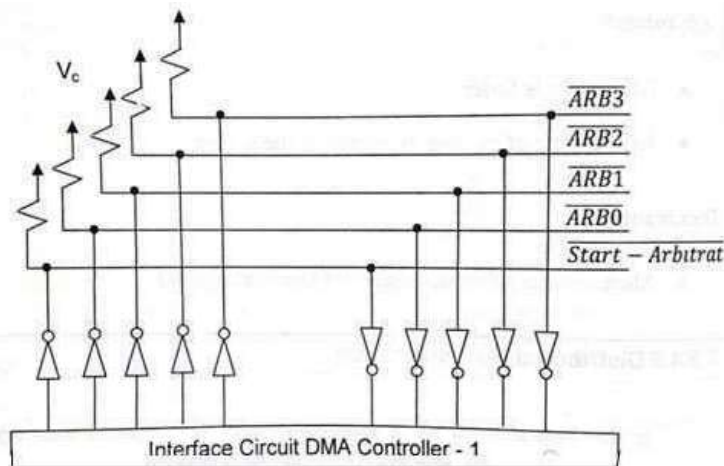


- In distributed bus arbitration, all devices participate in the selection of the next bus master. In this scheme each device is assigned with a 4-bit identification number.
- When a device requests for the control of the bus, it enables the $\overline{\text{Start-Arbitrat}}$ signal and places its 4-bit ID on arbitration lines through $\overline{\text{ARB3}}$.
- These arbitration lines are open collectors. Therefore more than one device can place their ID to indicate that they also need the control of the bus.
- In this scheme the device which has the highest ID number has the highest priority.

Advantages:


- Decentralized arbitration provides higher reliability.
- The operation of the bus is not dependent on any single device.

ARBITRATION

- There are occasions when two or more entities contend for the use of a single resource in a computer system. For example, two devices may need to access a given slave at the same time. In such cases, it is necessary to decide which device will access the slave first.
- The decision is usually made in an arbitration process performed by an arbiter circuit. The arbitration process starts by each device sending a request to use the shared resource. The arbiter associates priorities with individual requests.
- If it receives two requests at the same time, it grants the use of the slave to the device having the higher priority first.
- To illustrate the arbitration process, we consider the case where a single bus is the shared resource. The device that initiates data transfer requests on the bus is the bus master.
- It is possible that several devices in a computer system need to be bus masters to transfer data. For example, an I/O device needs to be a bus master to transfer data directly to or from the computer's memory. Since the bus is a single shared facility, it is essential to provide orderly access to it by the bus masters.
- If a single Bus-request is activated, the arbiter activates the corresponding Bus-grant. This indicates to the selected master that it may now use the bus for transferring data. When the transfer is completed, that master deactivates its Bus-request, and the arbiter deactivates its Bus-grant.

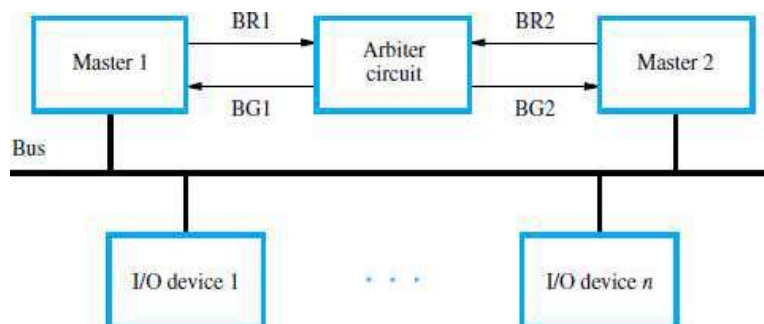

Bus arbitration

 

Granting use of the bus based on priorities

- Figure illustrates a possible sequence of events for the case of three masters. Assume that master 1 has the highest priority, followed by the others in increasing numerical order. Master 2 sends a request to use the bus first. Since there are no other requests, the arbiter grants the bus to this master by asserting BG2.
- When master 2 completes its data transfer operation, it releases the bus by deactivating BR2. By that time, both masters 1 and 3 have activated their request lines. Since device 1 has a higher priority, the arbiter activates BG1 after it deactivates BG2, thus granting the bus to master 1.
- Later, when master 1 releases the bus by deactivating BR1, the arbiter deactivates BG1 and activates BG3 to grant the bus to master 3. Note that the bus is granted to master 1 before master 3 even though master 3 activated its request line before master 1.

INTERFACE CIRCUITS:


- The I/O interface of a device consists of the circuitry needed to connect that device to the bus. On one side of the interface are the bus lines for address, data, and control. On the other side are the connections needed to transfer data between the interface and the I/O device. This side is called a *port*, and it can be either a parallel or a serial port.
- A parallel port transfers multiple bits of data simultaneously to or from the device. A serial port sends and receives data one bit at a time. Communication with the processor is the same for both formats; the conversion from a parallel to a serial format and vice versa takes place inside the interface circuit.
- Before we present specific circuit examples, let us recall the functions of an I/O interface. I/O interface does the following:
 - Provides a register for temporary storage of data
 - Includes a status register containing status information that can be accessed by the processor
 - Includes a control register that holds the information governing the behavior of the interface
 - Contains address-decoding circuitry to determine when it is being addressed by the processor
 - Generates the required timing signals
 - Performs any format conversion that may be necessary to transfer data between the processor and the I/O device, such as parallel-to-serial conversion in the case of a serial port.

Parallel Interface

- First, we describe an interface circuit for an 8-bit input port that can be used for connecting a simple input device, such as a keyboard. Then, we describe an interface circuit for an 8-bit output port, which can be used with an output device such as a display.

Input Interface

- Figure shows a circuit that can be used to connect a keyboard to a processor. Assume that interrupts are not used, so there is no need for a control register. There are only two registers: a data register, KBD_DATA, and a status register, KBD_STATUS. The latter contains the keyboard status flag, KIN.
- A typical keyboard consists of mechanical switches that are normally open. When a key is pressed, its switch closes and establishes a path for an electrical signal. This signal is detected by an encoder circuit that generates the ASCII code for the corresponding character.
- A difficulty with such mechanical pushbutton switches is that the contacts bounce when a key is pressed, resulting in the electrical connection being made then broken several times before the switch settles in the closed position. Although bouncing may last only one or two milliseconds, this is long enough for the computer to erroneously interpret a single pressing of a key as the key being pressed and released several times.
- The effect of bouncing can be eliminated using a simple debouncing circuit, which could be part of the keyboard hardware or may be incorporated in the encoder circuit. Alternatively, switch bouncing can be dealt with in software.
- The software detects that a key has been pressed when it observes that the keyboard status flag, KIN, has been set to 1. The I/O routine can then introduce sufficient delay before reading the contents of the input buffer, KBD_DATA, to ensure that bouncing has subsided.
- When debouncing is implemented in hardware, the I/O routine can read the input character as soon as it detects that KIN is equal to 1.

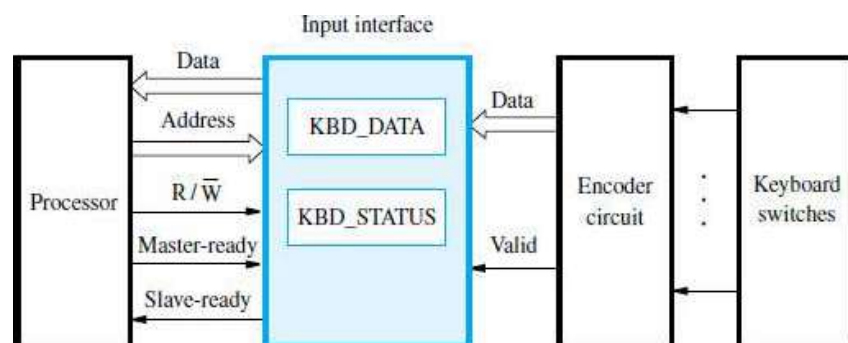


Keyboard to processor connection

- The output of the encoder in Figure consists of one byte of data representing the encoded character and one control signal called Valid. When a key is pressed, the Valid signal changes from 0 to 1, causing the ASCII code of the corresponding character to be loaded into the KBD_DATA register and the status flag KIN to be set to 1.
- The status flag is cleared to 0 when the processor reads the contents of the KBD_DATA register. The interface circuit is shown connected to an asynchronous bus on which transfers are controlled by the handshake signals Master-ready and Slave-ready. The bus has one other control line, R/\bar{W} , which indicates a Read operation when equal to 1.

- Figure shows a possible circuit for the input interface. There are two addressable locations in this **Output Interface**

- Let us now consider the output interface shown in Figure, which can be used to connect an output device such as a display. We have assumed that the display uses two handshake signals, New-data and Ready, in a manner similar to the handshake between the bus signals Master-ready and Slave-ready.
- When the display is ready to accept a character, it asserts its Ready signal, which causes the DOUT flag in the DISP_STATUS register to be set to 1.
- When the I/O routine checks DOUT and finds it equal to 1, it sends a character to DISP_DATA. This clears the DOUT flag to 0 and sets the New-data signal to 1. In response, the display returns Ready to 0 and accepts and displays the character in DISP_DATA.
- When it is ready to receive another character, it asserts Ready again, and the cycle repeats.

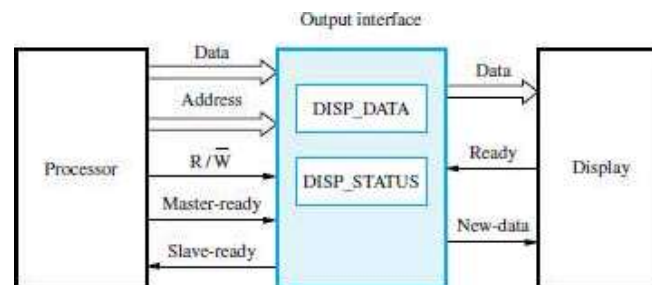

Display to processor connection

Serial Interface

- A serial interface is used to connect the processor to I/O devices that transmit data one bit at a time. Data are transferred in a bit-serial fashion on the device side and in a bit-parallel fashion on the processor side. The transformation between the parallel and serial formats is achieved with shift registers that have parallel access capability.
- A block diagram of a typical serial interface is shown in Figure. The input shift register accepts bit-serial input from the I/O device. When all 8 bits of data have been received, the contents of this shift register are loaded in parallel into the DATAIN register. Similarly, output data in the DATAOUT register are transferred to the output shift register, from which the bits are shifted out and sent to the I/O device.
- Two status flags, which we will refer to as SIN and SOUT, are maintained by the Status and control block. The SIN flag is set to 1 when new data are loaded into DATAIN from the shift register, and cleared to 0 when these data are read by the processor.
- The SOUT flag indicates whether the DATAOUT register is available. It is cleared to 0 when the processor writes new data into DATAOUT and set to 1 when data are transferred from DATAOUT to the output shift register.

UNIVERSAL SERIAL BUS (USB):

- The Universal Serial Bus (USB) is the most widely used interconnection standard. A large variety of devices are available with a USB connector, including mice, memory keys, disk drives, printers, cameras, and many more.
- The commercial success of the USB is due to its simplicity and low cost. The original USB specification supports two speeds of operation, called low-speed (1.5 Megabits/s) and full-speed

(12 Megabits/s). Later, USB 2, called High-Speed USB, was introduced. It enables data transfers at speeds up to 480 Megabits/s.

- As I/O devices continued to evolve with even higher speed requirements, USB 3 (called Super speed) was developed. It supports data transfer rates up to 5 Gigabits/s.
- The USB has been designed to meet several key objectives:
 - Provide a simple, low-cost, and easy to use interconnection system
 - Accommodate a wide range of I/O devices and bit rates, including Internet connections, and audio and video applications
 - Enhance user convenience through a “plug-and-play” mode of operation

Device Characteristics

- The kinds of devices that may be connected to a computer cover a wide range of functionality. The speed, volume, and timing constraints associated with data transfers to and from these devices vary significantly.
- In the case of a keyboard, one byte of data is generated every time a key is pressed, which may happen at any time. These data should be transferred to the computer promptly. Since the event of pressing a key is not synchronized to any other event in a computer system, the data generated by the keyboard are called asynchronous.
- Furthermore, the rate at which the data are generated is quite low. It is limited by the speed of the human operator to about 10 bytes per second, which is less than 100 bits per second.
- Consider now a different source of data. Many computers have a microphone, either externally attached or built in. The sound picked up by the microphone produces an analog electrical signal, which must be converted into a digital form before it can be handled by the computer. This is accomplished by sampling the analog signal periodically.
- For each sample, an analog-to-digital (A/D) converter generates an n -bit number representing the magnitude of the sample. The number of bits, n , is selected based on the desired precision with which to represent each sample.
- Later, when these data are sent to a speaker, a digital to- analog (D/A) converter is used to restore the original analog signal from the digital format. A similar approach is used with video information from a camera.
- The sampling process yields a continuous stream of digitized samples that arrive at regular intervals, synchronized with the sampling clock. Such a data stream is called isochronous, meaning that successive events are separated by equal periods of time. A signal must be sampled quickly enough to track its highest-frequency components.
- An important requirement in dealing with sampled voice or music is to maintain precise timing in the sampling and replay processes. A high degree of jitter (variability in sample timing) is unacceptable. Hence, the data transfer mechanism between a computer and a music system must maintain consistent delays from one sample to the next. Otherwise, complex buffering and retiming circuitry would be needed.
- Data transfers for images and video have similar requirements, but require much higher data transfer rates.
- To maintain the picture quality of commercial television, an image should be represented by about 160 kilobytes and transmitted 30 times per second. Together with control information, this yields a total bit rate of 44 Megabits/s. Higher-quality images, as in HDTV (High Definition TV), require higher rates.
- Large storage devices such as magnetic and optical disks present different requirements. Their connection to the computer requires a data transfer bandwidth of at least 40 or 50 Megabits/s.

- Delays on the order of milliseconds are introduced by the movement of the mechanical components in the disk mechanism. Hence, a small additional delay introduced while transferring data to or from the computer is not important, and jitter is not an issue. However, the transfer mechanism must guarantee data correctness.


Plug-and-Play

- When an I/O device is connected to a computer, the operating system needs some information about it. It needs to know what type of device it is so that it can use the appropriate device driver. It also needs to know the addresses of the registers in the device's interface to be able to communicate with it.
- The USB standard defines both the USB hardware and the software that communicates with it. Its plug-and-play feature means that when a new device is connected, the system detects its existence automatically.
- The software determines the kind of device and how to communicate with it, as well as any special requirements it might have. As a result, the user simply plugs in a USB device and begins to use it, without having to get involved in any of these details.
- The USB is also hot-pluggable, which means a device can be plugged into or removed from a USB port while power is turned on.

USB Architecture

- The USB uses point-to-point connections and a serial transmission format. When multiple devices are connected, they are arranged in a tree structure as shown in Figure. Each node of the tree has a device called a hub, which acts as an intermediate transfer point between the host computer and the I/O devices.
- At the root of the tree, a root hub connects the entire tree to the host computer. The leaves of the tree are the I/O devices: a mouse, a keyboard, a printer, an Internet connection, a camera, or a speaker. The tree structure makes it possible to connect many devices using simple point-to-point serial links.
- If I/O devices are allowed to send messages at any time, two messages may reach the hub at the same time and interfere with each other. For this reason, the USB operates strictly on the basis of polling.
- A device may send a message only in response to a poll message from the host processor. Hence, no two devices can send messages at the same time. This restriction allows hubs to be simple, low-cost devices.
- Each device on the USB, whether it is a hub or an I/O device, is assigned a 7-bit address. This address is local to the USB tree and is not related in any way to the processor's address space. The root hub of the USB, which is attached to the processor, appears as a single device.
- The host software communicates with individual devices by sending information to the root hub, which it forwards to the appropriate device in the USB tree.
- When a device is first connected to a hub, or when it is powered on, it has the address 0. Periodically, the host polls each hub to collect status information and learn about new devices that may have been added or disconnected.

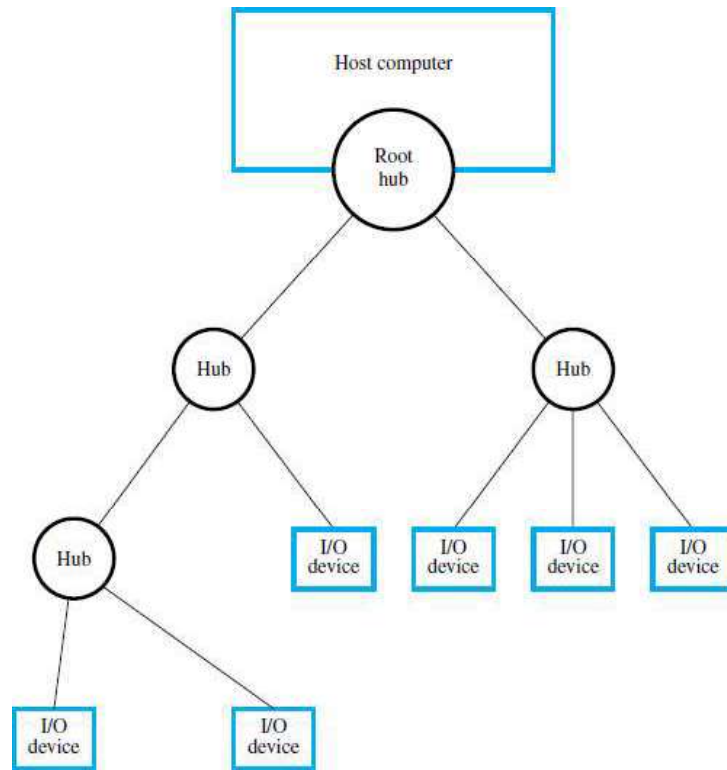- When the host is informed that a new device has been connected, it reads the information in a special memory in the device's USB interface to learn about the device's capabilities. It then assigns the device a unique
- USB address and writes that address in one of the device's interface registers. It is this initial connection procedure that gives the USB its plug-and-play capability.



Universal Serial Bus tree structure

Isochronous Traffic on USB

- An important feature of the USB is its ability to support the transfer of isochronous data in a simple manner. As mentioned earlier, isochronous data need to be transferred at precisely timed regular intervals.
- To accommodate this type of traffic, the root hub transmits a uniquely recognizable sequence of bits over the USB tree every millisecond. This sequence of bits, called a Start of Frame character, acts as a marker indicating the beginning of isochronous data, which are transmitted after this character. Thus, digitized audio and video signals can be transferred in a regular and precisely timed manner.